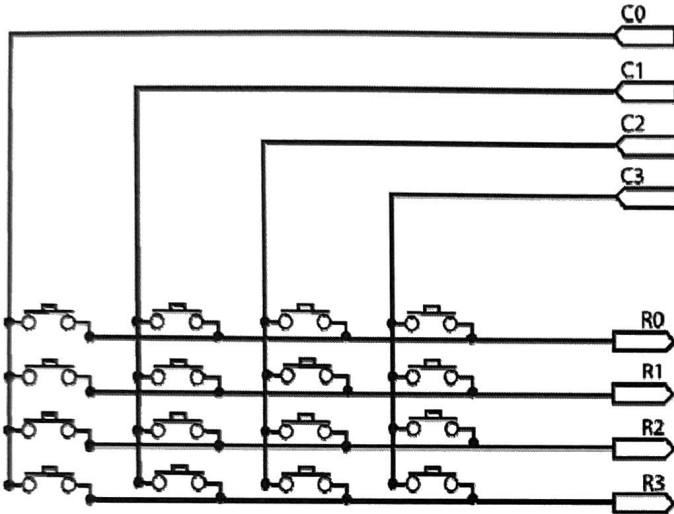


Adding peripheral and interface chips to your microcontroller. Why bother?

- Add new functionality to the system
- Relieve the micro of burdensome tasks
- Alter signal types (digital to analog, etc.)
- Alter signal levels (voltage, current, power)


EXAMPLE: Adding a "MATRIX" keypad to your kit



We could use port 1 on the microcontroller to "read" the keypad!


1

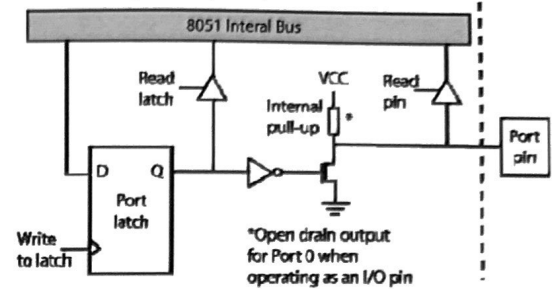Here is the internal diagram of a port 1 pin:



First, write a "1" to this pin to set it up for use as an input port. Discuss approach for reading a keypress.

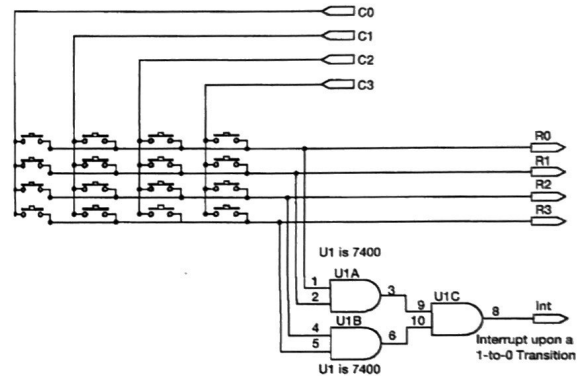Could add some additional logic to try to minimize the micro's burden:




2

This task is complicated by switch "bounce":



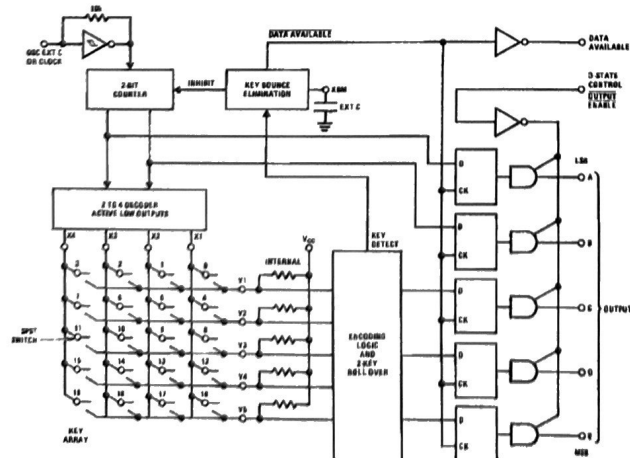
Reading the keypad is a burdensome task. Get help! 74C922:




3

Signal Conditioning with OP-AMPS:

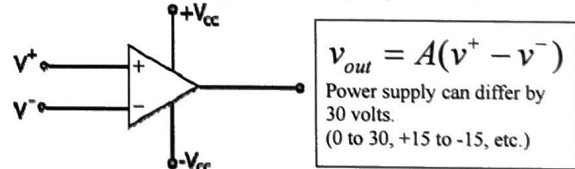Example: LM358 → an 8 pin IC with 2 op-amps on board



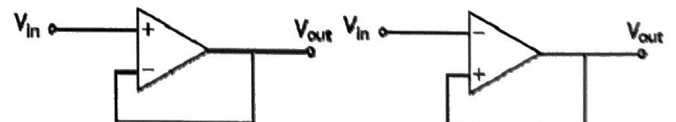OP-AMPS are generally configured with feedback. Consider these two possibilities:



$$v_{out} = A(v_{in} - v_{out})$$

$$\text{let } A \rightarrow \infty$$

$$0 = v_{in} - v_{out}$$

$$v_{out} = v_{in}$$

**STABLE
NEGATIVE FEEDBACK**

**USE THIS CIRCUIT!
☺ A BUFFER**

$$v_{out} = A(v_{out} - v_{in})$$

$$\text{let } A \rightarrow \infty$$

$$0 = v_{out} - v_{in}$$

$$v_{out} = v_{in}$$


**UNSTABLE
POSITIVE FEEDBACK**

WILL NOT WORK!!!

4

A short catalog of other useful circuits:

- Non-Inverting Amplifier

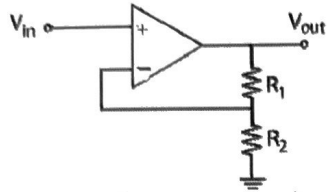


$$v_{out} = A \left(v_{in} - \frac{R_2}{R_1 + R_2} \cdot v_{out} \right)$$

let $A \rightarrow \infty$

$$v_{in} = \frac{R_2}{R_1 + R_2} \cdot v_{out} \text{ or } v_{out} = \frac{R_1 + R_2}{R_2} \cdot v_{in}$$

Can make a "variable gain" with a POT
Can limit gain with series resistors.


- Inverting Gain Block

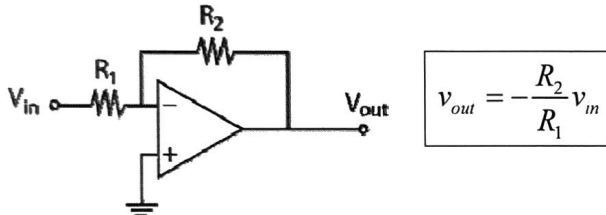

$$v_{out} = -\frac{R_2}{R_1} v_{in}$$


5

- Subtractor/ Level-Shifter

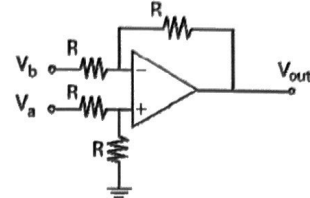


$$v_{out} = (v_a - v_b)$$

- Initial Adder

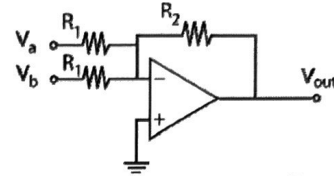

$$v_{out} = -\frac{R_2}{R_1} (v_a + v_b)$$


- Comparator (very crude ☺)

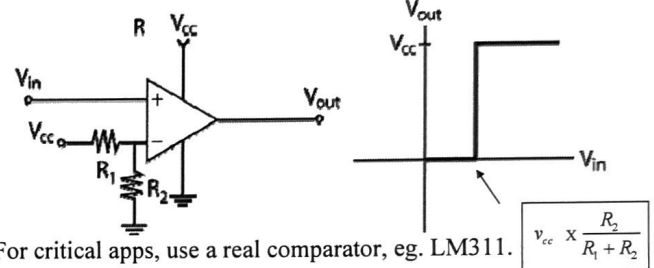

For critical apps, use a real comparator, eg. LM311.


$$v_{cc} \times \frac{R_2}{R_1 + R_2}$$

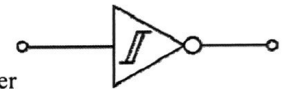- Schmitt Trigger Inverter
for cleaning up 0 – 5 V signals




6

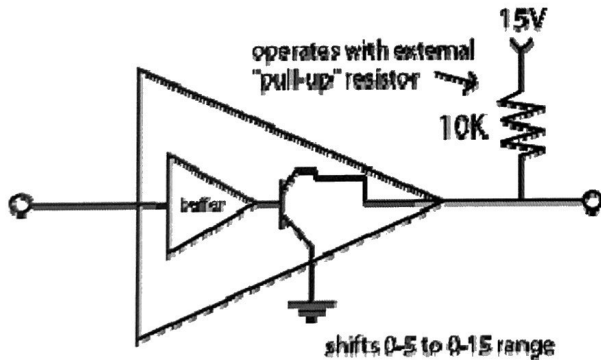- Open collector Buffer → for "level shifting" e.g. 7407:



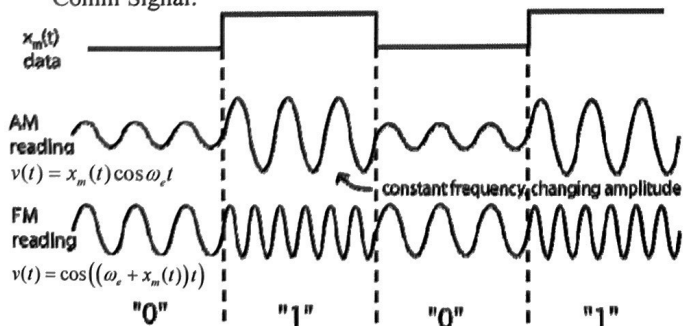
EXAMPLE → COMMUNICATION SYSTEM RECEIVER
Comm Signal:




7

How do we "decode" frequencies (in an FM input signal) to recover $x_m(t)$.

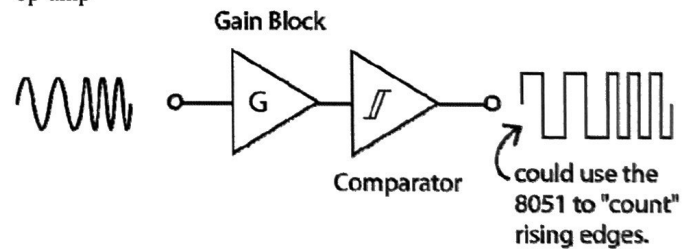FM's neat → use huge input gain and a comparator or saturating op-amp



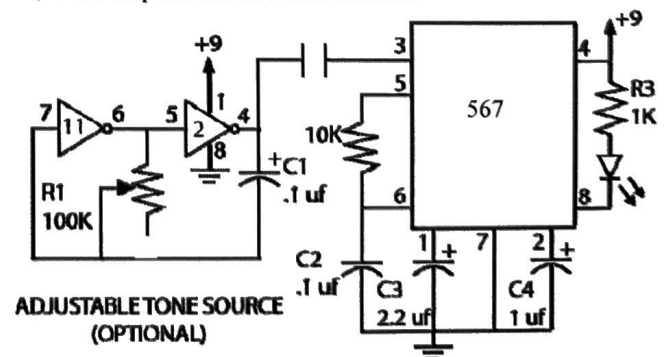Or, Use a chip like the 567 tone decoder!



8