

Regulated Power Supply: given an unregulated DC input, produce a regulated DC output voltage, e.g. 5V. Today consider two possibilities.

Linear Regulator

For sake of comparison
And analysis, let's compute
Efficiency.


(ignore i_{small})

$$P_{in} = v_{in} \cdot I$$


$$P_{out} = v_{out} \cdot I$$

$$\text{so, } \eta = \text{efficiency} = \frac{P_{out}}{P_{in}} = \frac{v_{out}}{v_{in}}$$

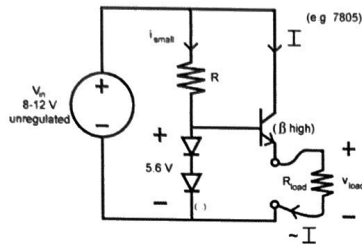
For a typical $v_{in} = 10V$, $\eta = 0.5$ (only 50% of input power goes to load)
Where does the rest of the input power go? Dissipated in the transistor as waste heat.



Switching Regulator

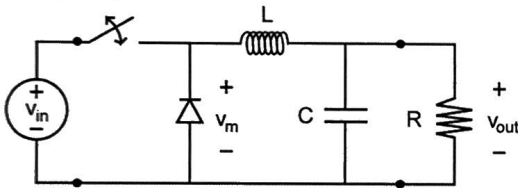

1

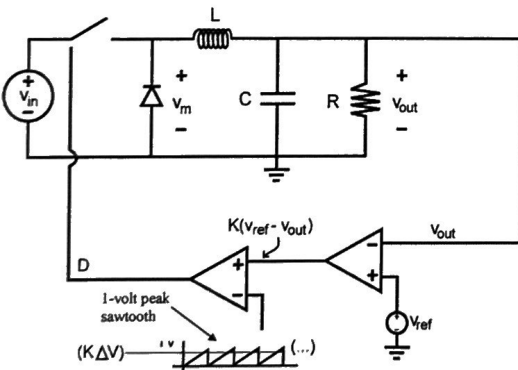

Used in many early PC power supplies!

RLC "filter": find transfer fcn $\frac{v_{out}}{v_m}(s)$


$$\frac{v_{out}}{v_m}(s) = \frac{R \parallel \frac{1}{sC}}{sL + R \parallel \frac{1}{sC}}; R \parallel \frac{1}{sC} = \frac{R}{1 + sRC} = \frac{R}{sRC + 1}$$

$$\text{so } \frac{v_{out}}{v_m}(s) = \frac{\frac{R}{sRC + 1}}{sL + \frac{R}{sRC + 1}} = \frac{R}{s^2 RLC + sL + R}$$


$$\text{or } \frac{v_{out}}{v_m}(s) = \frac{\frac{R}{sRC + 1}}{sL + \frac{R}{sRC + 1}} = \frac{\frac{1}{LC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} = P(s)$$

3

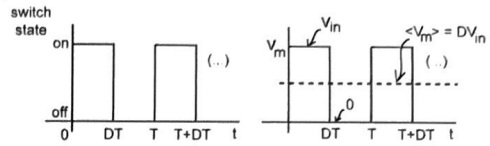
Controllable switch: operated periodically, with period T and "duty cycle" D:



NOTICE:

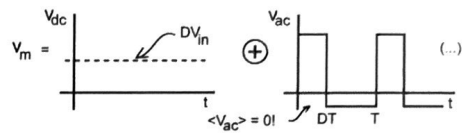


Design LCR "filter" so that

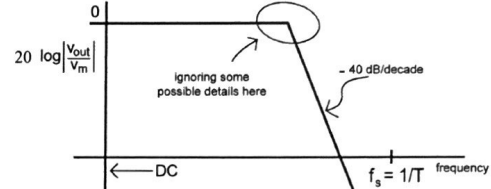

With this arrangement, v_{ac} will be severely attenuated.

$Dv_m = v_{dc}$ will pass right through.

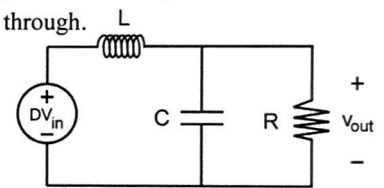
Equivalent Circuit:
(ignoring ripple due
to v_{ac})



100% efficient! All input power goes to load (for ideal L, C).

2

Block Diagram:

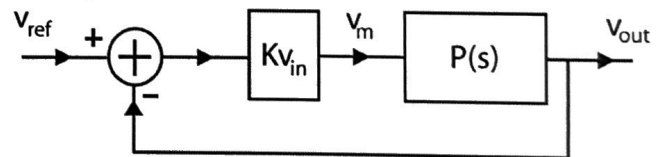

Over all transfer function (Black's formula):

$$\frac{v_{out}}{v_m}(s) = \frac{Kv_m P(s)}{1 + Kv_m P(s)} = \frac{\frac{Kv_m}{LC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

$$\text{or } \frac{v_{out}}{v_m}(s) = \frac{\frac{Kv_m}{LC}}{s^2 + \frac{s}{RC} + \left(\frac{1}{LC} + \frac{Kv_m}{LC}\right)}$$

Is it stable? Depends!

- If R is present, finite, then denominator is quadratic with all positive coefficients. STABLE
- No load, poles on $j\omega$ axis. NOT STABLE

4

With R present, how does the system perform?

Aside: What are we worried about here? ORIGINAL TTL Spec permitted $5V \pm 300mV$. So, over or undershooting the spec could cause serious problems; possibly even destroy the load!

DC, tracking performance: suppose $v_{ref} = u(t)$ (turn on). After a long time, what is v_{out} ?

Final value theorem: $h(t), t \rightarrow \infty = \lim_{s \rightarrow 0} s \cdot H(s)$

$$\text{So, } v_{out}(s) = \frac{\frac{Kv_{in}}{LC}}{s^2 + \frac{s}{RC} + \left(\frac{1}{LC} + \frac{Kv_{in}}{LC}\right)} \cdot \frac{1}{s} \cdot s_{input}$$

Limit as $s \rightarrow 0$:

$$v_{out}(s) = \frac{\frac{Kv_{in}}{LC}}{\frac{1}{LC} + \frac{Kv_{in}}{LC}} \approx 1 \quad \text{if } K \text{ is large}$$

5

So, for good steady state "tracking" performance, i.e., minimum steady state error, we would seem to want $K \rightarrow \text{large}$.


What happens to the closed loop pole (CLP) locations as K gets big?

$$P_{1,2} = -\frac{\frac{1}{RC} \pm \sqrt{\frac{1}{(RC)^2} - \frac{4(1 + Kv_{in})}{LC}}}{2}$$

As K gets huge, the term inside the square root gives us complex poles which are increasingly higher in frequency.

Real part stay fixed.

CLP locations in the s-plane:

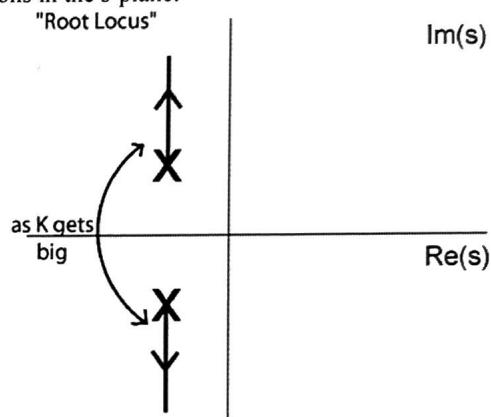

6

As K increases, decay rate remains constant, but oscillation frequency increases.

