

Laboratory Notebook

Name Simon Opsahl
Email sopsahl@mit.edu
Subject 6.115
Notebook # 1

Laboratory Notebook for 6.115: Microcontroller Project

Lab. This contains work for labs and for the final project.

Contact:

Simon Opsahl

550 Memorial Dr

(909) 645-0645

Tang 03A

sopsahl@mit.edu

Cambridge, MA 02139

Table of Contents

Exercises (cont.):

7. Build your Kovid Konsole.

8. Test your Konsole.

Exercise 1:

I started by adding minmax1 as found on the course website to my ROM. The EEPROM is the CA728C64B variety, when the switch is set to mon, we are able to communicate via TeraTerm.


I then uploaded the test program, and successfully turned on only the rightmost LED. The code is in the appendix.

The loop exists in order to keep the squirrel busy, so it doesn't start executing tasks that we don't tell it too. The PC will stay in the deterministic region.

To verify what light is in P1 MSB, I can use ~~#00h~~ or #80h instead of #01h to P1 and only the 8th bit LED from the right should light up. This worked, and the code is in the appendix.


We can use setb P1,0 instead of mov P1, #01h to set only the first bit. I expect this will accomplish the same as the test program. As expected, only the LSB LED turned on.

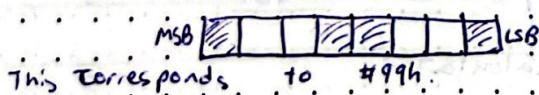To make a static pattern, I chose the pattern below.



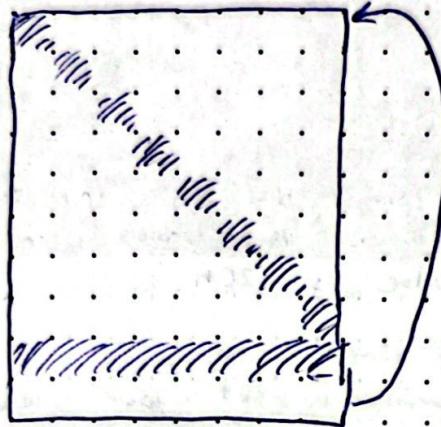Exercise 1 (cont):

We can use NOP to introduce a delay, but if we only use mov and nop, we'll have to hard code everything into the file. djnz can help loop over the nop functions so they don't have to be typed out many times. I will do a program that looks like the following.



I plan to use ~~clr~~ and ~~setb~~ for sets for the single single lights, then mov for the full and empty display. In order to make the flash last a reasonable amount of time, I will use the ~~registers~~ and djnz and do ~~nop~~ to 116 cycles.

I encountered difficulties making the timer delay long enough to visualize, but ultimately embedding two djnz loops with a counter of 255 worked.

Title	Lab 1 Report (p 4)	Date	2/20
Name		Partner	

Exercise 2:

In order to initialize the typewriter program, we need to find the register constants for 9600 baud communication.

tmod: selects the mode of the timers

- we want to use timer 1, so we will ignore bits 0-3

- we plan to use mode 2, which corresponds to ~~and an~~ an 8 bit reload with TH1 starting from the value $14h$.

TH1: Each overflow leads to an interrupt.

+ This corresponds to 10b for M1.M0.

- Finally, Gate# is low enabled, so it must be 0.

The final value is $20h$

tcon: controls the timer

- Everything will be set low except the bits pertaining to timer 1(6-7). T2I triggers the timer when set, and TFI is a flag initialized low.

The final value is $40h$

th1: stores the starting counter for TH1

- If we want a baud of 9600, we must use $3d$ as the value for th1, by the following formula:

$$\frac{11.0592 \times 10^6 \cdot 2^{15} \text{SMOD}}{12 \cdot 32 \cdot (256 - TH1)} = \text{baud rate}$$

$$(256 - TH1) = \frac{11.0592 \times 10^6 \cdot 2^0}{12 \cdot 32 \cdot 9600} = 3$$

thus, TH1 holds F0h

- Note: if we want a baud rate of 2400, we can just multiply r^2 by 4. TH1 would thus hold -12 .

scon: controls serial port behavior

- we don't need TB8 or RB8 as we only need 8 bit communication, TI and RI are involved in actual function so can be initialized low.

- we want receive enabled so we set REN. we want mode 1, so SMO, SRI, SRI² are 010

The final value is $50h$

Exercise 2 (cont.):

The typewriter program appeared to work, and I was able to display "Hello World!" in TeraTerm.

```
Welcome to 6.115!
MINMON>
*D
>.....
*Hello World!
```

Result of "Hello World!"

We could have used less program memory by not having the main body at 100h, but instead at the start of the memory. We also could just paste in the init, getch, and snd functions instead of making function calls. The current structure, however, thrives ~~exactly~~ off its modularity, as it is very easy to understand.

Exercise 3:

In order to also show the character on the LED bank, we can just move the value in the accumulator to PL when we call sndchr.

In order to create the auto-wrap, we can use djnz instead of loop with a counter of 65, and every 65th cycle do a carriage return and line feed.

I will determine the ASCII codes of each character by doing a sweep of every character on the keyboard and looking at what is shown on the LEDs. The completed table is pasted on the following page.

Exercise 3 (cont.):

	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	□	█	─	━	━	━	━	━	━	━	━	━	━	━	━	━
1	▀	○	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖	⊖
2	SP	!	”	#	%	\$	&	()	*	*	*	*	*	*	*
3	⌚	1	2	3	ψ	5	6	7	8	9	:	;	<	=	?	
4	@	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O
5	P	Q	R	S	T	U	V	X	Y	Z	[]	^	-		
6	,	α	β	γ	δ	ε	ϝ	ϛ	ϛ	ϛ	ϛ	ϛ	ϛ	ϛ	ϛ	ϛ
7	P	ρ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ	ϙ

8 9 A B C D E F

Exercise 4:

In order to make a simple calculator, several considerations must be had:

1. 3 numbers → value

We must convert the 3 integers in the 1s, 10s, and 100s place into a corresponding value in hex. To first get the hex value for the number from the dec ASCII representation, we can add d0h. Then, we can use $A \times x$, where A holds 1, 10, or 100, and x holds its factor. Finally, we can add the three results. We have our 3 digit number translated from ASCII!

2. +, -, and other

We must determine whether an input is '+', '-', or something else when the two numbers are stored. At this point, we can just compare the ASCII values, and I will arbitrarily designate the default output to be 0h. For the others, the subroutine will run, output the result on the LEPs, and restore to an initial state.


3. Restoring to an initial state

We must have all registers restore to an initial state, jump to the very start of the loop, and be ready to receive the two new numbers.

2/24/24

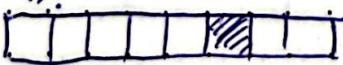Exercise 4 (cont.):

When we overflow the program, the numbers wrap around. 250 to 10 becomes 4, because 5 to become 255 (the maximum value), 1 to become 0 again, and 4 more. The result is:



Exercise 4 (cont.):

I tried a bunch of different operations, and this is what resulted:

Term 1	Term 2	Op	Output
000	001	+	001
000	001	-	255
250	010	+	004
250	010	-	240
128	127	+	255
128	127	-	001

Exercise 5:

In order to display the result, we need to convert the hex value into power of 10 ASCII representation. This can be done by first finding number of 100s, then number of 10s in the remainder, then number of ones for each digit. Finally, we subtract #0d0h to get the ASCII. I tried each of the combos above, and this is what I got:

```
Welcome to 6.115! 250
MINMON> 100
Welcome to 6.115! 150
MINMON> -D
>..... 128
>..... 127
>..... 255
000 128
000 127
001 -
001 001
000 250
001 010
255 240
250 010
004
```

Exercise 6:


I chose to go with the more physical keypad, primarily because I ~~don't care about~~ like the feel of pressing an actual button. The pinout is described below:

Pin X₈ — 1 2 3 A

B₇ — 4 5 6 B

A₆ — 7 8 9 C


85 — * 0 # 0

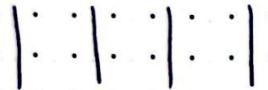

Pin A₈ Y₄ Y₃ Y₂
4 3 2 1

Notes from the 74C922 Datasheet:

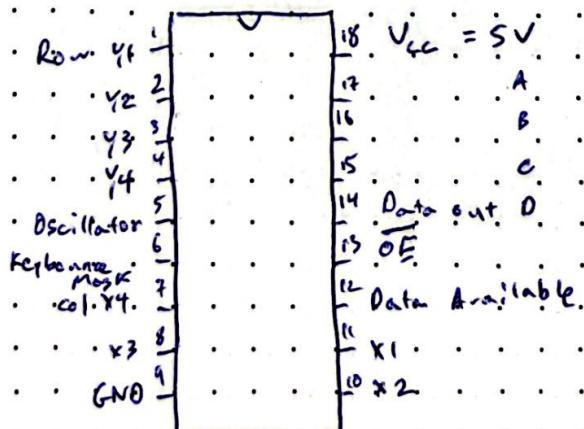
- Supports $\leq 50\text{ k}\Omega$ on resistance switches.
- Only one external capacitor is needed for debounce.
- Data available only goes high when a keyboard entry has been made.
- It takes one debounce period for DA to reset when a key is released.
- 2 key roll-over (one, then another is pressed) is supported.



Exercise 6 (cont.):

Waveforms:



Key.

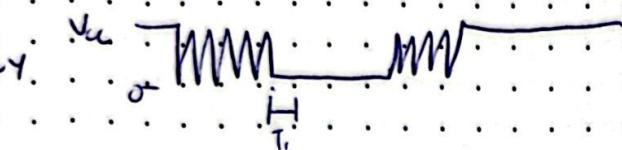

$$T_k = R C_{KBM}$$

$$R = 10k\Omega$$


$$C_{KBM} = ?$$

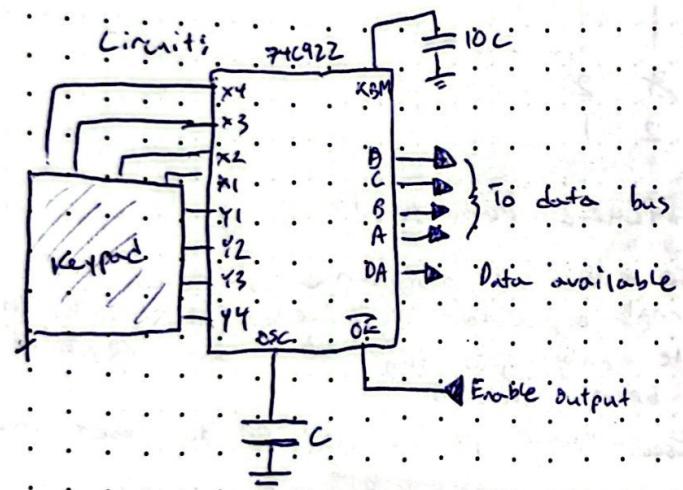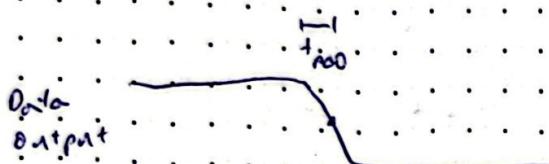

To find C , we want a capacitor that is \propto in the typical range. I looked on the graphs and decided on $0.1 \mu F$ using the $100 nF$ capacitor rated for 50V. This is for C_{KBM} : $C_{KBM} = 10 \times C_{osc}$, so I'll use the $1 \mu F$ capacitor rated for 50V.

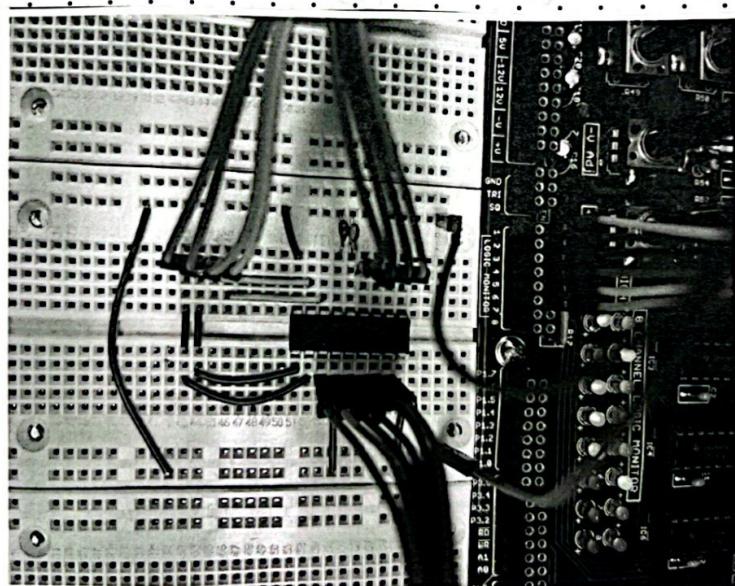Exercise 6 (cont.)

I wired up my circuit with the chosen capacitors, connected GND to GND and VCC to 5V. The other pins I connected to pins 1-6 of the logic monitor. When I connect OE to +5V, OA will switch with any button press, while no other pin switches. When I connect OE to GND, however, every time an output is held to GND, and when a button is pressed, the OA light triggers and the value is outputted and stored. The values cycle from A=On, 1=3h, ..., D=Ch, x=fh. Below is a picture of my circuit.



Exercise 6 (cont.):

I chose to connect the pins based on the following arrangement.

A	P1.3	P1.0
B	P1.2	P1.1
C	P1.1	P1.2
D	P1.0	P1.3
*		
OF	P3.3	
DA	P3.2	

I wrote code that used the value from the key, masked with 0100 1111 so that the output would be an ASCII @, A-D, the result is below.

1	2	3	A
C	B	A	C
4	5	6	B
G	F	E	O
7	8	9	C
K	J	I	H
*	N	M	L

When making the table lookup, I decided to have all non-digit characters be 0.

Exercise 6 (cont.):

When this sent to terminal, this is the result:

1	2	3	0	A
4	5	6	0	B
7	8	9	0	C
*	0	#	0	
0	0	0	0	

Now all that is left is to make the calculator. This can done using a very similar structure to the calculator from before, except that now the character is fetched by the keypad press.

Note: I plan to use A for '+' and B for '-'


I tested the same out inputs as the previous calculator, and the results all hold.

-Note: I used p3,4 to track whether or not a button press is a new one or ongoing so that the input doesn't get flooded.

Exercise 7:

I wired up the breadboard as instructed. A photo is attached below. Elements include:


- 1kΩ pull down resistors 3.0 - 3.7
- LED bank (10 lights) 15.0 - 15.1
- switch bank (6 switches) 0.0 - 0.7

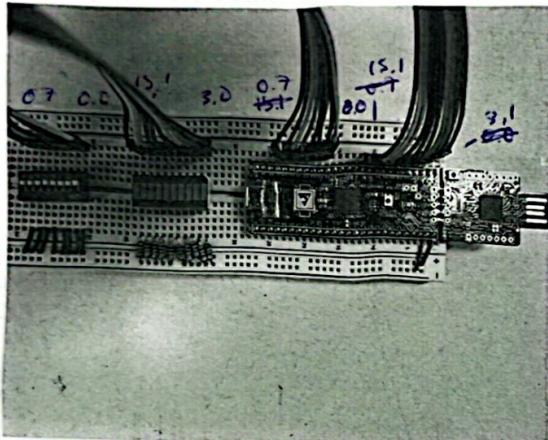


Exercise 8:

In my PSOC creator design, I made sure to specify it was building for the PSOC 5LP with chip C8C5886L71-LP097. I made the design very similar to the staff example, with a few notable exceptions.

Exercise 8 (cont.)

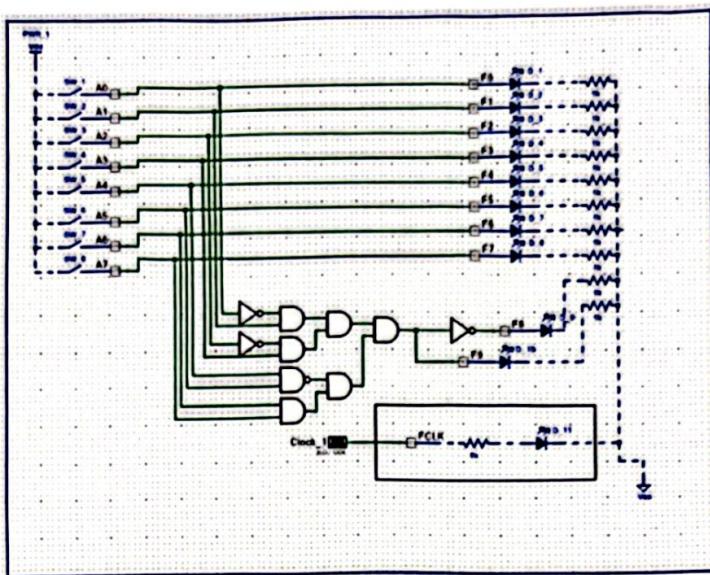

The top level diagram

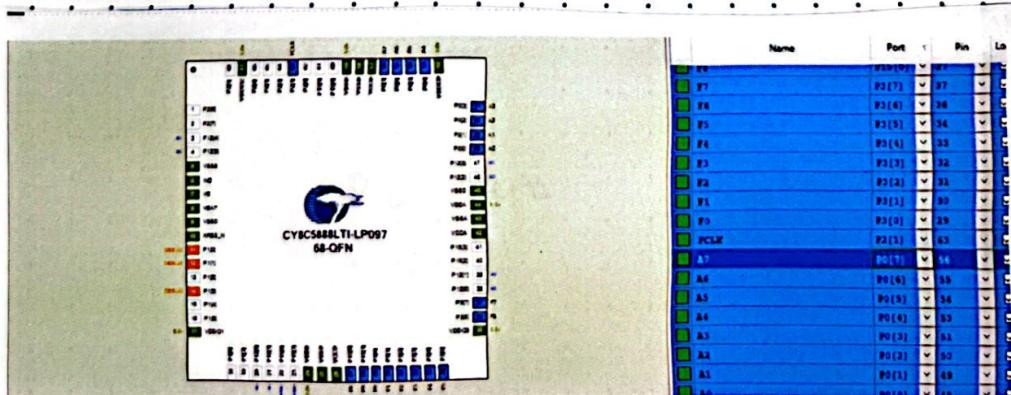

Title

Lab 1 report (p 16)

Date

Name


Partner

Exercise 8 (cont.):

I chose to have the 9th LED be a wrong, and the 10th a right for a specific combination: 01010011b., or 'S' in ASCII. That's the first letter of my name, and a difficult code to crack. I have the pictures below:


Code: 11101100

wrong

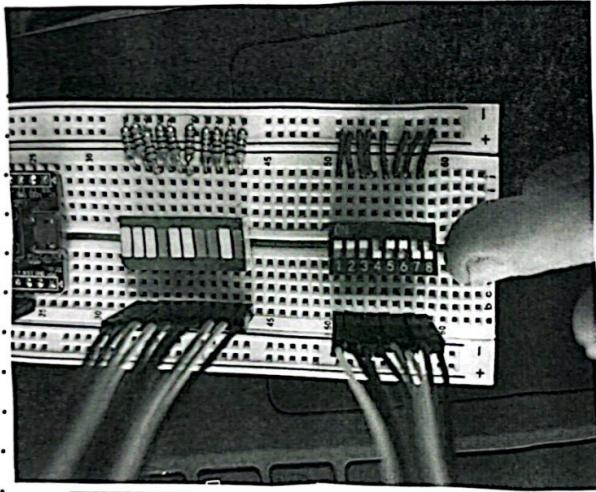

Code: 01010011

RIGHT

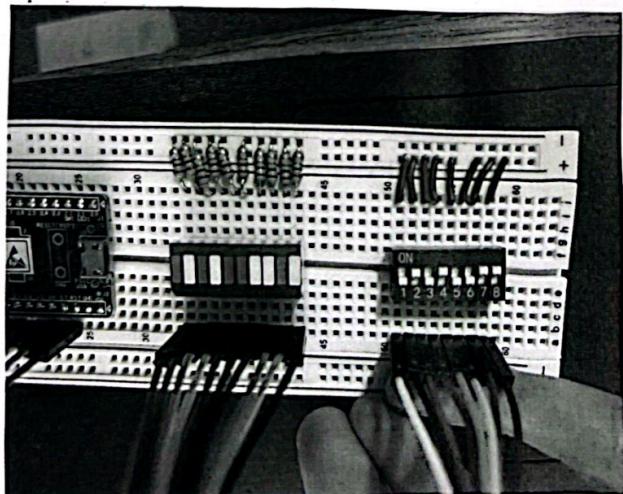

Title Lab 1 report (p 17)

Date 2-27

Name

Partner

10/10 Kl.

End

Y

Vab

Report X

6.115 Lab 2

Goals:

- Understand and modify the monitor code running on your R31JP board.
- Understand the structure of an Intel Hex file.
- Learn to use interrupts and timers.
- Connect a peripheral chip to your R31JP.
- Take control of a physical system (LED lamp) using your R31JP.
- Learn about the PSoC "Programmable System on Chip" and the C programming language.

Exercises:

- ① Expand MINMON
- ② Reverse assemble a hex file
- ③ A simple calculator
- ④ Get comfortable with the fluorescent lamp
- ⑤ Make some square waves
- ⑥ Understand the 8254 counter/timer chip

Exercises (cont.):

- ⑦ Control the lamp.
- ⑧ Understand the 8051 hardware
- ⑨ Learn about the PSoC Big Board

Exercise 1: Adding Read/Write to MINIMON

We will add read to 'R' and write to 'w'.

Read:

- We want to read the hexadecimal contents of a byte in external memory.
- We then want to display the output.

Ex: * R9000

FF

- We can use printhex, which prints the contents of A as 2 digit ASCII hex, and getbyt, which reads in a 2 digit ascii from the serial port.

- We can also use the DPLR, and DPL, its low byte, and DPH, its high byte.

- we can move and pop the values into the pointer and indirect address,

Title	Lab 2 report (p3)	Date
Name		Partner

Exercise 1 (cont.);

Write:

- Write can be implemented in a very similar way, but instead uses `movx @dptr, a`; we need to check formatting, but besides that, it should be straightforward.
- We can only write to memory locations accessible in the RAM, which is 8000-ffff, as the EEPROM is read-only.
- The result of several read/writes are below.

```
Welcome to 6.115!
MINMON>
-
Welcome to 6.115!
MINMON>
-R8000
02
-R8000
02
-R9000
ED
-08000-10
-R9000
ED
-09000-14
-R9000
14
-09000-31
-R9000
31
-R8000
02
-R8000
10
-
```

Title 6.115 lab report (p 4)

Date 2/2

Name

Partner

Exercise 2: Reverse Assembly Hex

In order to reverse assembly, we must deconstruct the inputs. The hex is in the following format:

: x x	x x x x	x x	x x	.. x x	x x
record length	address	data	type	data bytes	checksum

Record length will say the number of words in the data, and address will say the location.

Everything else is unimportant to the decoding. The data types are consistent, the checksum is just checking for corruption.

Line 1:


1 0 0 0 0 0 0 0	7 4 0 0 8 5 E 0 9 0 D 2 9 2 8 0 F
16 bytes at 00h	datatype
FF jnc. 61	dr 74 mov H, A20h xRL A, B
F 7 5 0 6 1 7 2 7 4 7 9 2 0 6 F 0 0	

Line 2:

11 bytes at 10h	data rel A, B6 jb 69 6E jb 36 2E call 31
0 B 0 0 1 0 0 0 6 E 2 0 6 9 6 E 2 0 3 6 2 E 3 1 3 1	
addr A, B6	
3 5 2 1 4 4	

Exercise 2 (cont.)

Line 3:

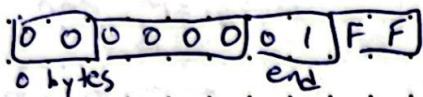

The code, thus, is as follows:

```

start: org 00h
       mov A, #00h
       mov 40h, E0h → 40h=P1
       setb 92h → 92h=P1.Z
       sjmp start

```

if C == 0 : branch
if C == 1 : proceed

$\rightarrow 61 + 2 = 63 + 9 = 6C$

```

jnc 61h
orl C, 74h → 74h=
mov R1, #20h
xrl A, R7

```

```

xrl A, R6
jb 69h, 6E
jb 36h, 2E
call, 31
addc A, #21h

```

$11 + 3 + 6E = 82h$
 $14 + 3 + 2E = 45h$
 $001 - 0011_0001 = 13h$

Although we have a number of instructions, the only important ones are at in the first block. In this, we load P1 (the LEPs) with 00h, then set P1.Z, then loop over it again, the rest of the code is not reached, and when converted to ASCII, says "Party on in 6.115!"

The code is in the Appendix, and the hex is included with it.

Title	6.115 lab report (p6)	(29)	Date	2/29
Name		Partner		

Exercise 3: A simple calculator

In order to have a program run from mon and update locations in memory with the output of arithmetic operations, we can use the dptr, and have subroutines for each of +, -, *, and / add their results and increment.

I will try two sets of numbers:

40 and 01

25ff and 254fd

	sum	diff	product	quotient	remainder
40 and 01	41	3F	0040	40	00
ff25 and 254fd	fc	02	fc03	01	02

* Note, I started the program at 8000h so it all works for the subroutines.

```


Welcome to 6.115!
MINMON> *R9000
*R9000
40
*R9000
40
*bad parameter
*R9001
01
*R9002
41
*R9003
3F
*R9004
00
*R9005
00
*R9006
40
*R9007
00
*G8000

Welcome to 6.115!
MINMON> *
* Welcome to 6.115!
MINMON> *
* Welcome to 6.115!
MINMON> *R9000
FF
*R9001
FD
*R9002
FC
*R9003
02
*R9004
03
*R9005
FC
*R9006
01
*R9007
02
*G8000

```

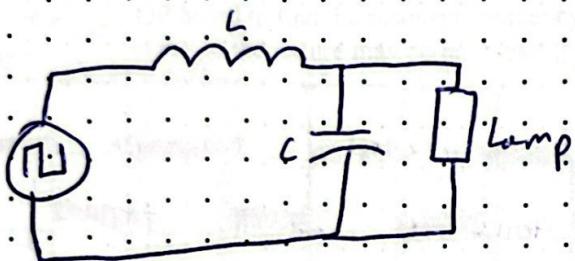
Exercise 4: Understanding the Lamp

When working with a fluorescent lamp, our strike voltage is 200 V, and after, we have a negative V : relation in the range $\approx 100-500$ mA. In order to strike and maintain low current, we need the following circuit:




We plan to tune the circuit assuming L and C are poorly controlled.

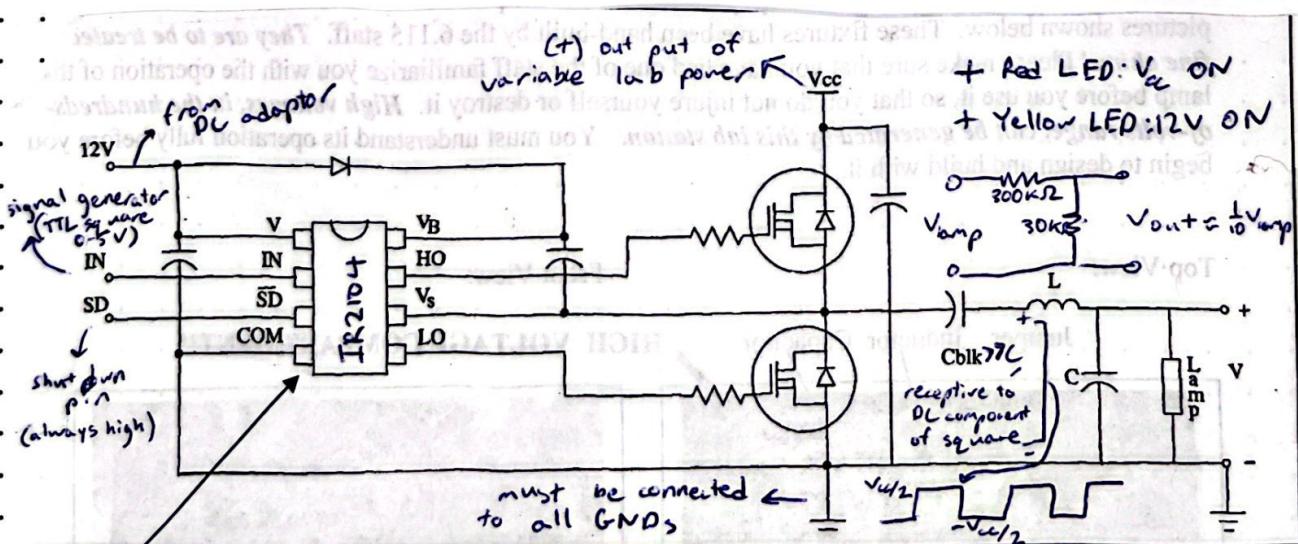Our lamp ballast is wired up the following way:




Exercise 4 (cont.)

The timing is like below:

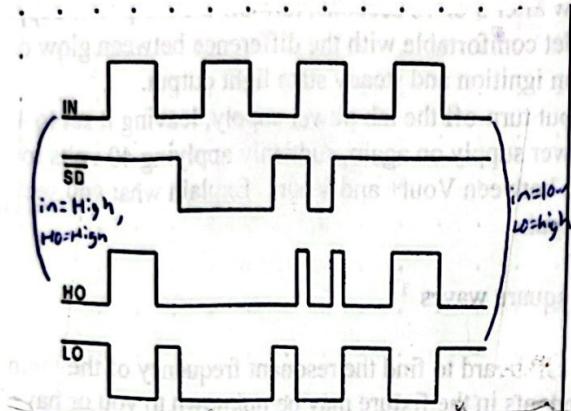


To set up, I connected the BK precision 5 MHz function generator to it. I used the TTL square wave source, when connected to the probe, the plot at 54 kHz looks like the following.

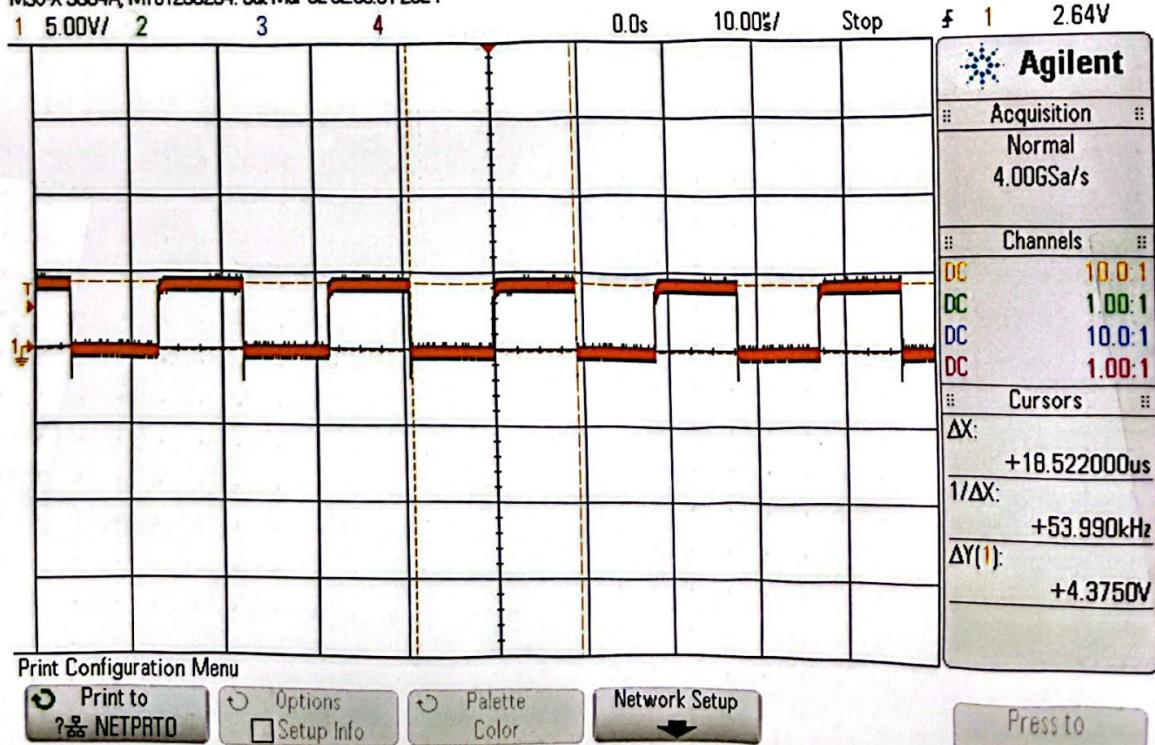MSO-X 3054A, MY51290234, Sat Mar 02 02:59:31 2024



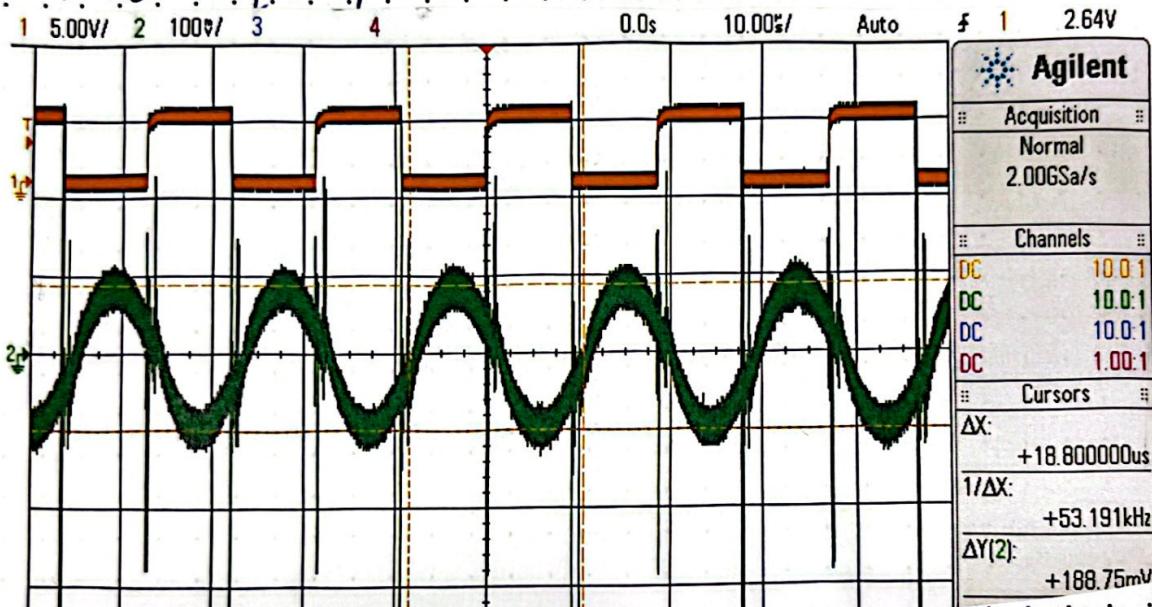Exercise 4 (cont.):

I set the signal generator at 60 kHz, then put the lab supply at 3.0 V when we see the output, we have a sinusoid with an inverse waveform, the peak of the sinusoid corresponds to the TTL low. At 3 V, 54 kHz, the amplitude is ~ 94 mV. The frequency is ~ 54 kHz.



As we decrease the frequency, the period increases and so does the amplitude. The phase also shifts so that the peak of V_{out} is at the end of the square HIGH; the maximum amplitude is ~ 9.73 (p+p) or ~ 34 kHz. The plot is on the previous page. This maximum is at $f = \frac{1}{2\pi R}$. If we


Title G.115 lab report (p 10)

Date

Name


Partner

Exercise 4 (cont.):

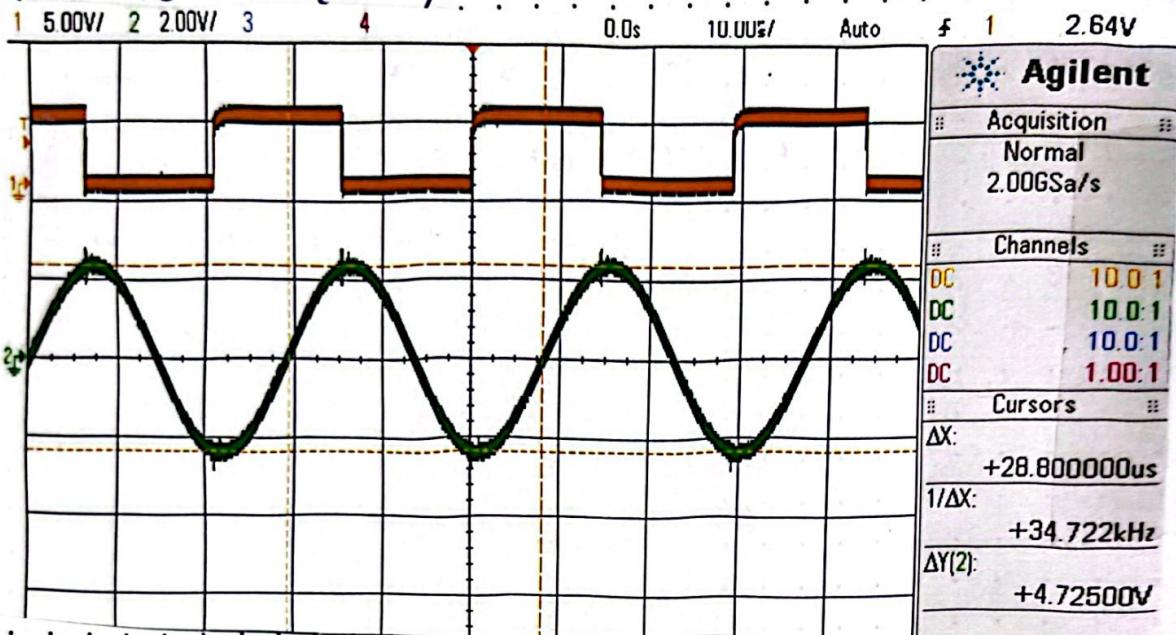


If we bring the frequency down to 15 kHz, the sinusoid starts to separate into a half-period wave

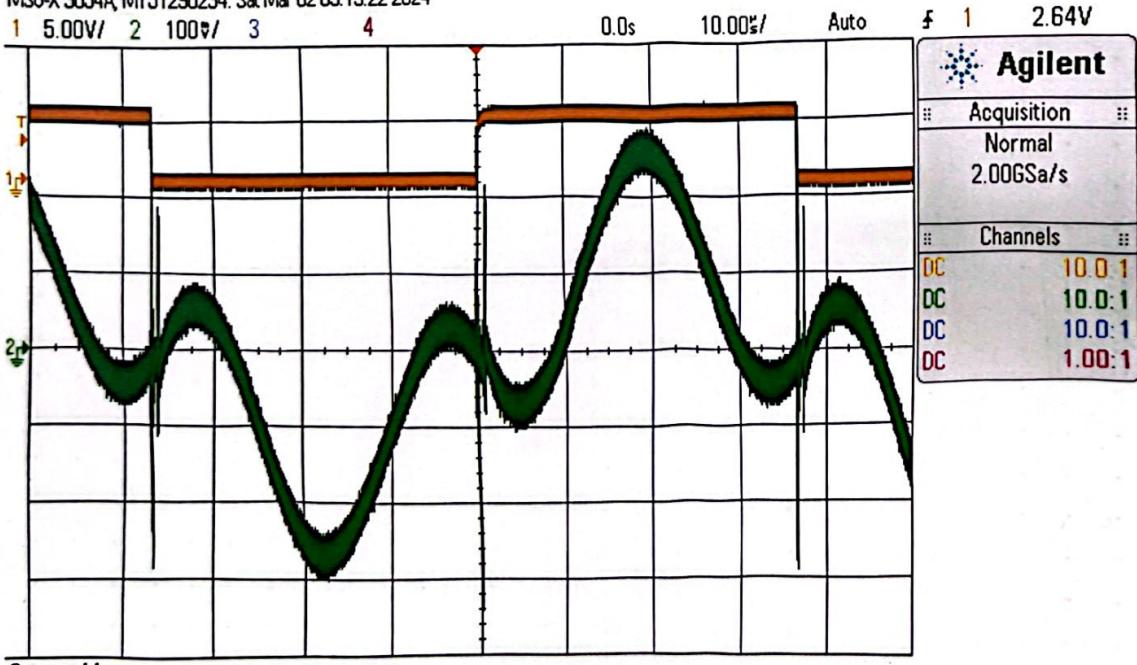MSO-X 3054A, MY51290234 Sat Mar 02 03:19:22 2024



Cursors Menu

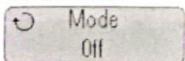


To turn on cursors, press the [Cursors] key on the front panel.

Exercise 4 (cont.):

so I will use 34.5 kHz as the resonant frequency. The lamp light struck once I had crossed the 20 V threshold. It flickered, then started glowing. The power supply maxed out at ~30 V, so I kept it here.

When I turned on the bulb, we see a small glow; when observing the phasor plot of $V_{out}-V_{in}$, we see an initial spike in the sinusoid, then a restoration to around 80 V on $V_{out}-V_{in}$, which corresponds to about 80 V across the bulb, a typical operating equilibrium voltage.

MSO-X 3054A, MY51290234, Sat Mar 02 03:27:26 2024

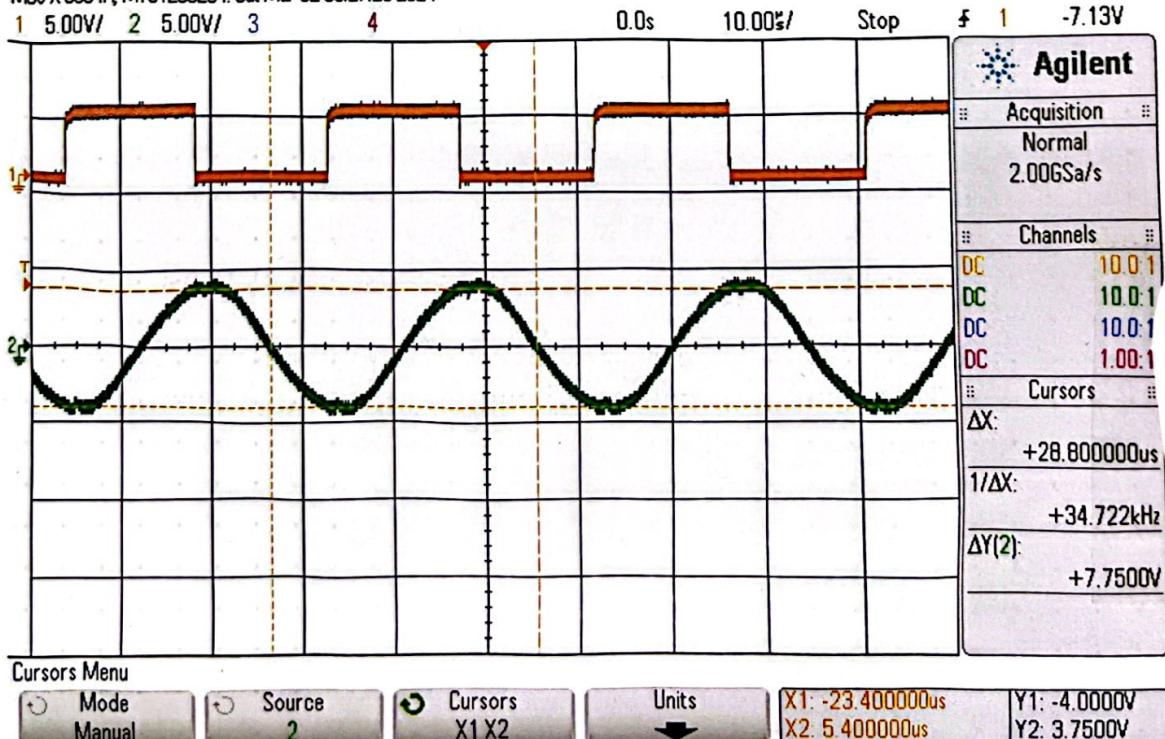

Exercise 5:

In order I will make the offset accessible from ~~1000~~
~~address~~ in the RAM (set by ~~W9000h = ?~~), it can be.
The code will follow as:

main:

movx a, dptr @100h

movx

loop:

djnz ~~RO~~, loop

cpl p1.0

sjmp main

mov a, R0 ; R0 holds the

mov R0, ~~xx~~; ~~xx~~ holds the
xx, R0 from 100h

1 cycle

2 cycles

2 cycles

2 cycles

The total cycles are $2(53 + 2 \cdot (R0))$. Each takes 12 clock cycles, and the clock is 11.0592 MHz. Thus, over range is

$$\frac{11.0592 \text{ MHz}}{12 \cdot 6 \cdot 2} \geq f \geq \frac{11.0592 \text{ MHz}}{12 \cdot 256 \cdot 2 \cdot (256 \cdot 2 \cdot 5) \cdot 2}$$

$$\frac{131.657 \text{ kHz}}{62.83 \text{ kHz}} \geq f \geq \frac{131.657 \text{ kHz}}{76.8 \text{ kHz}}$$

At around 34 kHz, the resolution is

$$\frac{11.0592 \text{ MHz}}{12 \cdot 2 \cdot (256 \cdot 2 \cdot 5) \cdot 2} = 34 \text{ kHz}$$

$$x = 4$$

Exercise 5 (cont.);

At $x=5$, $x=3$ $x=5:$

$$f = \frac{11.0592 \text{ MHz}}{12 \cdot 2(2+5)} = 30.72 \text{ kHz}$$


 $x=3:$

$$f = 41.9 \text{ kHz}$$

The resolution is around 5 kHz in the region we want it to be, which is not ideal resolution for fine tuning.

The plots of $\omega_{9000} = 0$ and 00 are below.

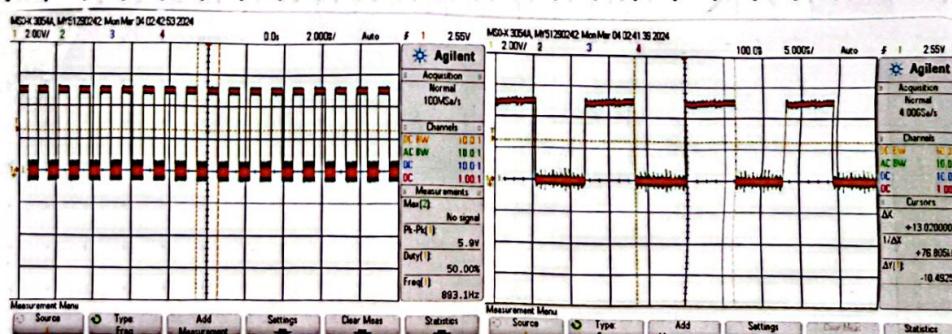The actual range appears to be 76.8 kHz to 893.1 Hz.



Exercise 5 (cont):

We want higher resolution in the 34 kHz range, which means we want it in the center of our range. We can use the timer in mode 1 for a 16 bit counter and check if TFO is set. We also need to disable interrupts, possible if we clear it at the beginning. (It defaults to 7m.

We can do this as

```

cycles over main
2 [    mov TLO, R0 ) Have low and high values
      mov THO, R1 from the data
      clr cc set TRO
      loop:
2-*     jnb TFO, loop
      1     clr TFO TRO
      2     cpl P1.0
      2     sjmp main

```


$$\text{cycles} = 10 + 2(\cancel{x})(\cancel{10000} - x)$$

$$\text{max: } x = \text{FFFFh}$$

$$f = \frac{11.0592 \text{ MHz}}{12 \cdot 2(10 + 2(1))} = 38.4 \text{ kHz}$$

$$\text{min: } x = 0h$$
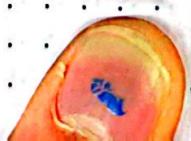
$$f = \frac{11.0592 \text{ MHz}}{12 \cdot 2(10 + 2(0ab))} = 56 \text{ Hz}$$




Exercise 5 (cont.):

$$f = 34 \text{ kHz} = \frac{11.0592 \text{ MHz}}{12.2(10 + 2(10000\text{Hz}))}$$

$$x = FFFFh$$

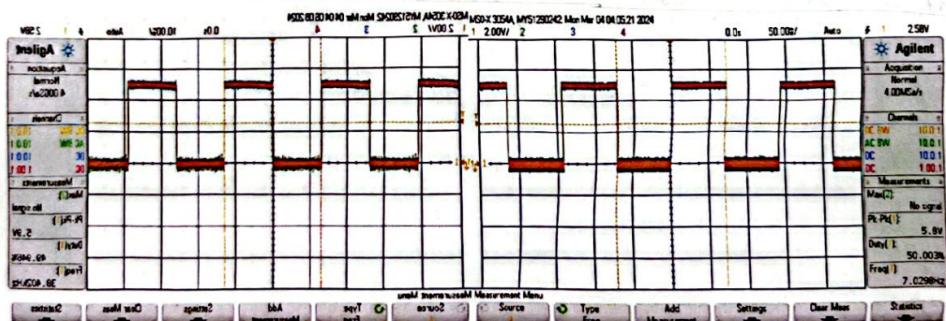The resolution barely improves to around 4 kHz in our desired region, we need something better. The plots are below, showing a max of ~~4.4~~
38.4 kHz at FFFFh and a minimum of 7 kHz at 0000h.



Exercise 5 (cont'd):

For the auto reload, we can use the interrupt handling to toggle P1.0, but in all other cases, just need to be in a do nothing loop. We need CS to be set and TFO to be set for timer 0 overflow. We also want falling edge control, so we'll use 1 for IRO.

In total:

$$IE = 10000010$$

$$TCON = 00010001$$

$$TMOD = 00000010$$

$$TH0 = x$$

we handle the interrupt at 0084. The resulting range is 1.8 kHz for $x=00h$, and 65.83 kHz for $x=ffh$. 34 kHz is in the center of this range, which is ideal.

The range around 34 kHz (F2, F3) goes from 32.9 kHz to 35.45 kHz, a resolution of 1.25 kHz, which is much, much better.

JIO

Exercise 5 (cont.):

The timing comes from:

interrupt $\xrightarrow{\text{jmp}}$ cpl P1,0 2 cycles
 2 cycles
 ret ;



As a result, the total time is

$$\frac{11.0592 \text{ MHz}}{12 - 2(\frac{1}{1000000} \times \frac{1}{1000}))} \Rightarrow 1.79 \text{ KHz} \Rightarrow 65.83 \text{ kHz}$$

The reason the third option is so much better is because the delay from overflow to restart is none due to the autoreload. Thus, the only kinks in the time are the interrupt handling, which are much less than the other routines.



The plots are on the following page for the third controllable frequency.

Exercise 5 (cont.) :

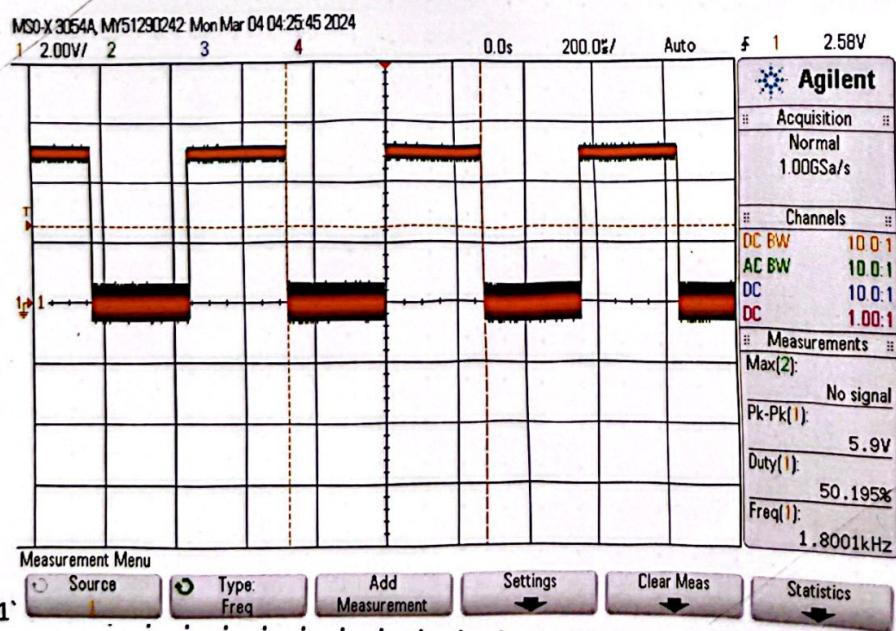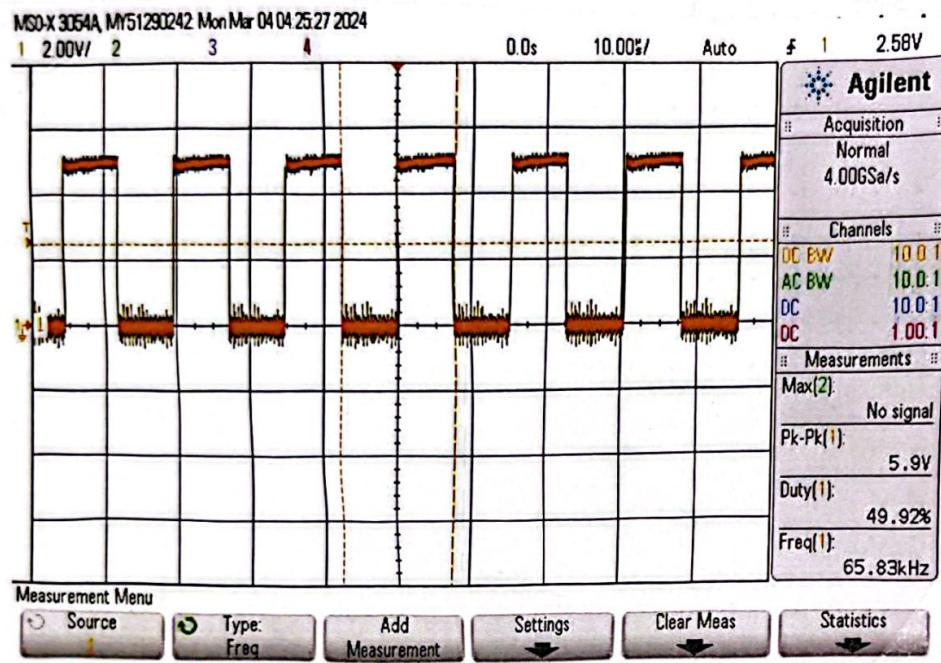

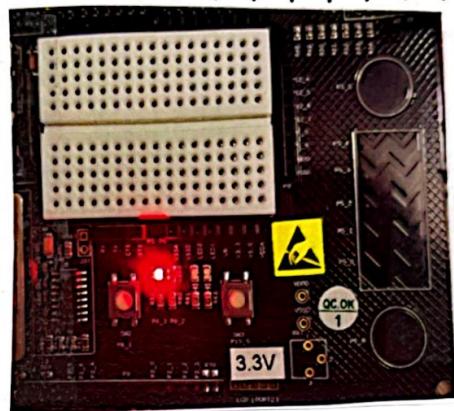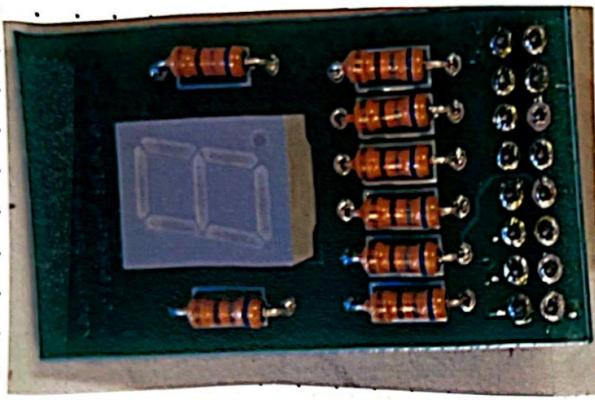Exercise 9: PSoC Big Board

I went to a solder clinic on 2/29, and a picture of my result is below.



When the project is built and flashed, it displays "6.115 IS COOL" on the led display.


In working with Exercise 1, I created a digital output pin w/ no external or hw connection. It is set to P6.3, or LED4 on the Dev Board. When built and programmed, we get a red flashing LED4.

To make a flashing SOS signal, we need to add code to the main.c file using CyDelay(), which specifies a number of milliseconds to wait. The led on photo is above.

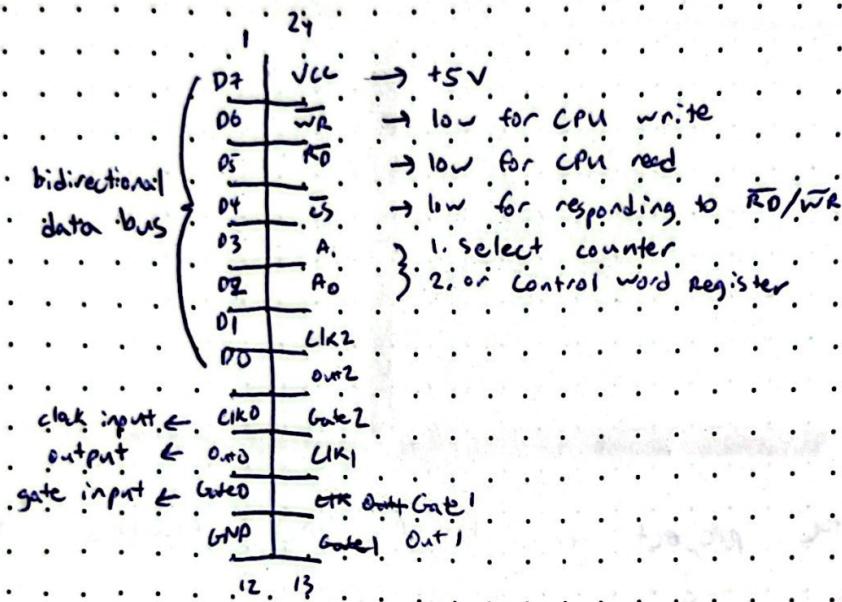Exercise 6: The 8254 Timer

Notes:

- Contains bank of 3 timers, 16 bit, up to 10 MHz.



- Control word Register ($A=111$) stores operation of counters

- Any read measures the contents of a latch downstream of the counting element.

- Any write puts the value into the upstream count registers.

- To use, you write a control word then add a count

- CW format:

0	7	6	5	4	3	2	1	0
Sel	Sec	Rw1	Rw0	M2	M1	M0	Ben	
select counter								
read back								

what do we write

note

Binary Coded Decimal

00 counter latch
01 LSB
10 msb
11 lsb + msb

Exercise 6 (cont.):

- The control word must be written before initial count.
- A counter latch latches the count when the command is received, but doesn't disrupt the CE.
- Read back can be used to latch on a count or status of multiple counters.

CW: 1, 1, $\overline{CT\ status}$, CNT2, CNT1, CNT0, 0

- Status reads can show output:

Output, N11, R11, R10, M2, M1, M0, BCD

- Modes:

0: Interrupt on count running out

1: One shot

2: Divide by N counter

3: Square wave

- Mode 3:

+ Out is initially high when half of count expires out goes low. Initial count of N is N period wave

+ Gate=1 enables counting, used to synchronize the counter.

+ Gate is sampled on the rising edge.

Setting up in 8254:

1. Connect DO-D7, RD, WE, A0, A1, Vcc, and GND to their appropriate spots.

2. GND Gate & CLK for counters 1 & 2.

3. Connect DO CS to $\overline{DSE_1}$ or ie $\overline{X0_SELECT}$ line.

Exercise 6 (cont.):

4. Connect Gated to +5V, connect 10 MHz clock to QKO.

5. Use Mode 3 for ~~clock 0~~ counter 0

$$\underbrace{0}_{\text{control}} \underbrace{0}_{\text{LSB mode}} \underbrace{1}_{+} \underbrace{1}_{\text{MSB}} \underbrace{0}_{3} = 36\text{h}$$

6. For FEO0-FE0Fh, ~~the~~ ~~xi0sElect~~ is active, we must look at A0, A1

- All addresses with A1A0=11 write to the control register (64 addresses).


FE00h (04,...) = Counter 0

FE01h (05,...) = " 1

FE02h (06,...) = " 2

FE03h (07h,...) = Control Word

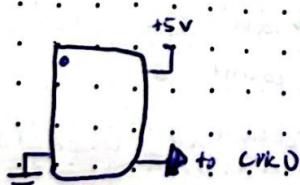
For the 10 MHz clock, we have the pin out




Note: If we had a 1 MHz crystal instead, it would have a lower possible output freq, but the max and resolution would be worse. It would have lower Δf , however.

I used WFE03 = 36h and 0126 h to provide the values for 34 kHz. The wiring and plots are shown to the right.




Exercise A.6 (cont.):

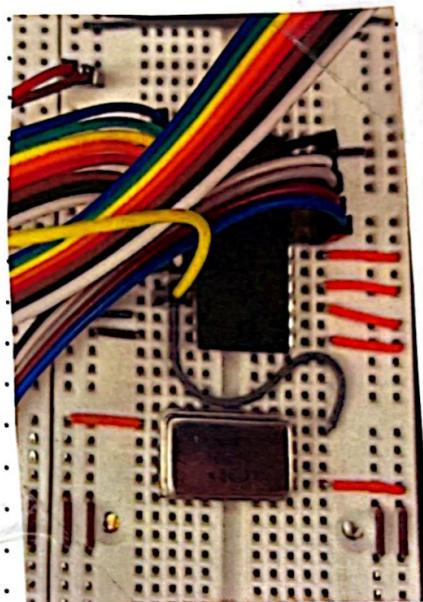

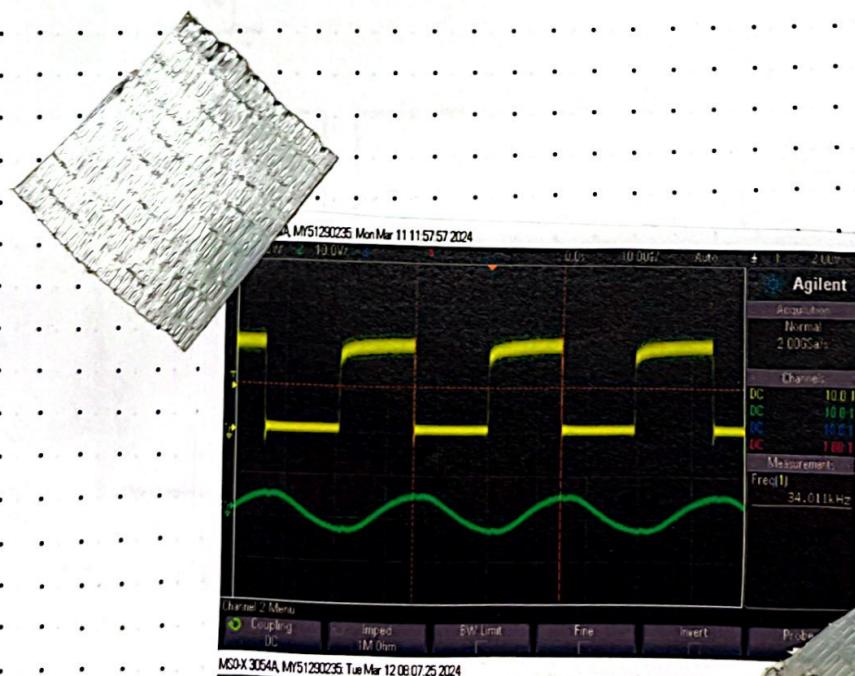
The circuit of the
8254 and
10 MHz crystal



square wave
generated
w/ 0.125 h

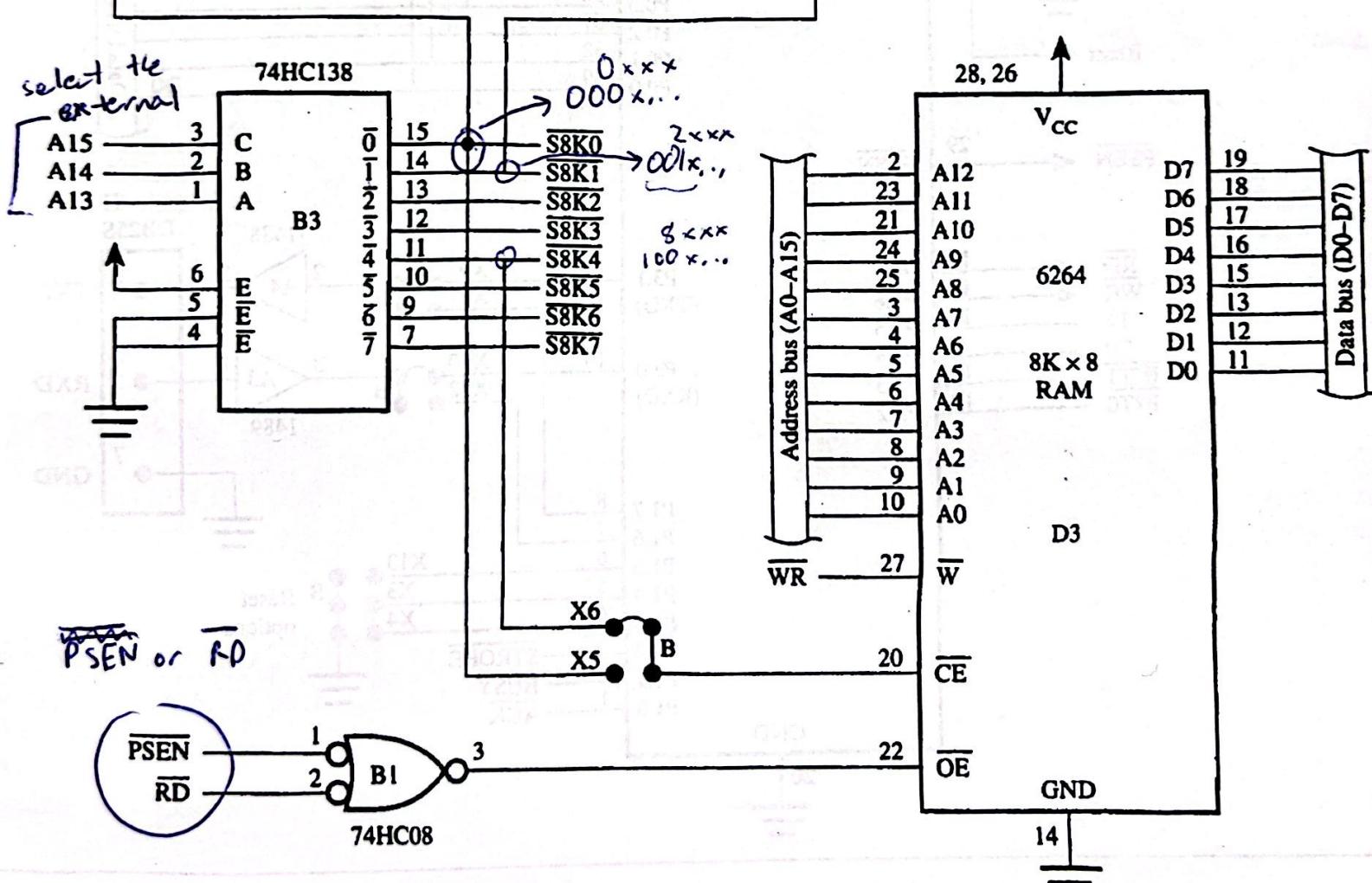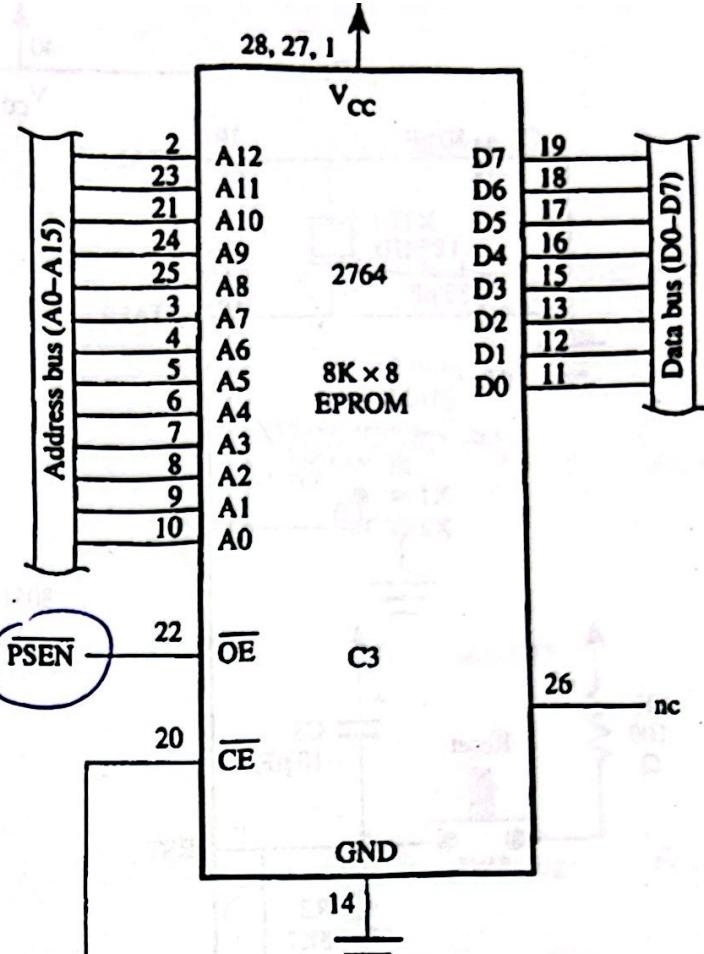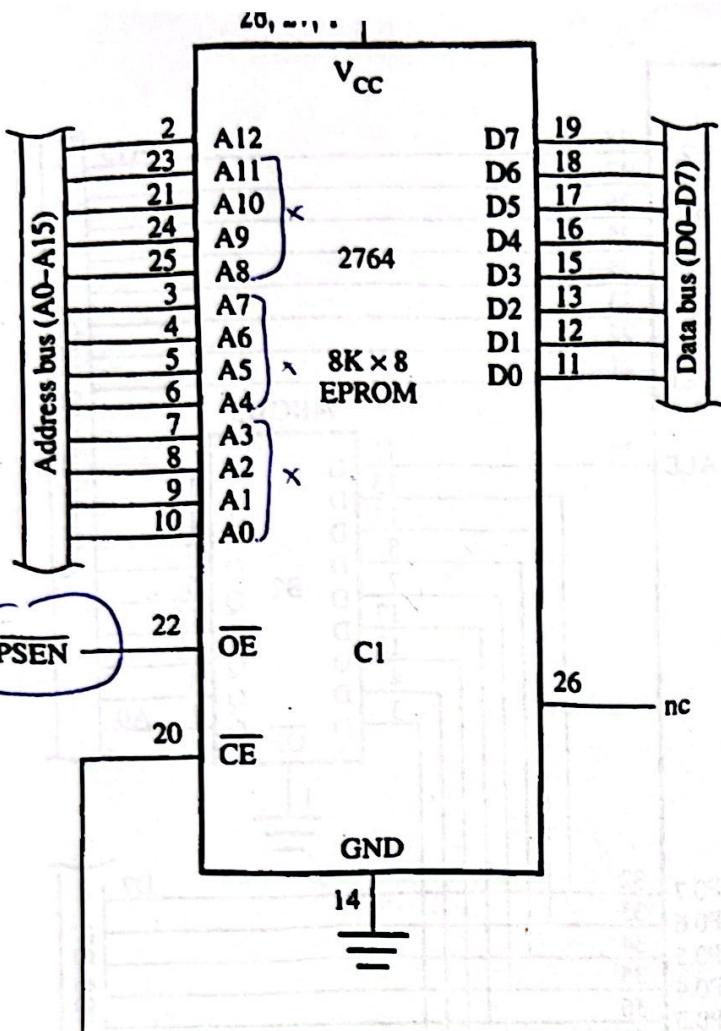

Exercise 8: Understand the 8051

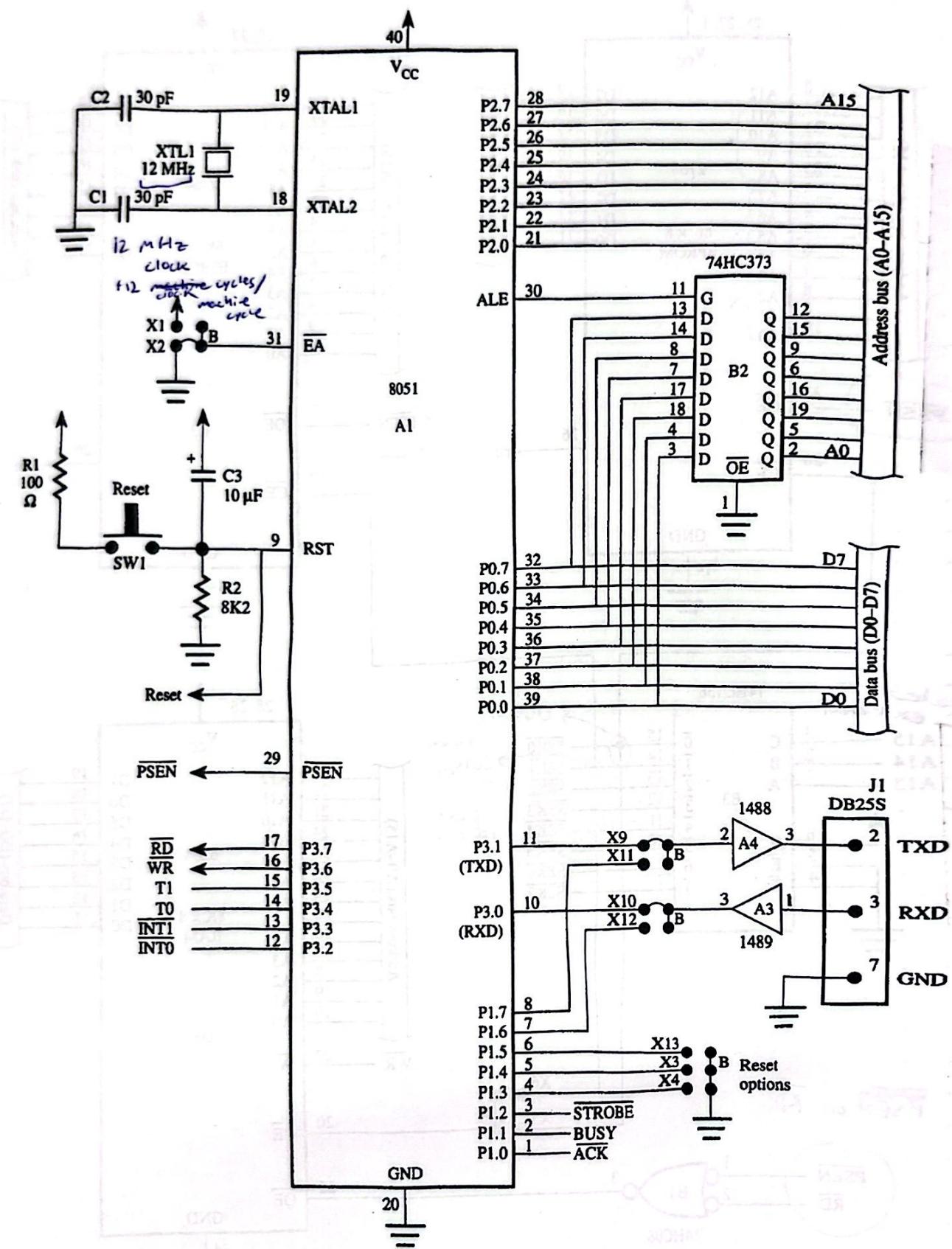


Exercise Exercise 8 (cont.)

Single Board Computer:

- 1) 1 ms machine cycle.
- 2) C1 could contain memory address stored at 0x00h and is ROM.
- 3) After power-on reset, the routine could fetch code from internal ROM or C1.
- 4) G800 would jump to D3, the RAM.
- 5) G200 would jump to C3.
- 6) Because movx sends a low pulse for PSEN, any of C1, C3, or D3 could read by movx.
- 7) Because movx doesn't send the low pulse, only D3 (RAM) can be read.


Exercise 7: Control the lamp

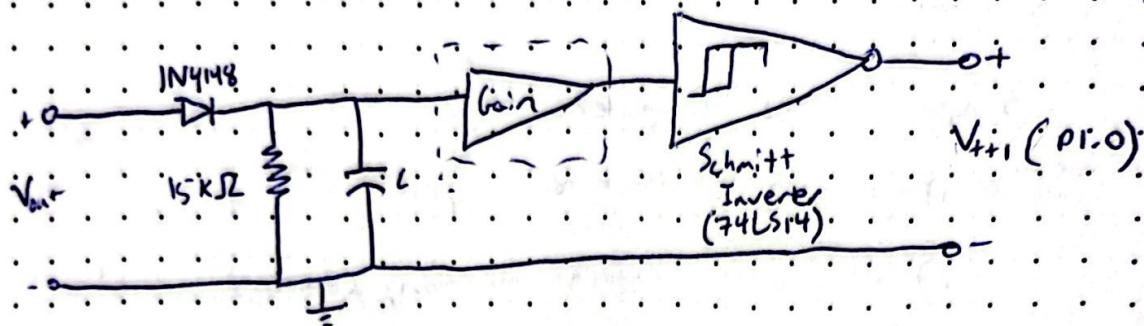


$$RL = 1.15 \text{ mS} \Rightarrow 10 \text{ ms}$$

$$L = \frac{10 \cdot 10^{-3} \text{ s}}{15 \cdot 10^3 \text{ } \Omega} = 0.667 \times 10^{-6} \text{ F} = 0.67 \mu\text{F}$$


Gain Block:

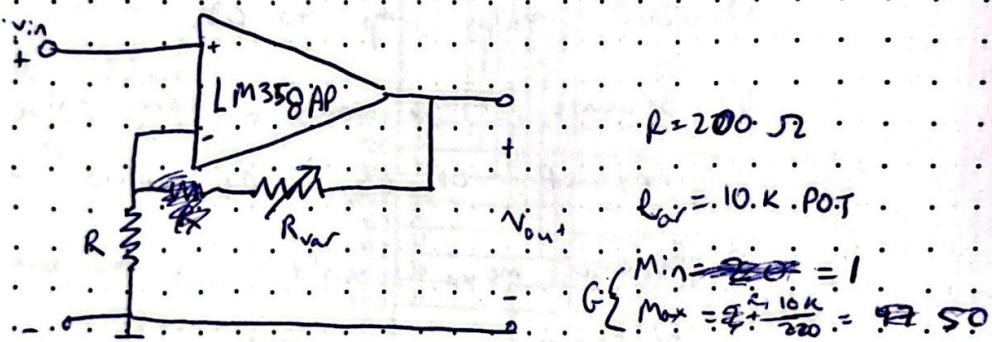

LM358AP:

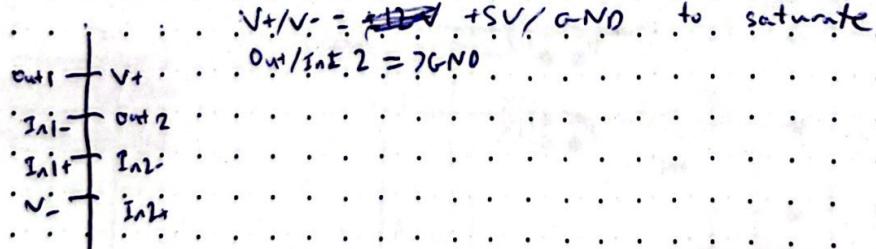


Schmitt Inverter:

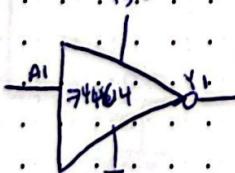

A1	V _{CC}
A2	A ₆
Y ₁	Y ₆
A ₃	A ₅
Y ₂	Y ₅
A ₄	Y ₄
Y ₃	A ₄
GND	Y ₄

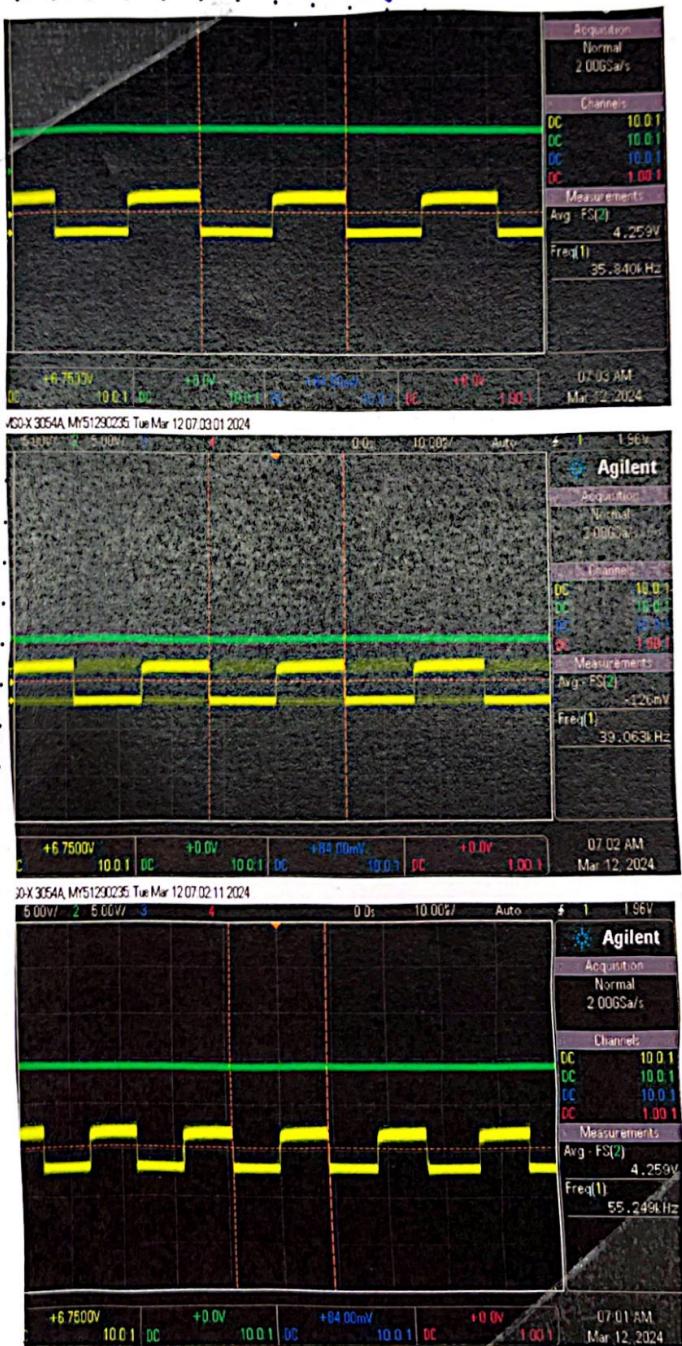
Exercise 7 (cont.);

I was able to establish a threshold where the Schmitt output is high when out of range, low when close, and high again when triggered. The plots and circuit are shown below.



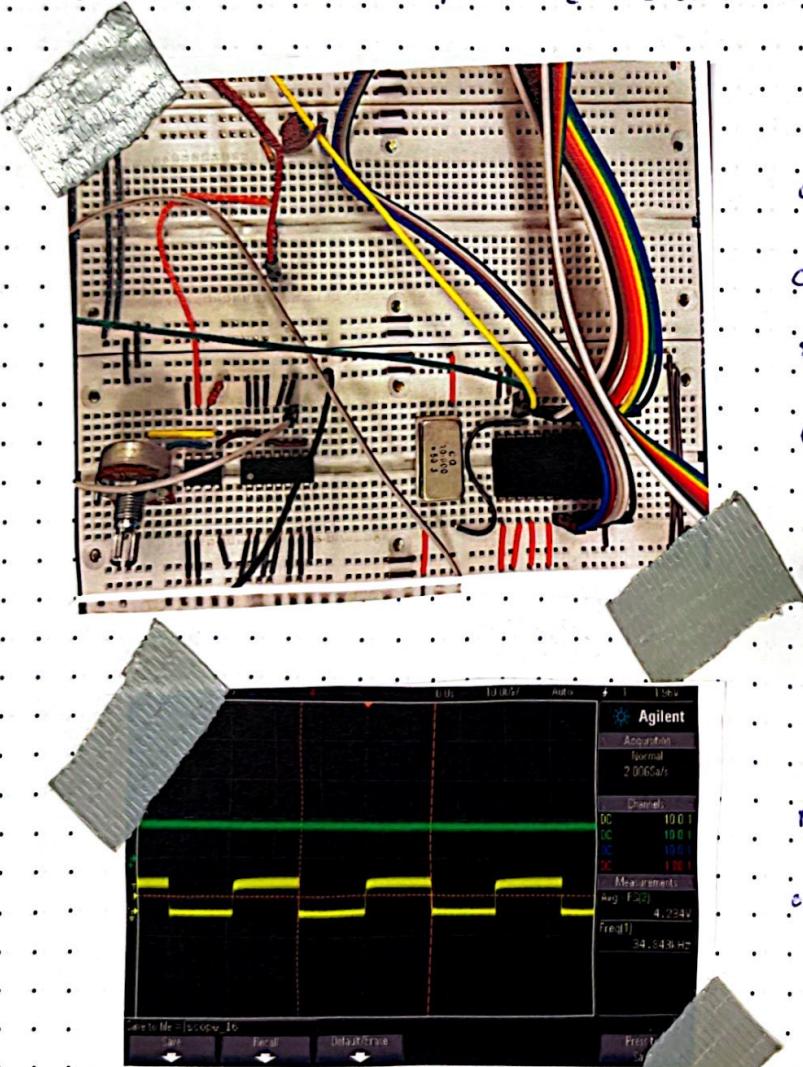Exercise 7 (cont.):

When striking the lamp, I decided to step down in frequency in large steps ($\frac{1}{10}$) at first, then decrease to 1 when close (Schmitt low), and 0 when struck (schmitt high again). This can be done by using a timer delay. I used a 16-bit timer with 5000h load. This allows the real time system to not fall behind the machine. The final plot and circuit are shown below.



complete Lab
circuit w/
8254 timer and
feedback circuit

Driven frequency
once striked

End

of

Z

Vd

Rec or

Dinner (Omkar)

3.12.24

Title Lab 3 Report (p1)

Date 3/16

Name Simon Opsahl

Partner

Exer Lab 3 Report

Goals:

- Further understand and modify the monitor code
- Finish getting familiar with 8051 assembly.
- Connect multiple peripherals to the R31JP.
- Make a collection of digital waveform synthesizers
- Explore the PSoC!

Exercises:

- ① Modify MinMon
- ② Analog output from digital squirrel
- ③ Make a sine wave generator
- ④ Add some more useful peripherals
- ⑤ Lissajous curves
- ⑥ Secrets of the squirrel

Exercise 1: Modify MINMON

In this exercise, we use "V" to enter a vector of bytes to create waveforms. I want to automatically print the dptr each time, then enter will escape the entry. Entering 256 bytes also escapes the entry. The result is below:

```
*U90  
9000=00  
9001=01  
9002=02  
9003=  
*R9000  
EF  
*R9001  
BD  
*R9003  
EE  
*R9002  
02  
*  
*U90  
9000=00  
9001=01  
9002=02  
9003=  
*R9000  
00  
*R9001  
01  
*R9002  
02  
*
```

Exercise 2: Analog Output


We must overcome the sharing of D0-D7 to add another IC to our R31JP. We will be adding the AD558 (SN 90609 397413), an 8 bit DAC.

Notes:

- Operates on a single +5 - +15 V supply.
- Has ± 1 LSB resolution.
- The S is for use in 0-70°C.
- The output range is 0-2.56 V

Exercise 2 (cont.):

The pinout of the AD558 is as follows:

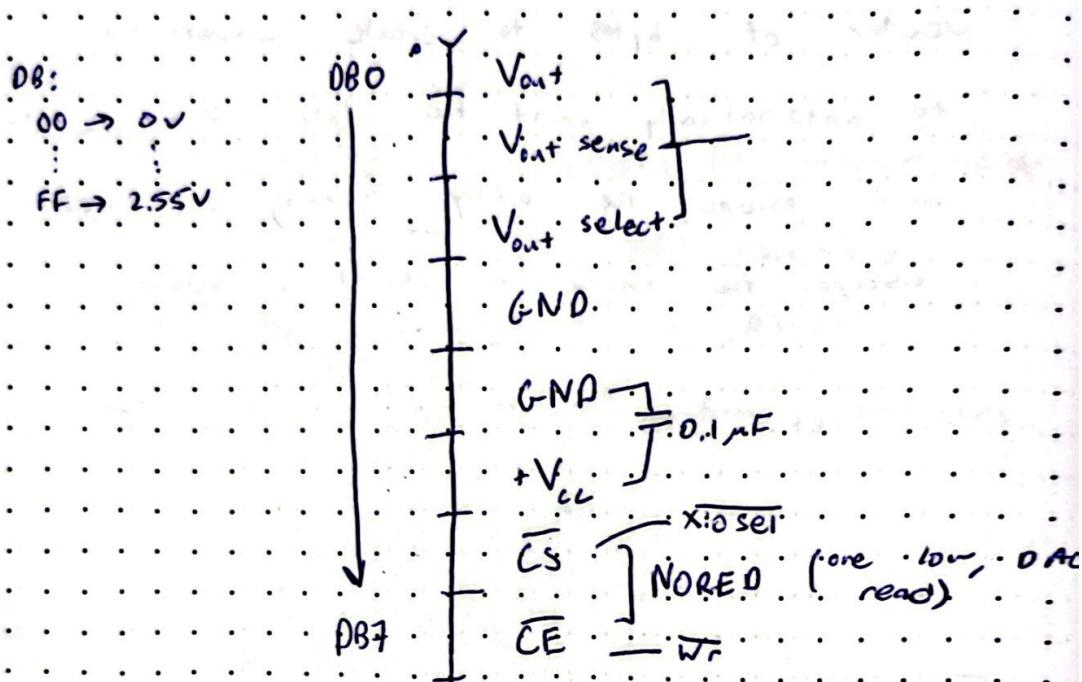

We must connect the V_{out}'s for the 0-2.55 V and add a bypassing capacitor of 0.1 μ F.

To allow for multiple I/Os, we need a demultiplexer to control the CS line.

DM74LS138N:

- 3 select inputs \rightarrow 8 lines

- 3 enable pins:

$G_1 \rightarrow H$ enables an output

$G_2(A; 0) \rightarrow L$ enables a low-active output

Exercise 2 (cont.)

The pinout is as below:


select {	A	V _{cc}
	B	Y ₀
	C	Y ₁
	G _{2A}	Y ₂
	G _{2B}	Y ₃
	G ₁	Y ₄
	Y ₇	Y ₅
	GND	Y ₆

We need G_{2A} and G_{2B} to be low and G₁ to be high to enable the chip. This can be done by tying G₁ to +5V and G_{2A}; B to ~~XIOSELECT~~.


For the select pins, we want each to be addressable by while leaving open the first 3 addresses. Thus, A₈, A₉, and A₁₀ will be A, B, and C select pins.

	Addresses	Device
Y ₀	F _e 00 - F _e ff	8254
Y ₁	F _e 00 - F _e ff if	A0558
Y ₂	F _e 20 - F _e 7f 2f	-
Y ₃	F _e 30 - F _e ff 3f	-
Y ₄	F _e 40 - F _e ff 4f	-
Y ₅	F _e 50 - F _e ff 5f	-
Y ₆	F _e 60 - F _e ff 6f	-
Y ₇	F _e 70 - F _e ff 7f	-


Exercise 2 (cont.):

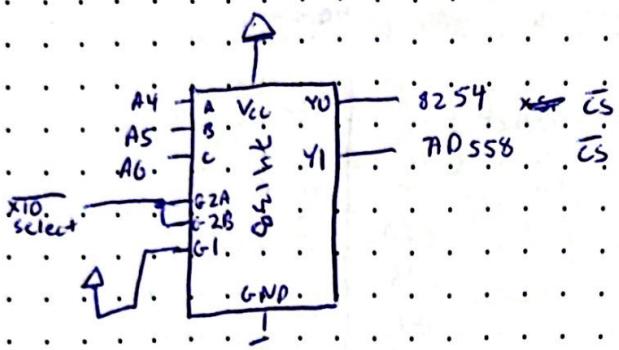

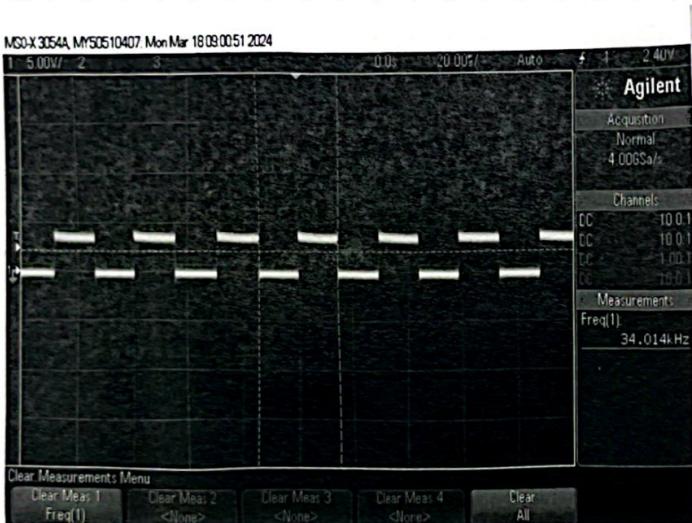when I tried 34 kHz ($w_{FEO3} = 76$, $w_{FEO4} = 26$, $w_{FBP} = 01$)
the plot looked like the below:





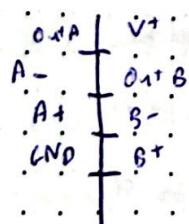In order to protect the DAC, we can use the LM358 Op Amp



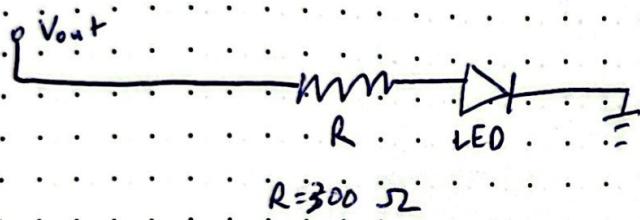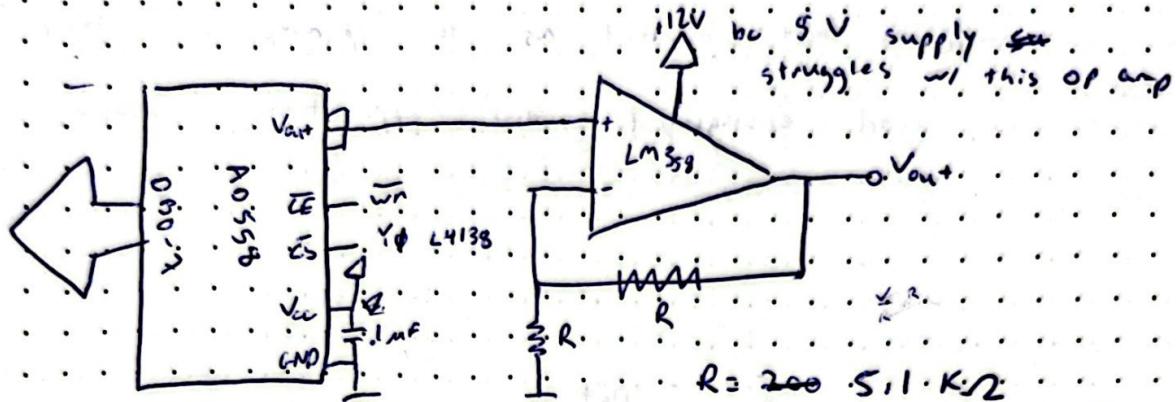Exercise 2 (cont.)

The final circuit looks like the following:



we want current

maxed at 10^{-6} A

✓

At 5V, linear LED max 2V = V_f .

$$R = \frac{V_s - V_f}{I} = \frac{5 - 2}{10^{-6}} = 300 \text{ } \Omega$$


For the DAC, I plotted some values

00 = 0	80 = 1.206	1.2814
10 = 150.8	90 = 1.2814	1.4422
20 = 311.6	A0 = 1.603	
30 = 472.4	B0 = 1.7138	
40 = 633.2	C0 = 1.9246	
50 = 794	D0 = 2.0854	
60 = 954.8	E0 = 2.2513	
70 = 1.1206	F0 = 2.4121	
	FF = 2.5578	

The plot appears roughly like this


Exercise 2 (cont.):

I plotted the results on desmos. Note: the range is not perfect, as the op-amp is cheap. It is good enough for our applications, however.

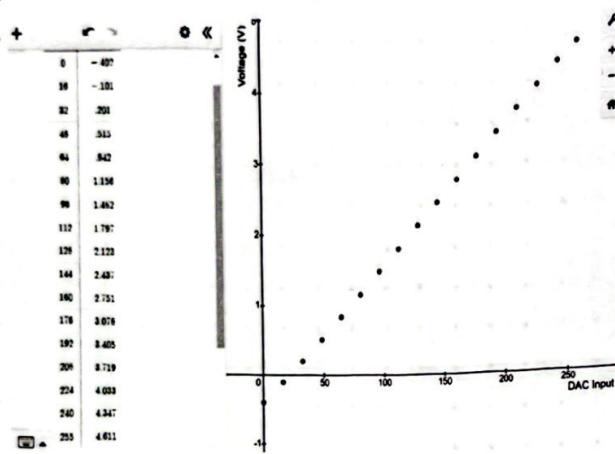

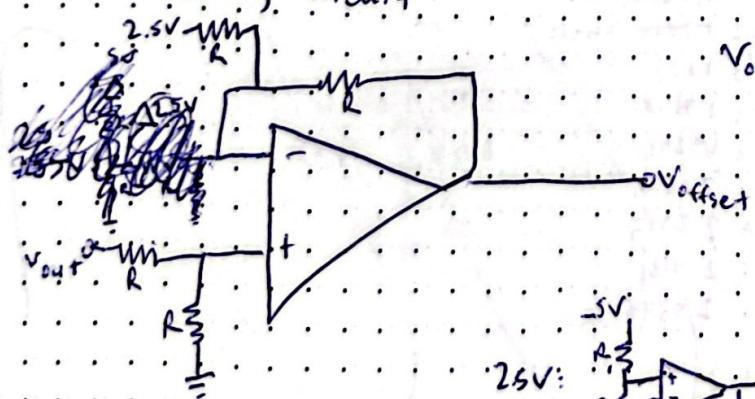Exercise 3: Sine wave generator

We can use another LM358 to make a difference amplifier, powered by $\pm 12V$. We want to create the following circuit:



$$\begin{aligned} V_{\text{offset}} &= V_2 - V_1 \\ &= V_{\text{out}} - 2.5 \text{ V} \end{aligned}$$

$$R = 10 \text{ k}\Omega$$


$$\begin{aligned} 2.5V &= R_2 / (R_1 + R_2) \cdot 5V \\ &= 2.5V (\text{buffered}) \\ R_1 + R_2 &\approx 10k \Omega \\ \text{Used. } &\approx 90 \end{aligned}$$

Exercise 3 (cont):

The result is a variable amplitude between -2.5 and 2.5 V. The actual output is -2.6 to 2.4, within a reasonable range for our application. By using a 10 k Ω pot for the offset, we can tune this to be in range.

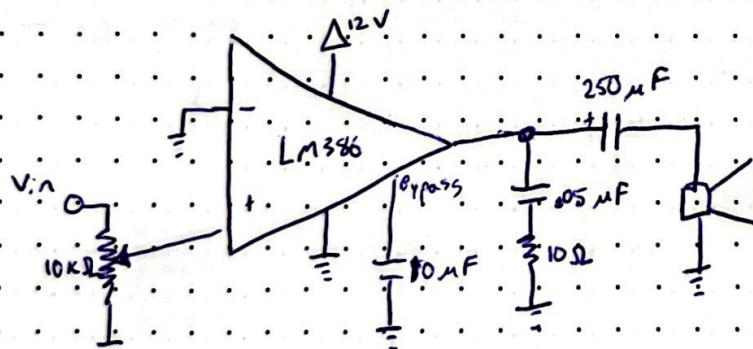
3.1.9. To make the audio amplifier, we can use the following circuit:

Gain 18 Gain
-In 2 Bypass
+In 3 Vs
GND 5 Vout
Initially set to 20
ranges 20-200



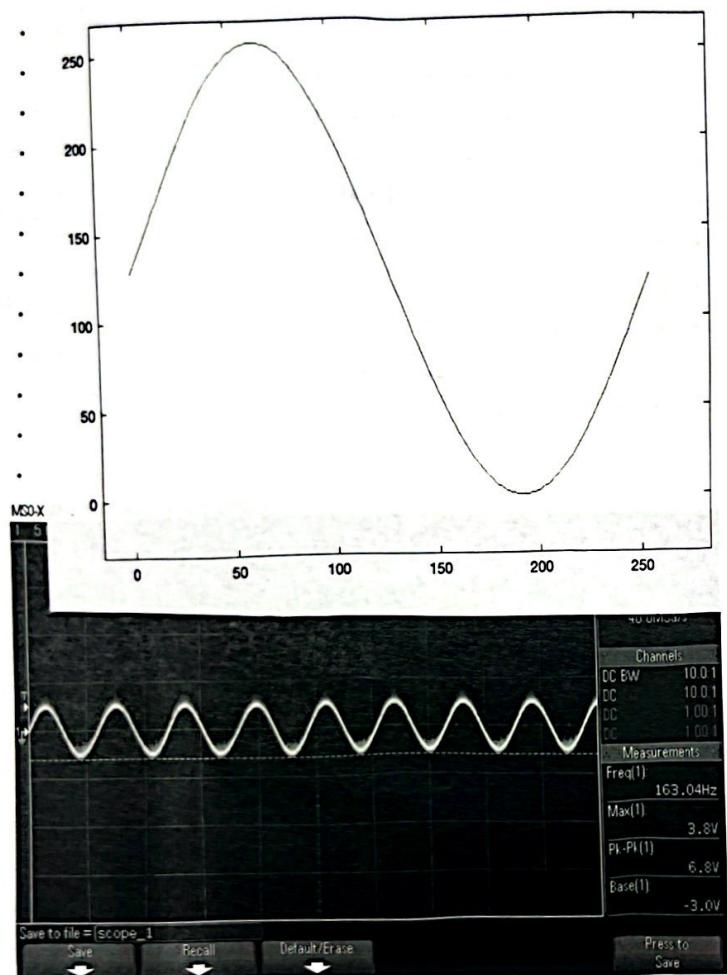
Exercise 3 (cont'd):

When I run the generated sine wave (generated in matlab), the below plot is what I get on the offset op-amp.



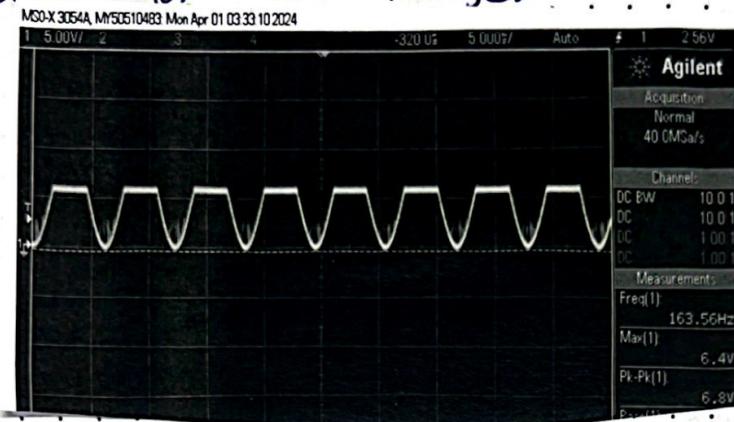Exercise 3 (cont):

When the output is connected to the speaker, the output saturates around 6.5 V, which is good enough for our range.



The output gets more grainy as we increase the volume and the output saturates.


Timing: around 163.64 Hz

	# cycles	done 256 times for 16 256 entries
lcall	2	
mov	1	
inc	1	
push	2	
push	2	
mov (to sp+?)	2	
more	2	
pop	2	
pop	2	
ret	2	
movx	2	
jmp	2	
	$= 22 \times 12$	

$$f = \frac{11059200}{22 \times 12 \times 256} = 163.64 \text{ Hz}$$

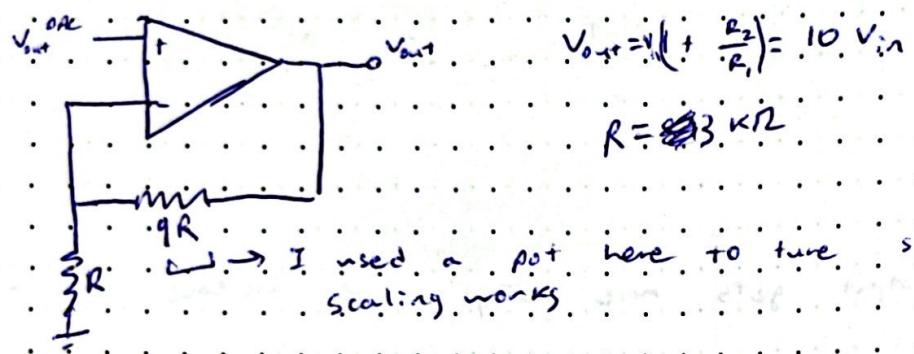
Exercise 3 (cont.):

In order to complete the 10-fold scaling, we can add div a,b, where b holds 10 before sending to the DAC. The scaling op-amp must look like the following:



I used a pot here to tune so the scaling works

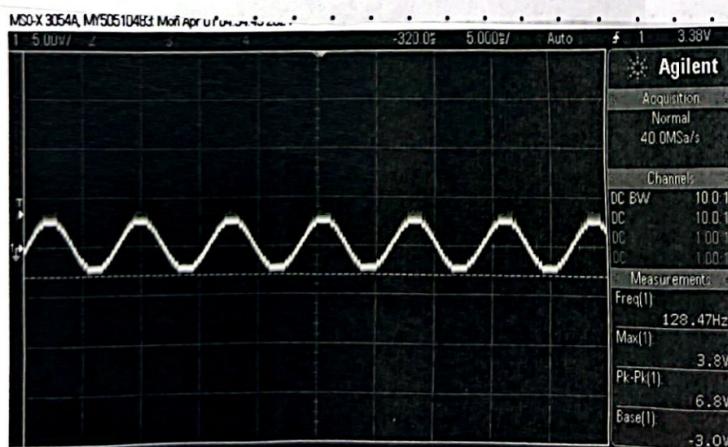When we connected the output to the scope, we see something with more step sizes, or more discrete.




Exercise 3 (cont):

The new sound output is even more grainy, but behaves ~~similarly~~ similarly to the result before. The wave shape appears more discrete because we cannot track fractions. The new freq, 128 Hz, corresponds to the addition of 6 more operation cycles per loop. We added div and mov b, #distr, which add 4 and 2, respectively.

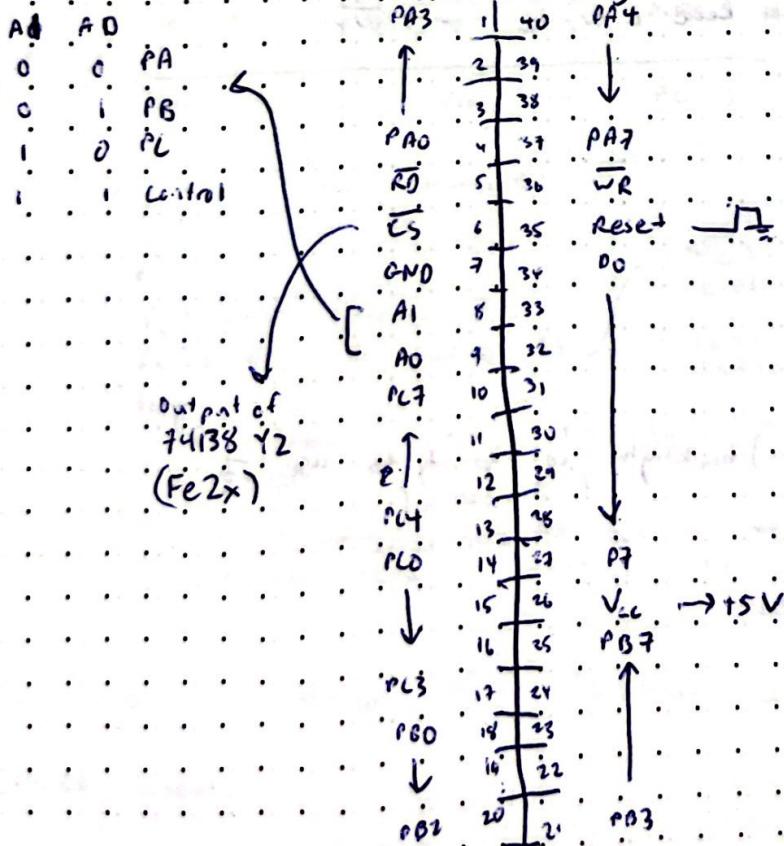Exercise 4: Adding more peripherals


The 8255:

This is essentially adding 3 new P1 outputs:



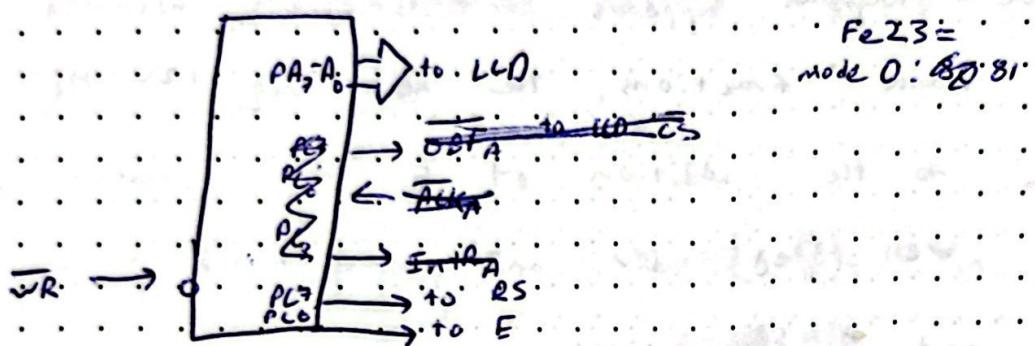Exercise 4 (cont.):

In mode 0 (output), we can use port A and the following configuration:




For the LCD (1602A-1), we can use the following pinout:

1	V _{SS}	— to GND
2	V _{dd}	— to +5V
3	V _D	— \uparrow \uparrow 20kΩ pull
4	RS	i: Data Input f: Instruction Input \rightarrow To PIC
5	R/W	i: Read / Write \rightarrow WR
6	E	— \rightarrow to PIC
7	PSD	
8		
9		
10		
11		
12		
13		
14	PB7	
15	B14	
16	B1K) backlight; not going to use it

To start, for

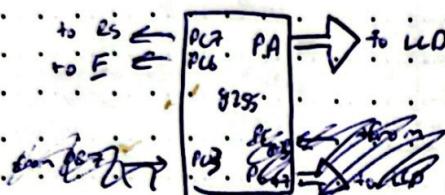Exercise 4 (cont.)

The intuition is that we will have PA send info to the LCD, PLC612 control whether we have data/instruction and whether we are enabled. PLC323 will be inputs from D87 for the RD busy flag. I will use RT delay instead.



To start, we use CW 81 at Fe23, initializing mode 0 with A, B, and C output and 60:3 input. We then set PLC6 to 10. We then write to PA with the character. We then write the enable, or 11 to PLC6. We then can enable. We then RD to the busy flag in PLC0-3 until it's 0. We then write the next character.

init:	Fe23 = 80	mode 0	Fe20 = 38) Sx7 char set.
	Fe22 = 00	initialize RS	Fe22 = 40)
loop:	Fe20 = 0C		= 00) display on, no cursor.
	Fe22 = 40) pulses E	(20, 50) set RD#1 to 0
	<u>Fe22 = 80</u>	sets RS low to read out bit	
	(<u>Fe22 = 00</u> until <u>Fe22 = 03</u>)	writes until busy flag set	
		jump loop	

There are a number of additional initial steps needed, detailed above.

Title	Lab 3 report (p15)	Date
Name		Partner

Exercise 4 (cont.):

The result is below. The output, "6;115 Rules," is


as follows

	output
6	36
0	2E
1	31
1	31
5	35
	20
R	92
u	95
1	6C
e	65
s	73
1	21
.	00 term


It's faint, but it's there

Exercise 4 (cont.):

The ADC0804:

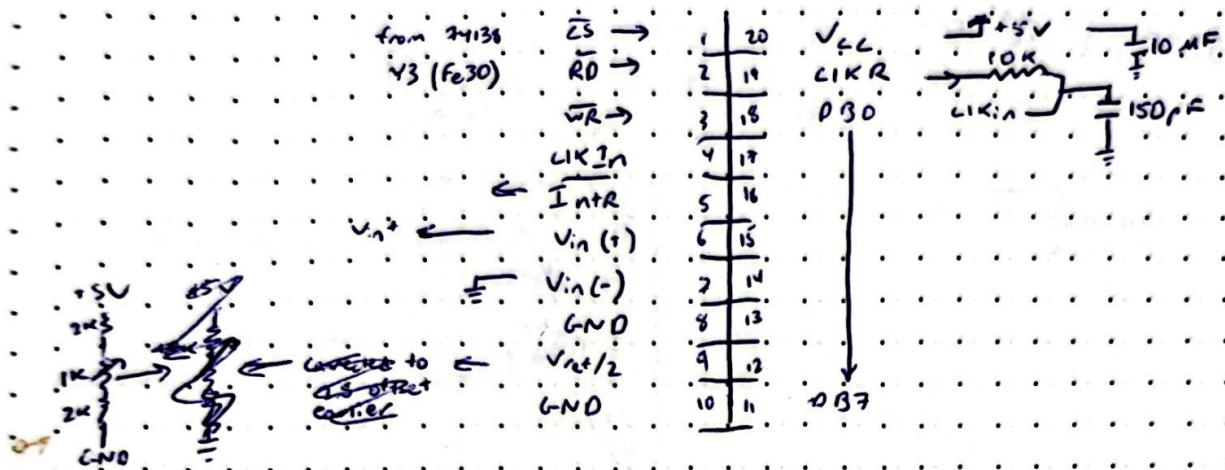

Testing circuit:

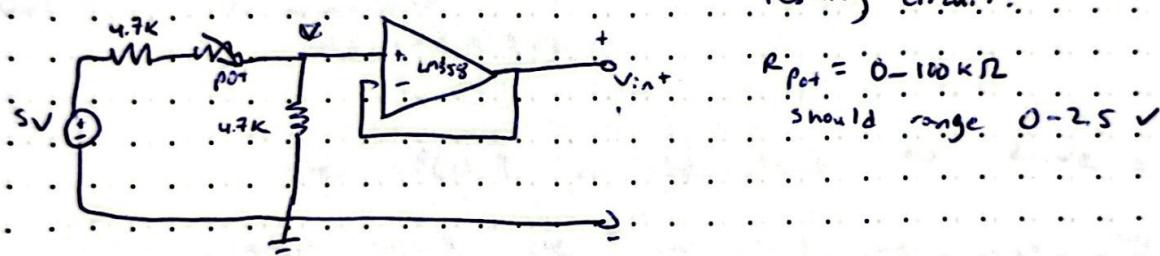

To display on the LCD, I used the same code as the LED display before, but it loops by measuring voltage. The voltage is divided, then uploaded, then checked again... the output is like follows:

$$\begin{array}{r} \times \\ 30 \\ \times \\ 20 \\ \hline 30 \\ 20 \\ \hline 56 \end{array}$$

The output ranges 0-255 for 0-5 V. Dividing by 51 will give the ones place, and dividing the remainder by 5 will give the tenths.

Exercise 4 (cont.):


We can see the resolution is pretty good, i.e.:



Time	Vol.
4.00	0.0000
4.00	1.0000
4.00	2.0000
4.00	200.0000

Exercise 4 (cont.):

Tie L293D:

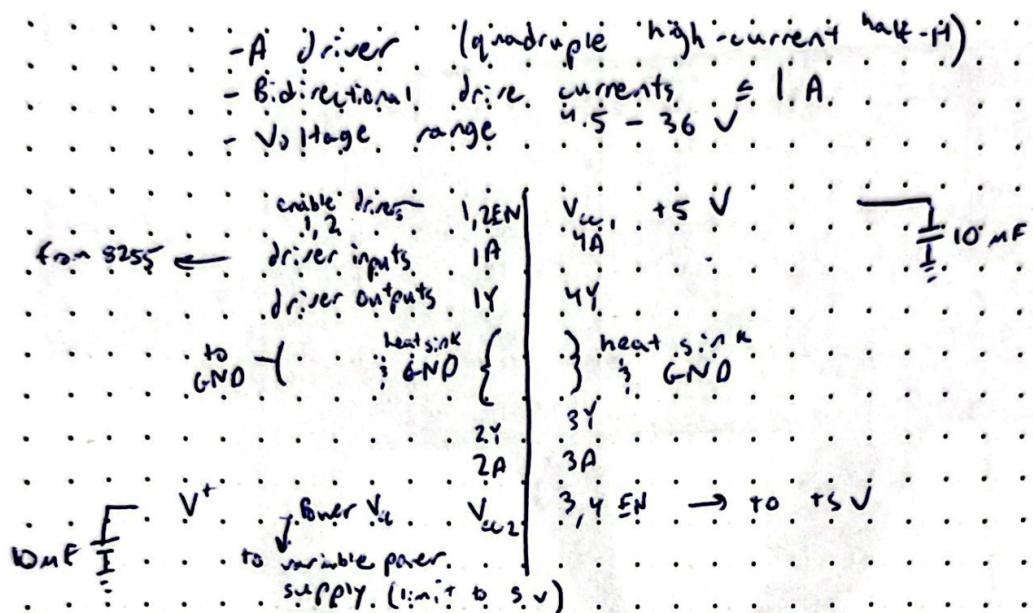

We can use PL0-3 or the 8255 to drive xA. nothing changes about the wr (80), we just need to write to Fc22 to get our desired output (wr/o).

Exercise 5: Lissajous Curves


The schematic for the Laserdiode is attached on the following page.

Lissajous waves:

$$x = A \sin(2\pi f_a t) \quad y = B \sin(2\pi(f_b + \phi) t)$$

$$\textcircled{O} \Rightarrow \frac{a}{b} = 1, \phi = \frac{1}{4} \quad / \Rightarrow \frac{a}{b} = 1, \phi = 0$$

Exercise 5 (cont)

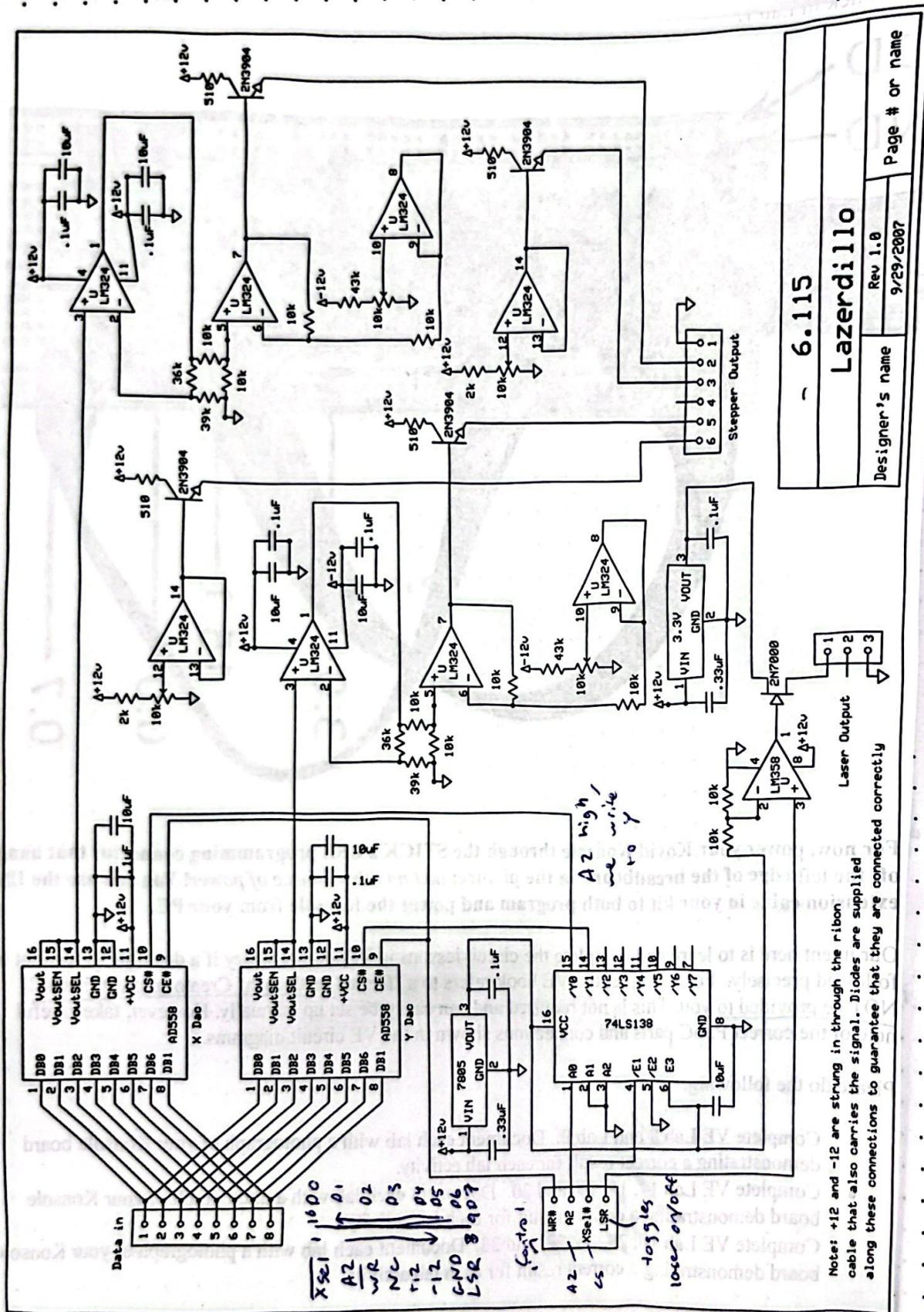

Note: +12 and -12 are strung in through the ribbon cable that also carries the signal. Diodes are supplied along these connections to guarantee that they are connected correctly

- 6.115

Lazerdi110

Designer's name Rev 1.0 Page # or name
9/29/2007

Exercise 5 (cont.):

- The mirrors cannot go above 80 Hz.

- The figure must be completed in 1/20 th of a second or we see movement.

Interfacing:

- using the 256 byte sine wave table and movx a, @a+dptr

- Table advance by frequency (how much we inc each time):

- Timer 0, $T_{HO} = 404\text{ch}$

- + we need to leave enough time for computation

- Leads to 5120 interrupts/second

- for 80 Hz, inc by $4 = \frac{256}{5120} \cdot 80$

- for 54 Hz, inc by 2.7 ? what do we do?

- + use a 16 bit 'count'

- + add bottom (fractional count), then

- + add top with carry

- we can add rotations by offsetting freq by 1 or ... ie.


$$x = \sin(2\pi \cdot 5t + \phi) \quad y = \sin(2\pi \cdot (8t - \phi))$$

- + rotates once a second

Exercise 5 (cont.)

Ai selects between X & Y

Tie Tie fighter:

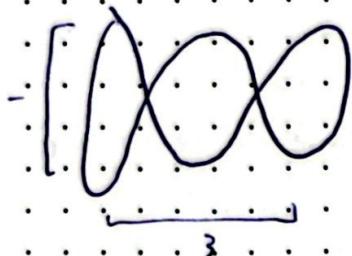

$$\frac{a}{b} = \frac{1}{3}$$

we can use 80 and 24 as our values

$$\frac{256}{5120} \cdot 80 = 2.4$$

$$\frac{256}{5120} \cdot \frac{80}{3} = \frac{2.4}{3}$$

$$\begin{array}{r} 02 \\ 02 \\ \hline 0266h \end{array} \quad \begin{array}{r} 00 \\ 00 \\ \hline 0000h \end{array}$$


$$\begin{array}{r} 11001100 \\ 00001100 \\ \hline 10101010 \\ 0111h \end{array}$$

When we swap x, and y, we get

We found that this doesn't result in perfect matching, so I'll use

 $\frac{1}{20} \cdot X$ and $\frac{1}{20} \cdot Y$ to find good values

$$\text{offset} = \frac{60}{3} \quad \text{and} \quad \frac{1}{20} \cdot Y = 60 \quad X = 20$$

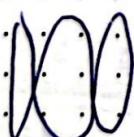Note, we need a phase shift of $\frac{\pi}{4}$ to x to make tie shape

Exercise 5 (cont.):

Circle: $\frac{a}{b} = 1$, $\phi = \frac{1}{4}$ (start y at 40n)




$a = b = 80$, offset = 4

$a = 1$, $b = 4$, $\phi = 0$

$b = 80 \text{ Hz} \rightarrow 4$ starts at
 $a = 20 \text{ Hz} \rightarrow 1$ 0000 0000

The resulting shape is

hard to draw

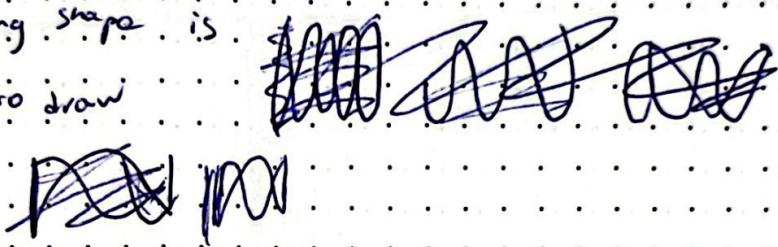

To rotate, we can use a offset on 80 to make it rotate faster. ^{phase} offset of 1 \Rightarrow 1 Hz. phase offset of 1.5 leads to 1.5 Hz. I will use


~~offset (for rotation), instead set 2.25 to get the right rotation.~~

$$\text{offset } 1.25 \quad \frac{50}{58.75} : \frac{1}{20} = 3 - \frac{1.25}{20} = 3 - 0.0625 = 2.9375 = 0.2 \text{ EF}$$



25
20
625
125

Note: I also added a rotation up/down button to the keypad relay.


Exercise 6: PSoC1I

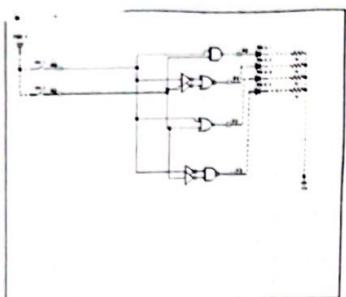




Ex 8

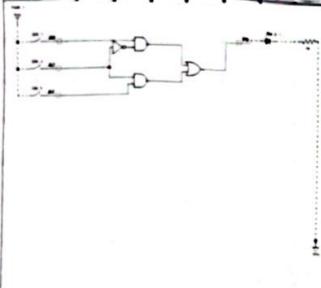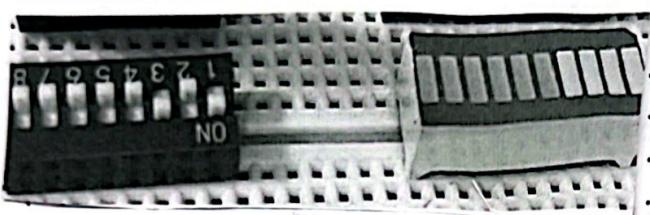


Ex 9

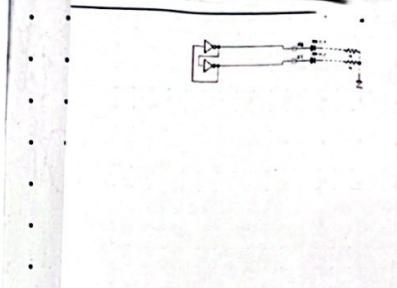



Ex 17

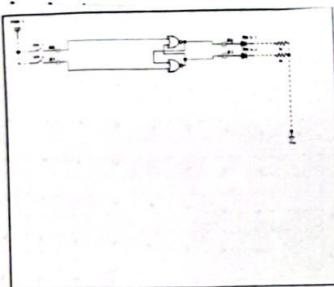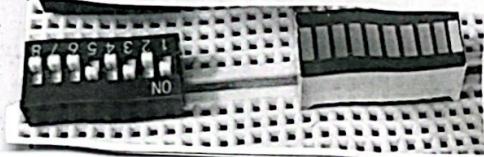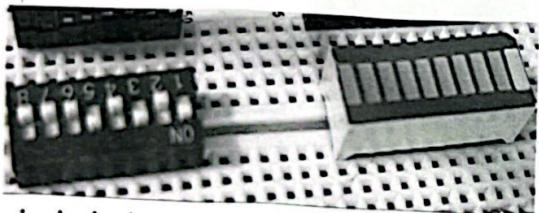


Ex 18

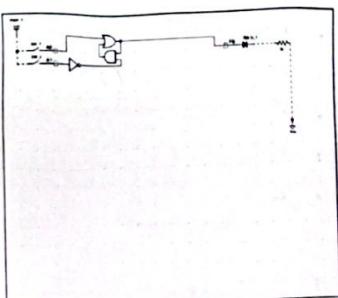



Ex 19

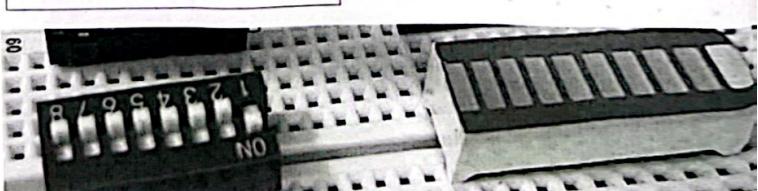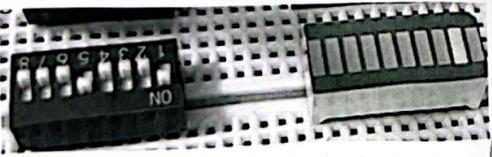



Exercise 6 (cont.):

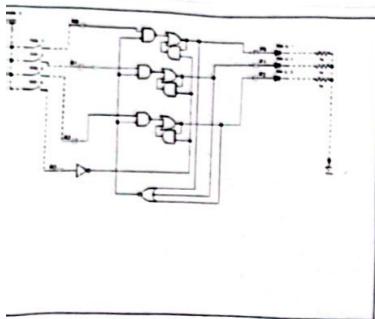



Ex 20

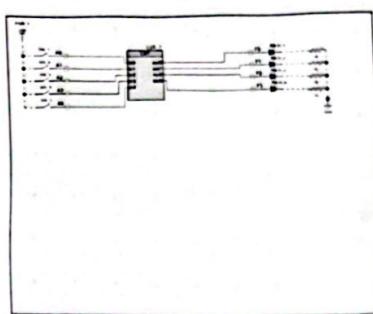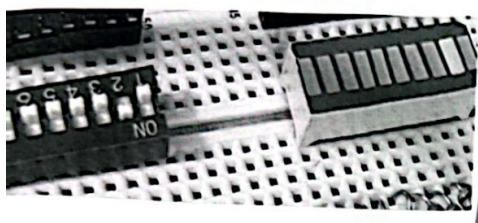


Ex 16

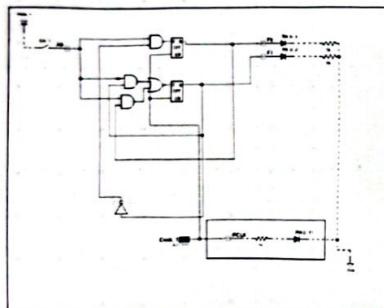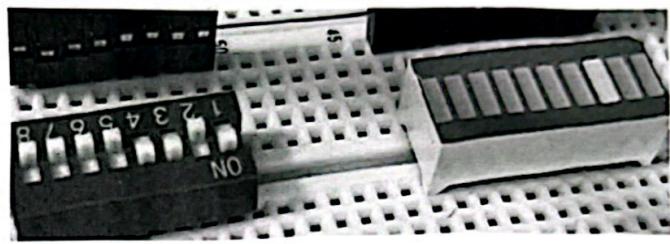


Ex 25

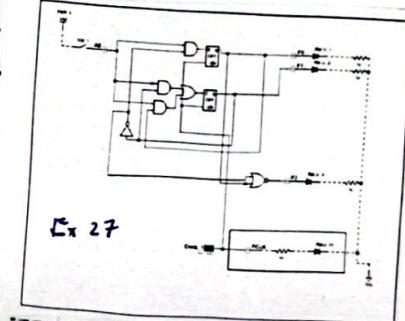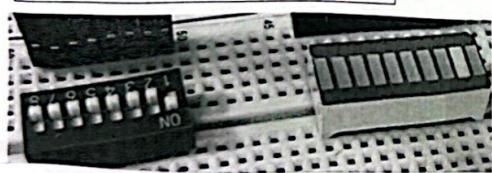


Ex 27

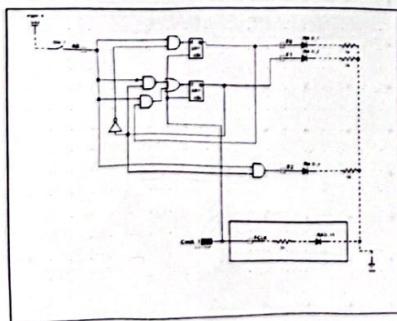

Ex 26

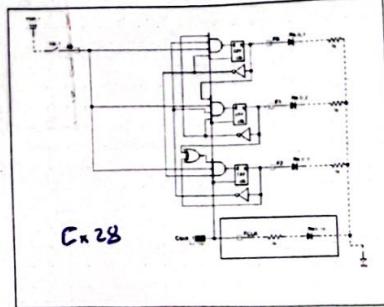

Ex 28

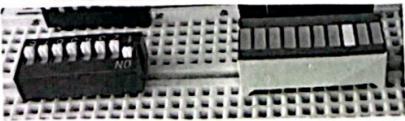

Title

Date

Name

Partner

of
End ref of
3
Lab

Checkoff: Savannah Gordon

10/10 SGU

Sinow Ospell
4-2-24



6.115 Lab 4

Goals:

- ① Learn how to use peripherals on the 2313P
- ② Use an A/D converter and LCD screen
- ③ Learn about electromagnetic actuators
- ④ Understand, design, and construct a digital feedback controller.
- ⑤ Practice writing C code for the PSOC.

Exercises:

- ① Tie relay (a simple linear actuator)
- ② Get to know the DC motor.
- ③ Pulse Width Modulation
- ④ Model the DC Motor
- ⑤ Play with the robot arm
- ⑥ Feedback control for a 1st order plant
- ⑦ Stepper motors
- ⑧ PSOC
- ⑨ Spin Diode Image Reconstruction

Note:

I revised my kit to allow for better wire management. Attached is...

① Keypad and 74C922N:

- Output connected to P1.0-3
- DA connected to -

② ADC0804

- located at F010h located @ F010h
- Intr \rightarrow P3.5

③ DAC (AD5583N + LM358N)

- Connected to F000 and adjustable gain block.

④ 8255

- PA0-7 : LCD D0-D7

- PB : open

- (Q) - PC0-3 : 1A-4A on driver

- PC4-7 : open, E , R_s , A_S on LCD

⑤ DM74LS138N (multiplexer)

F000 : DAC

F010 : ADC

F010 : 8255

Note (cont.):

⑥ L293DNE (Driver)

- 1A-4A connected to 8255 PA0-3

⑦ LCD screen


- D0-7 connected to 8255 PA0-7

- E R_S, Rx, E connected to 8255 PL7-86
↓ GND.

Exercise 8: PSoC!!

4/12/24

Exercise 2: (^{I shorted R70} I connected +3V_{IO} to A1K) to see the result
for a photo (ADC output from POT)

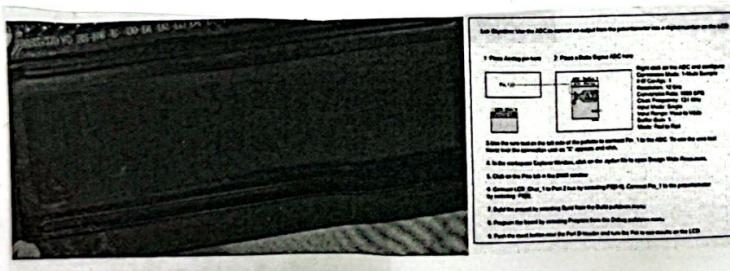


Exercise 3: "Breathing" LED

~~I made PWM1 have a duty cycle of 0.5 and PWM2~~


~~a duty cycle of 0.5. I connected the pin to PWM 1 1/2~~

~~have duty of 128, but 2 has period of 255, Pin 1 is connected to P6.2.~~

Exercise : 8 (cont.) :

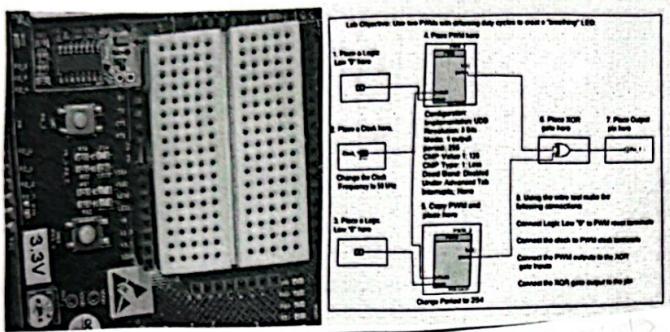


Custom Design:

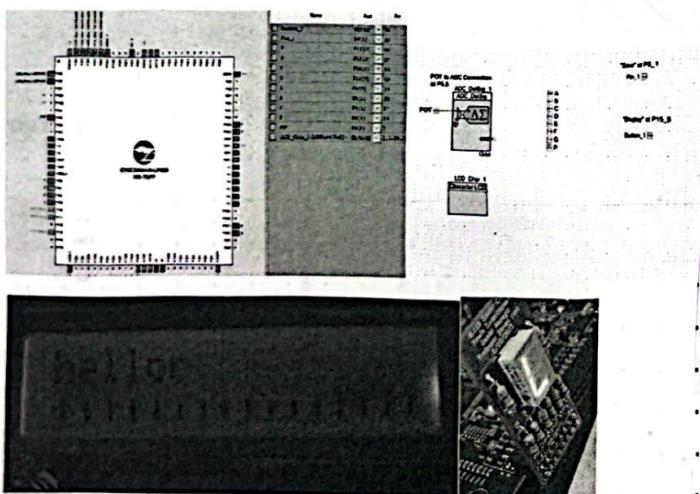

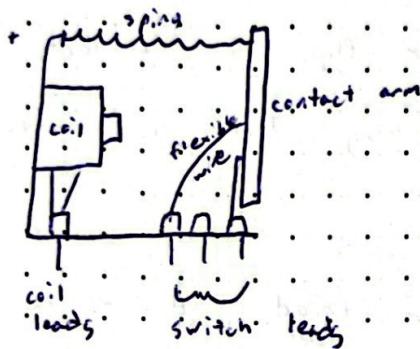Exercise 1: The Relay!


Relays: (From notes and instructions)

- A current sent through a coil magnet pulls a flexible, spring-loaded conductive-plate from switch contacts (for mechanical relays).
- Allow for high currents and slow switching.



- Ours is a subminiature relay
- + rated for 12 V, ~160 Ω coil resistance
- + The coil acts as an inductor, meaning -
 - high voltage spike when current cut
- + As a result, we need a diode (IN4001)


+ Our relay is SPDT

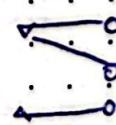

Turning on power supply should flip from one switch to another

Exercise 1 (cont.)

This is the schematic:

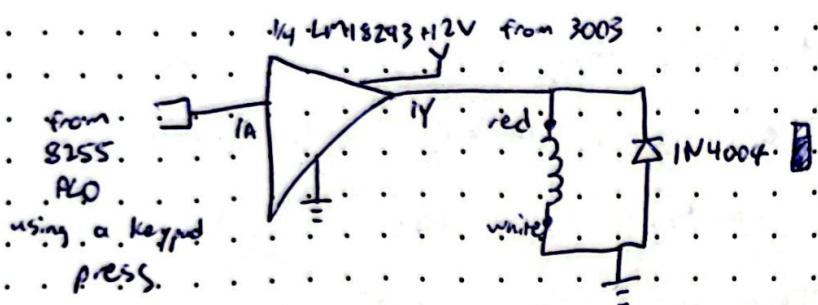

Toggling the power flips the contacts from one to the other. Tie leads switching does not affect the behavior of the relay.

Note: I believe I fried 2A w/ a 12V supply, so I will avoid using it. *I replaced the chip.

4/9/24

Exercise 2 (cont.); DC Motor

Our motor has a brushed DC motor and an AC generator from a spinning magnet disk.

- The AC generator frequency is 8x the rotation frequency.

- The AC generator is used to measure rotation frequency, important for feedback systems.

- We will connect to lab power, and connect the AC generator to the oscilloscope.

Exercise 2 (cont):


Pinout

AC Generator → to oscilloscope

V_t } to 3003 power supply

V₋

R	I	I _{load}	I _{load}	V _{drive}
0	0			0
1	0			0
2	33			1
3	113			2.6
4	153			4.26
5	243			5.63
6	314			7
7	370			8.8
8	422			10
9	500			11.3
10	570			12.9
11	635			13.7
12	700	.22	.4	15.3

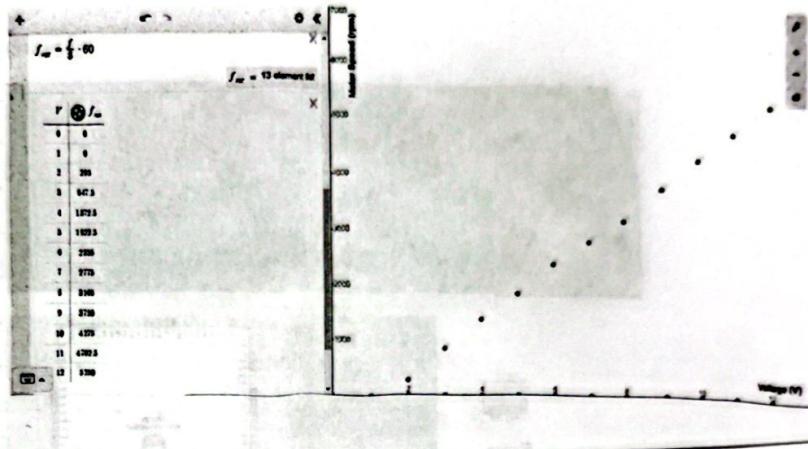

When we apply a load, the shaft speed goes down, and current goes up. This implies that voltage drop affects the speed of the motor, while current affects the amount of force/torque the motor can apply.

Exercise 3: PWM


Instead of using the DAC for variable drive voltages, we can use PWM with different duty cycles and a binary waveform.

Exercise 3 (cont.):

The average V is DV_s , where D is the proportion of the period spent at V_s ; $f_{sw} = \frac{1}{T}$. The waveform should repeat every T seconds, spending DT high and $(1-D)T$ low. By adding a low-pass filter to the load, we can extract the DC component of the average voltage. This is a Buck converter.

To test, we can make a low frequency system (0.5 Hz) with $D=0.5$ and high frequency (5000 Hz) with $D=0.5$.

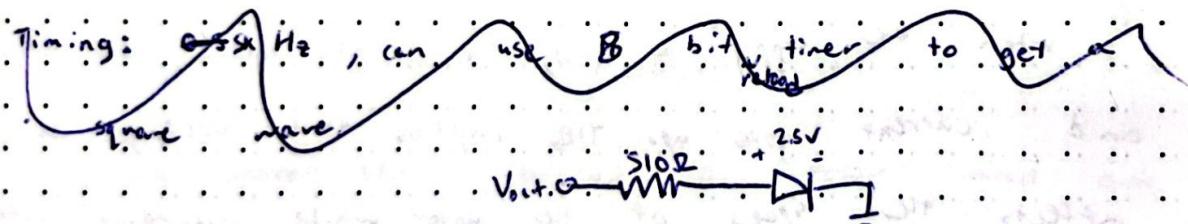~~I will disconnect 4A from PC3, and instead connect it to pin 14 so that I can use a direct~~




In the high freq case, we have the light appearing consistently lit. The diode is the low pass filter. To make the 0.5 Hz square, I used a 10,000x decrease in period by nested counters. The led flashes every other second.

Exercise 3 (cont.)

when we instead connect Volt to the DC motor, we get the following responses:


High frequency:

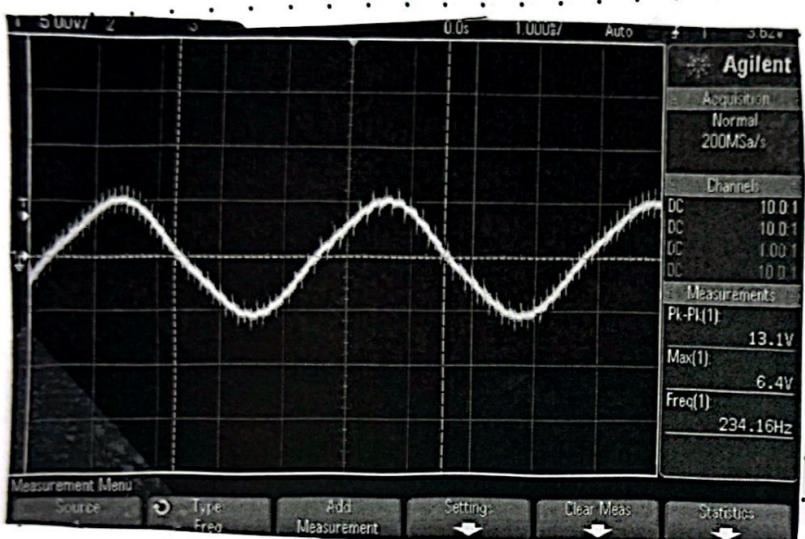

$$\text{freq} = 250 \text{ Hz}$$

$$|V| = 6.8 \text{ V}$$

Low frequency:


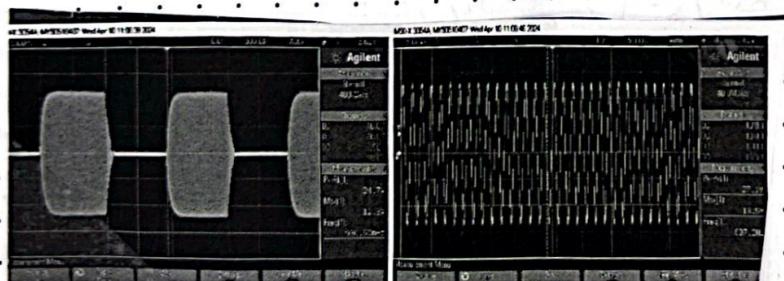


$$\text{freq} = 0 \text{ Hz or } 637 \text{ Hz}$$

$$|V| = 0 \text{ V or } 12 \text{ V}$$

The motor is on/off in the 0.5 Hz situation, reaching SS in both before the next step. In the high freq case, we have a voltage output and frequency roughly equivalent to 5-6 V, half of our drive. The coil is our low pass filter.

Exercise 4: DC Motor model

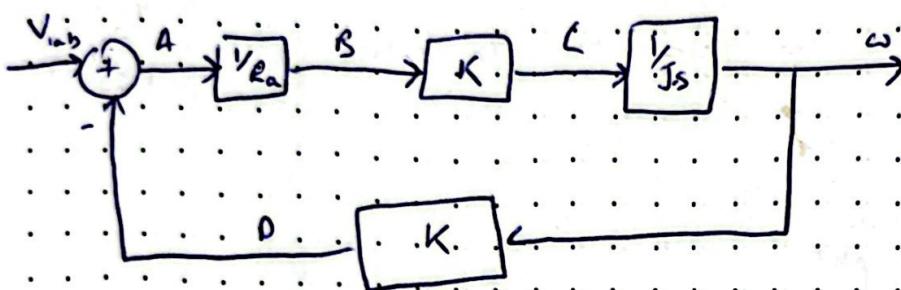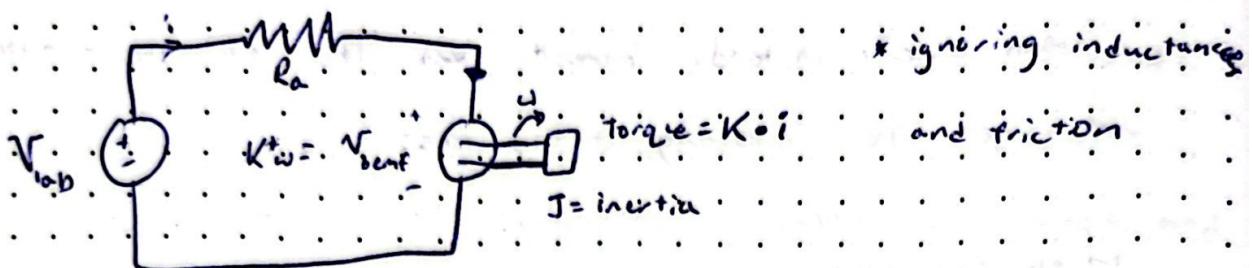

$$A = V_{lab} - K\omega = (\text{voltage across resistor})$$

$$D = K\omega \in V_{backf.}$$

$$B = \frac{V_{lab} - K\omega}{R_a} (= \text{current})$$

$$C = \frac{K}{R_a} (V_{lab} - K\omega) (= \text{Torque})$$

$$\omega = \frac{K}{R_a(J \cdot s)} (V_{lab} - K\omega) = \left(\int \frac{10^{-3} \text{ Nm}}{J} dt \right)$$


$$\omega \left(1 + K^2 \right) = \frac{K}{R_a(J \cdot s)} V_{lab}$$

$$\omega = \frac{K}{1 + \frac{K^2}{R_a J_s}} \frac{1}{J R_a s} V_{lab}$$

$$\omega = \frac{K}{J R_a s + K^2} V_{lab}$$

$$\omega = \frac{1}{K + \frac{R_a}{J} s} V_{lab}$$
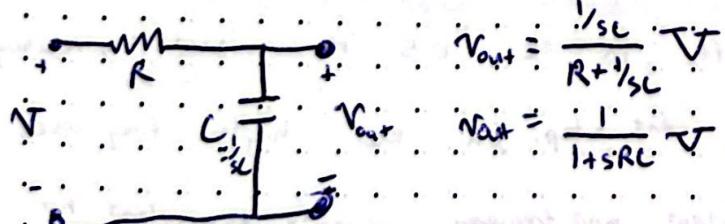
$$\omega = \frac{K}{J R_a s (1 + K)} V_{lab}$$



$$V_{out} = \frac{1/sL}{R + 1/sL} V$$

$$V_{out} = \frac{1}{1 + sRL} V$$

Exercise 4 (cont.):

The two circuits (RL and DC motor) differ in a number of ways. First off, at low frequencies (DC), the angular speed is $\frac{1}{K} V_{out}$, where V_{out} is just V . They are both proportional to input voltage. However, both circuits attenuate higher frequencies.


4/11/24

Exercise 5: Robot Arm

- we have 5 joints, maximally driven at 6 V

Wrist +	Gripper +	We will control two of these joints with the L293.
Shoulder +	NC	
Base +	NC	I will use the Base + gripper forearm elbow
Elbow +	NC	
	NC	
	8 16	

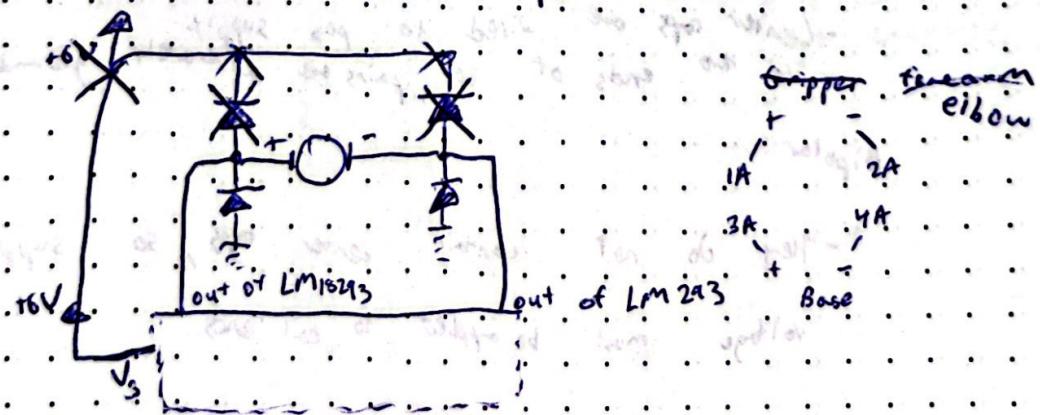Per the wiring, the circuit per each motor should be



- For the keypad, A-D will be each of the motors

Exercise 5 (cont.):

- Q will be 1 ~~is~~ Duty cycle, 1 is 0.1, 2 is 0.2, and so on and so forth.

- Closed loops are better in industrial arms, as we don't have to worry about predicting the exact location of the arm after a amount of input, we can just respond to the way the arm is behaving in the system as a whole.

Exercise 7: Stepper Motors

Stepper Motors respond to square waves, useful because position can be controlled.

- our stepper motor steps 15° each step

Unipolar:

- Center taps are wired to pos supply.
- The two ends of coil pairs are alternately grounded.


Bipolar:

- They do not contain center taps, so supply voltage must be applied to coil ends.

Exercise 7. (cont.):


To drive stepper motors, you need freewheeling diodes and bypass capacitors.

For one coil:

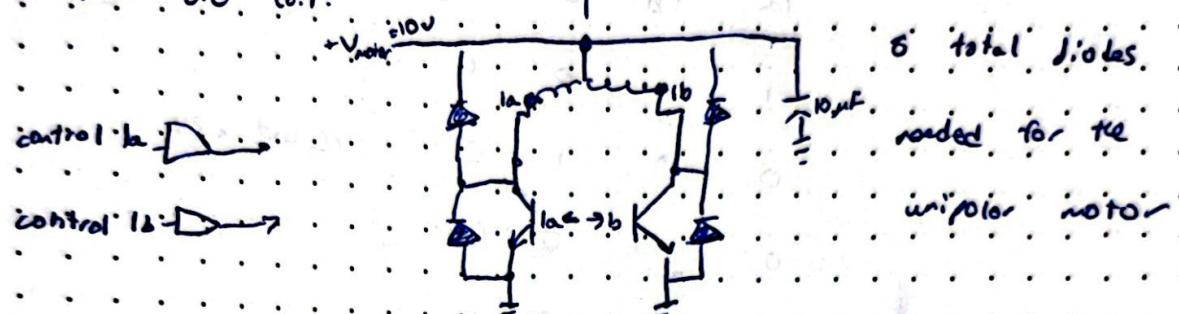

We have a unipolar motor (6 leads)

To identify, we have

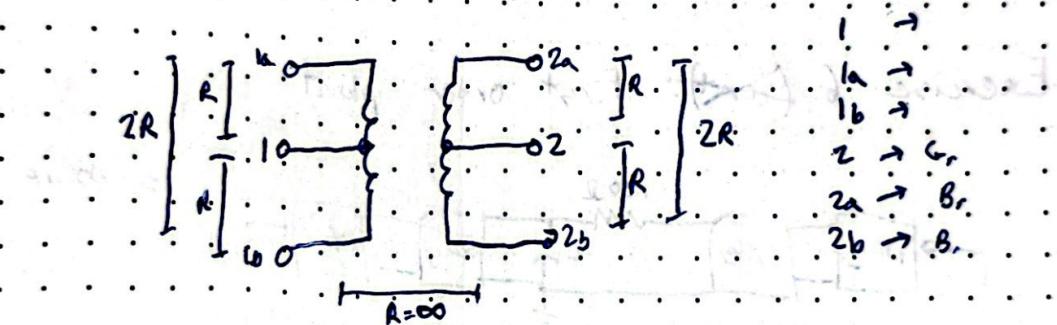


Spin diode:

A _D	1	24	S _O	
	2	23		
	3	22	3	
A _B	7	21		
E _I	5	20	X	
GND	6	19	GND	
V _{cc}	7	18	V _{cc}	
GND	8	17	GND	
GND	9	16	GND	
1 - R _D	10	15	B _r	- 2a
1a - Y _E	11	14	B _r	- 2b
2b - O _r	12	13	B _r	- 2


will only connect pins 10-15 for this exercise

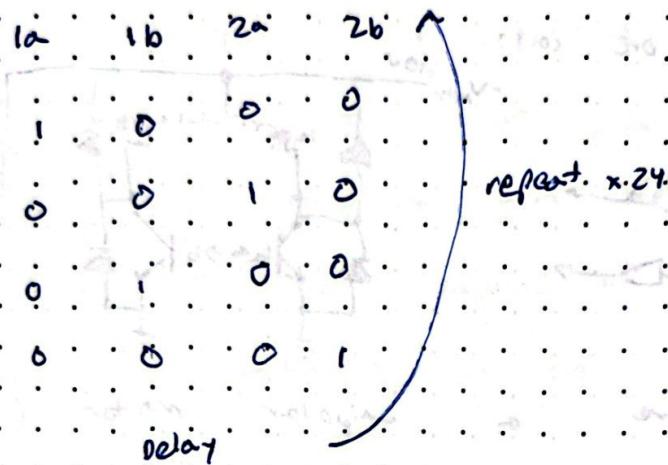Exercise 7 (cont):


In order to rotate spin diode, we must follow the following step routine:




Exercise 6 (cont): First order plant

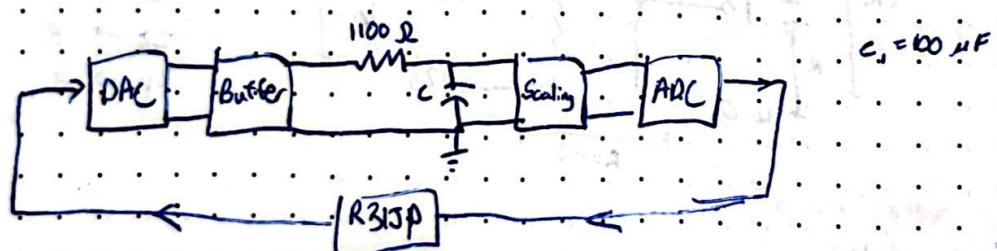

Buffer:

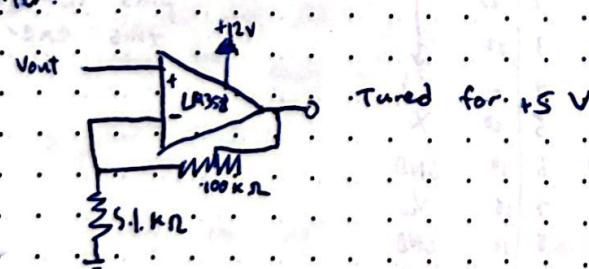


Scaling:

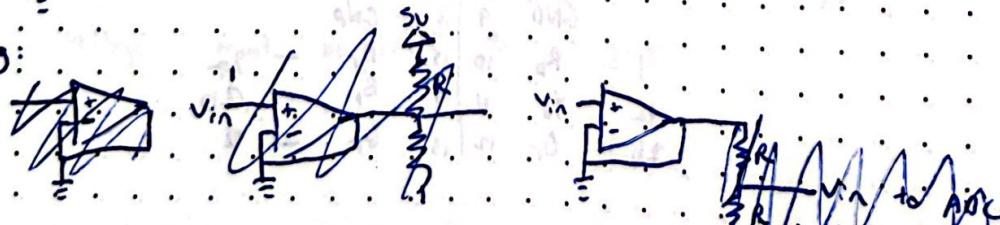

We have a divider to avoid too much voltage.

Exercice 6 (cont.);

Total schematic:

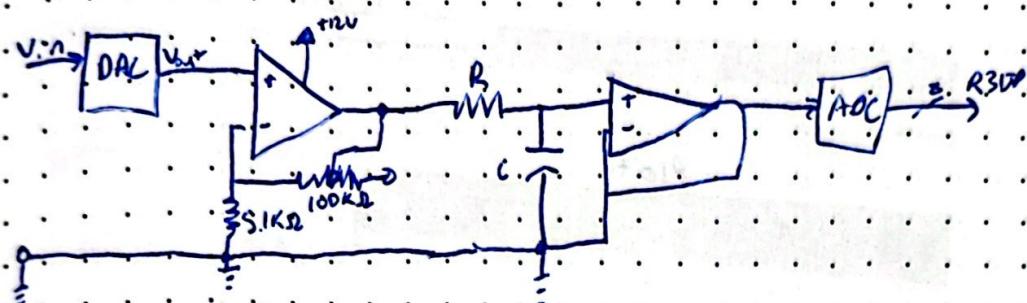

There appears to be a faster rise time than fall:

(more resolution in positive error)

$$Y_{fall} = \frac{1.64 \text{ V}}{\frac{444 \text{ ms}}{81}} = 1.04 \text{ V}$$


$$1.48 \text{ V} - 368 = \frac{1.4 \text{ V} - 368}{2} = 71 \text{ ms}$$

$$t_{rise} = 105 - 71 = 34 \text{ ms}$$


~~we expect~~

We expect convergence to $V_{ctrl} = \frac{1}{\sqrt{L^2 R^2 C^2}} \cdot \frac{1}{N_{ADC}} = \frac{1}{\sqrt{(2 \pi 100 \cdot 10)^2}} \cdot \frac{1}{2^8} \cdot 2.5 \text{ V} = 2.06 \text{ V}$

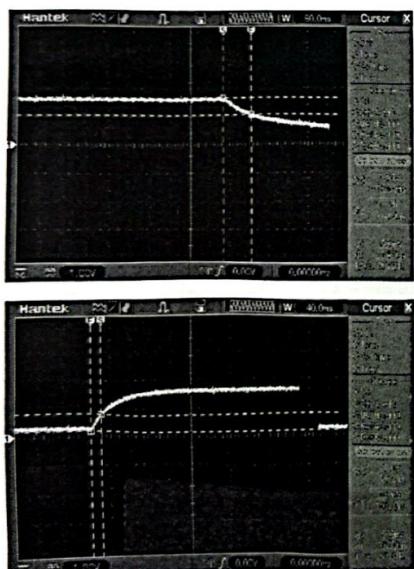Difference comes from resolution in devices and internal capacitances.



Exercise 6 (cont):

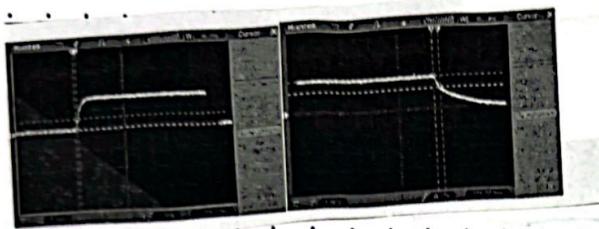Now with $33 \mu F$ 


Rise:
Exponential $T = 7 \text{ ms}$

Fall: 39 ms

we expect V_o to be $\frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} V_{in} = 2.437 \text{ V}$

Finally with $1 \mu F$:

Note: we have an oscillatory response at the top

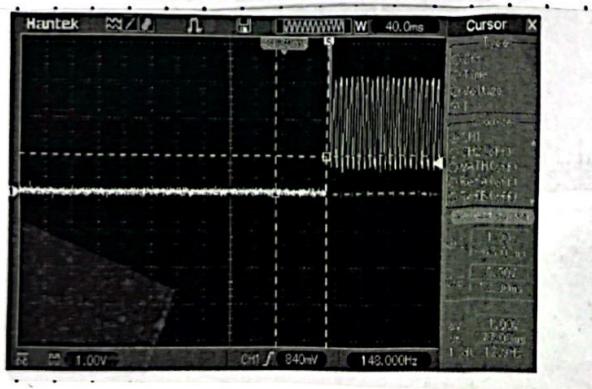rise time: $\sim 2 \text{ ms}$ Fall: $\sqrt{3} \text{ ms}$

Exercise 6 (cont.):


We have $V_{out} = \frac{K}{1+sRL+K} V_{in}$ so in all cases, $V_{out}(t=0)$

should be $\frac{K}{1+K} V_{in}$, or $\frac{2}{3} V_{in} = 1.67 \text{ V}$. Differences

come from the small contribution of the sRL and the internal R/L of the circuits.

Exercise 9: Image Reconstruction

4/16/24

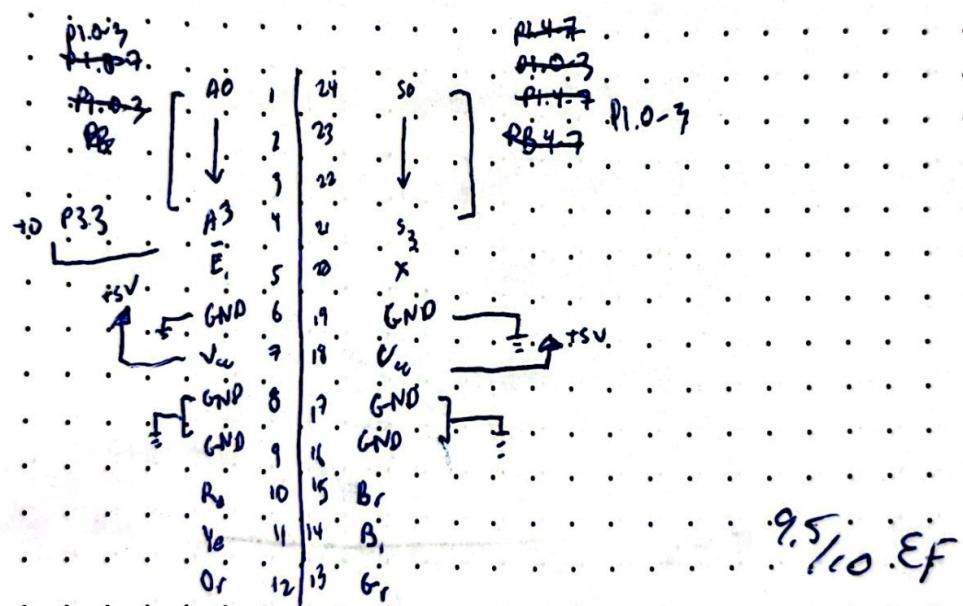


6.115 Final Project

Goals:

- ① Develop a close-to fully functional saxophone synthesizer.
 - (a) Buttons pressed lead to a note that is played on a lab kit speaker.
 - (b) A sewing machine pedal controls volume.
 - (c) A mouthpiece (LED + photoresistor) detect intonation.
- ② Make a Karaoke ~~feantone~~ feature.
 - (a) Desired buttons pressed and note will be displayed on a TFT/LCD Display.
 - (b) Some measure of quality of tracking is recorded.
- ③ Make the sound resemble a saxophone.
 - (a) Use matlab to get a start of the intonation, the middle, and the end of a note.

Part I: Buttons to note

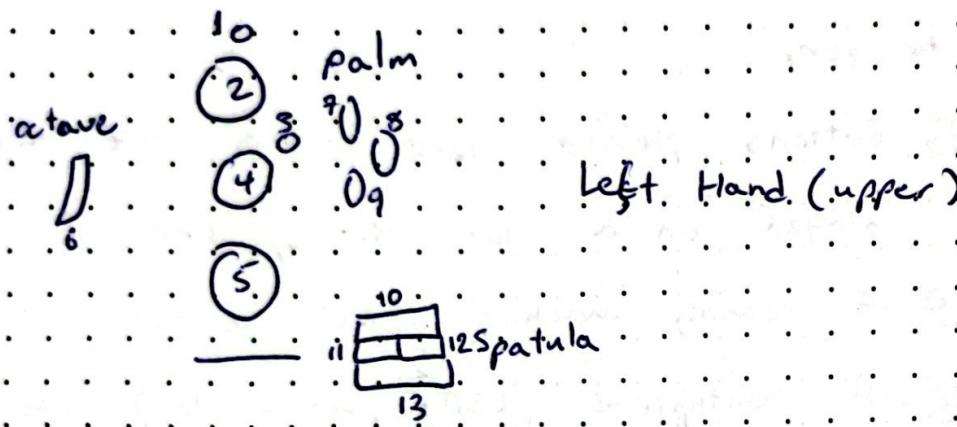The tenor saxophone has 23 buttons, but not all are necessary. The markings are below.




Right Hand (Lower)


note	fing	keys
B _b		2, 4, 5, 14, 15, 16, 23, 13
B		2, 4, 5, 14, 15, 16, 23, 11
C		2, 4, 5, 14, 15, 16, 23
C ₄		2, 4, 5, 14, 15, 16, 23, 12
D		2, 4, 5, 14, 15, 16
E _b		2, 4, 5, 14, 15, 16, 22
E		2, 4, 5, 14, 15
F		2, 4, 5, 14
F _#		2, 4, 5, 15
G		2, 4, 5
G _#		2, 4, 5, 10
A		2, 4
B _b		2, 11, 13

Part I (cont.):

note	freq	keys
B		2
C		4
C#		none
D		6, 2, 4, 5, 14, 15, 16
Eb		6, 2, 4, 5, 14, 15, 16, 22
E		6, 2, 4, 5, 14, 15
F		6, 2, 4, 5, 14
F#		6, 2, 4, 5, 15
G		6, 2, 4, 5
G#		6, 2, 4, 5, 10
A		6, 2, 4
Bb		6, 2, 4, 20
B		6, 2
C		6, 4
C#		6,

D → F require palm keys, but are high enough that they can be ignored for the initial iteration. As a result, only 14 keys are used, notated as follows.

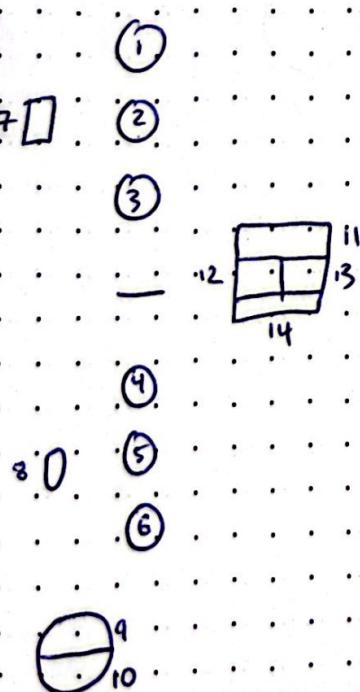

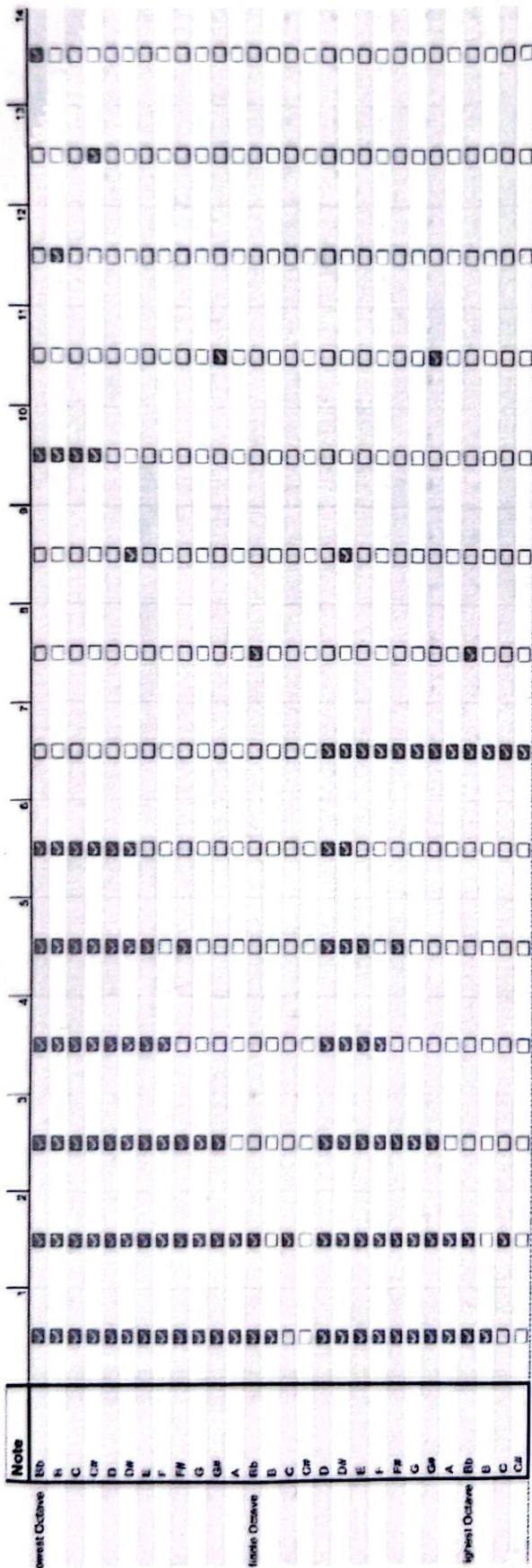

Part II : The sound wave

I downloaded a saxophone note waveform online and entered it into matlab. I was able to deconstruct the signal into a beginning, middle, and ending waveform. The beginning waveform is pressed started whenever a note is started; the middle is held for each all of the time the layout is pressed; the ending waveform comes before a new intonation (optional for now).


I will start with a repeated waveform in the output DAC. I also found the frequencies/period of a 16 bit counter on a 24 MHz clock for each note.

B _b	5838.75	4110	E	16520.625	1453
B _#	6187.5	3879	F	12499.375	1371
C	6553.75	3662	F#	18540	1294
C#	6946.875	3455	G	19642.5	1222
D	7359.5	3262	G#	20812.5	1153
D#	7776.25	3078	A	22050	1088
E	8257.5	2906	B	23360.625	1027
F	8752.5	2742	B#	24750	970
F#	9270	2589	C	26223.75	915
G	9821.25	2444	C#	27781.875	864
G#	10406.25	2306			
A	11025	2177			
B _b	11683.75	2054			
B	12375	1939			
C	13111.875	1830			
C#	13888.125	1728			
D	14715	1631			
D#	15592.5	1539			

these represent sampling frequencies of the waveform.

Part II (cont.)

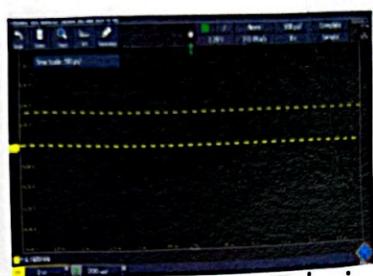When I test with the following circuit, I can get 1/2 of pulses at the frequencies needed.




Now I need to send the waveforms out of a DAC pin.

5/8/24


I created a ^{matlab} project that downloaded the waveforms for a note, split up into beginning, repeating, and ending. I stored those in flash memory, then used a dithered DAC (averages 4 outputs to generate a wave) to make a sin waveform across a 10 nF capacitor. The circuit is as shown on the following page. When sweeping through frequencies, I get varied size waveforms.

Part II (cont.)

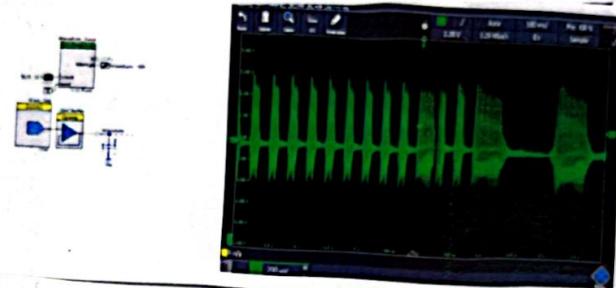


Part III: Buttons to output

Buttons were bought on Amazon, both with two terminal TTP type connected to GND and 3.3V and resistive pull-down. I created a network of 14 buttons (described earlier) that were debounced (at a frequency of 300 Hz) and stored in two status registers. An interrupt is also generated whenever buttons are change configuration. The I began by using each of the buttons to correspond to a different waveform. The configuration will come later. Pictures are on a separate the following page.

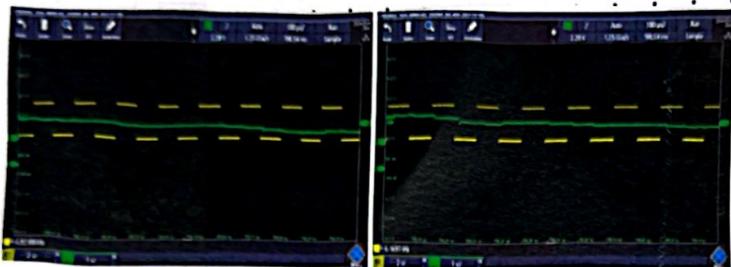Part III (cont.);


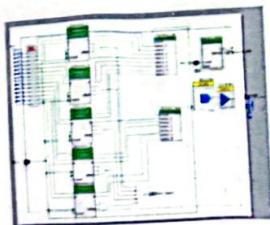
I tested the ~~voltage~~ press singular button press starting and stopping a note, and it behaved precisely how I expected. The pictures are above, demonstrating a switch from B2 to C#3. The out of the circuit is shown below.



Now the logic needs to be connected to a note. Using the logic table from earlier, we can regulate how button presses affect the note output.

Part III (cont.):


I used the following chunk of code and PCB wiring to create a board that took the button inputs to certain ports and the volume pedal to an ADC I also constructed a physical system for my parts that resembles a saxophone.

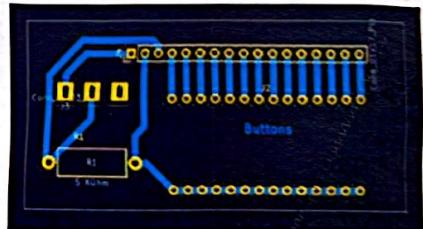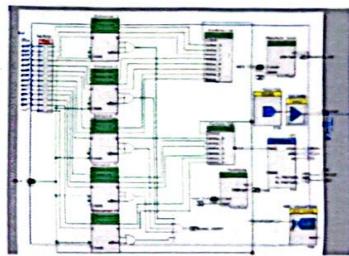

Part IV: The TFT Display

Now we need to create the TFT Display connection. The course website has a great demonstration of how to use the display with a ILI9341 controller and 8-bit SPI. The demo has functions for writing commands and data. We start with `tftStart()` to configure the display. We will also use `emWin` as a graphics library to draw on our display.


We will use the following pinout:

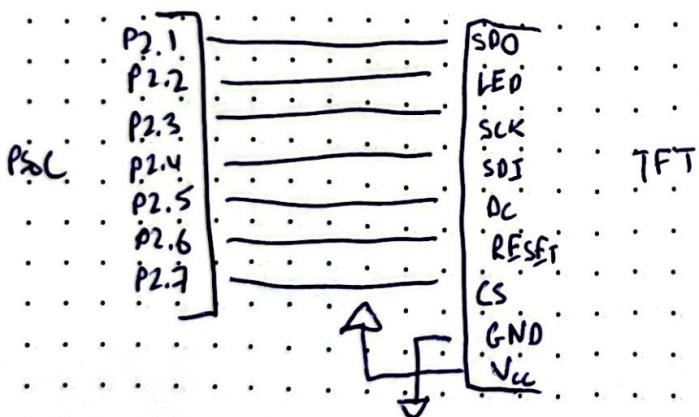

When connected to the PSoC, I made it click if I'm playing along to the song of choice (ode to Joy) and move the cursor to indicate what note is to be pressed. There is no change in the schematic, but below is the picture of the display.


Part IV (cont.);

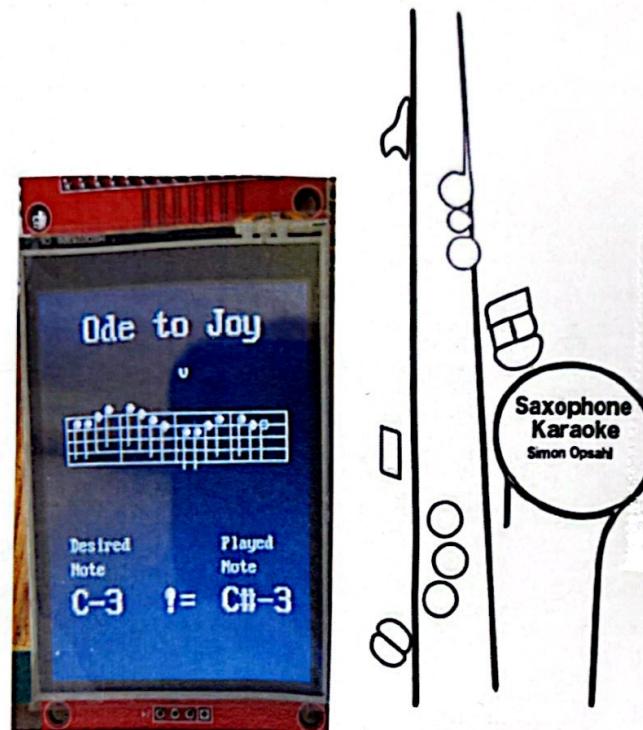I also want to have LEDs indicating which button to press, which can be done, with the following display.




Part V The Sound

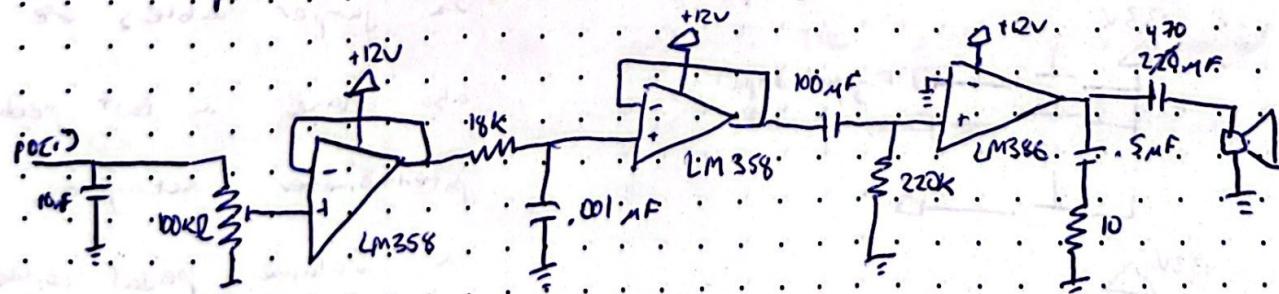The last thing to do is to connect the sound output to a speaker using the following circuit.



Part II (cont.):


The final sound circuit looks like:

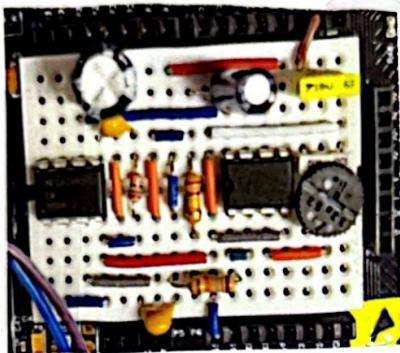

The 12V is supplied by a variable power supply on the breadboard, and the speaker is an 8Ω impedance (EZB-30P-g) that was left laying around.


Part VI: The completed system.

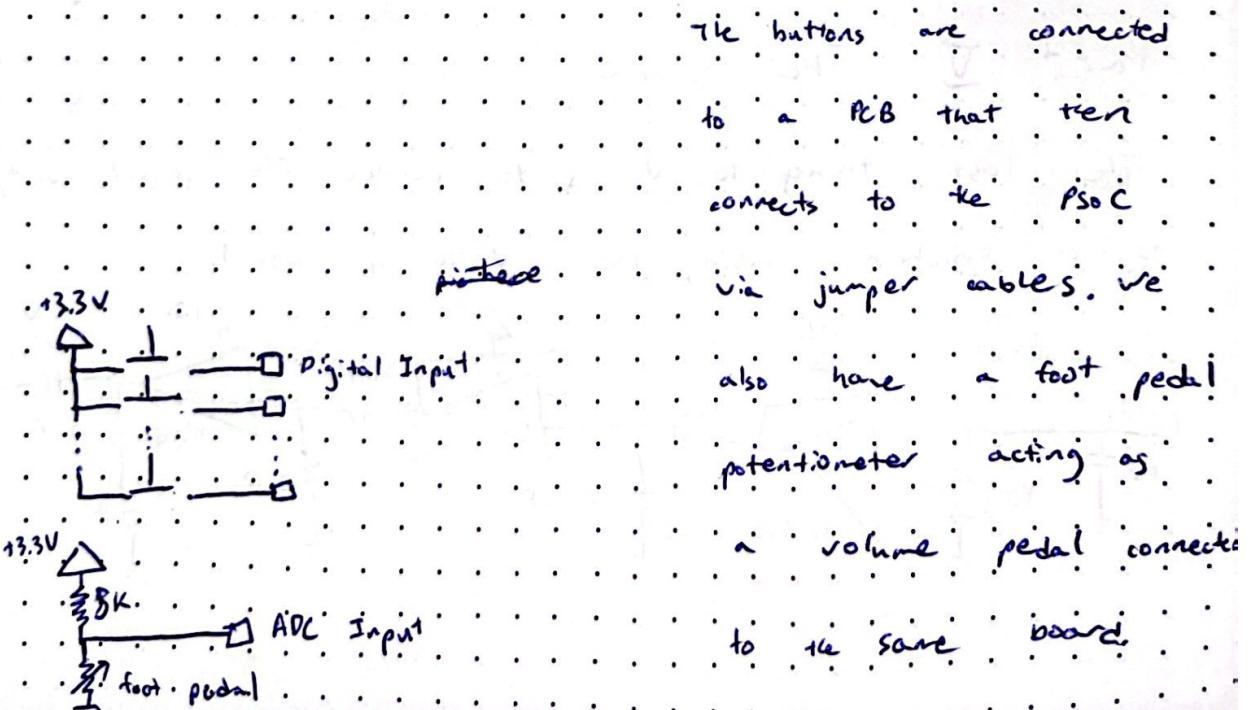The final product consists of a number of parts. We have the buttons on the saxophone itself.



Part VI (cont.):

Next is the sound output. I stored the output of processing some .wav files in matlab with the timer periods needed for each note's sampling frequency. When a new note is selected, the code changes the period and sends a new waveform. The waveform is sent through a filtered DAC buffered by a 10nF capacitor. This is connected in circuit to a series of amplifiers connected to a $+12\text{V}$ variable power supply.

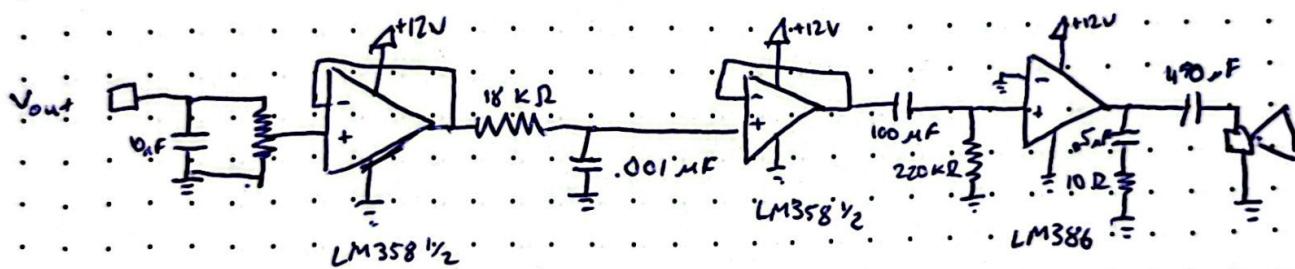

We also have a display. The display is comprised of a TFT that is driven by an ILI9341 chip and a series of LEDs driven by digital outputs. The LEDs tell you what note to press; the display shows the song and if you are correct. The plots of general schematics and pictures of the complete system are on the following page.

Part III (cont.):

