
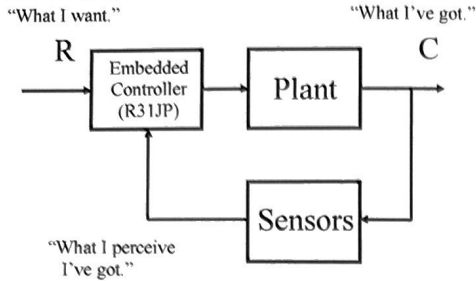


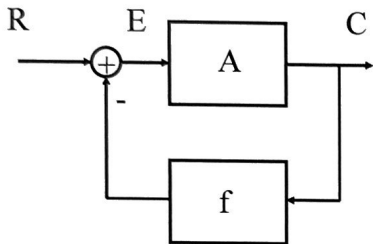Often, we may find an embedded controller in an over all system structure that looks like this:



This is a feedback or “error-driven” structure. Let’s try to understand how it might behave! We’ll surely depend on the characteristics of all 3 blocks.

Before we get to the digital controller, let’s look at an analog example:




1

Aha! But what do we do if one of the blocks (or more) is not simply a gain, but rather a “dynamic” block described by a differential equation?

Answer: Find a way to “pretend” that the differential equation is an algebraic equation!

Laplace Operator Calculus: $\frac{d}{dt} \Leftrightarrow s$

Example:

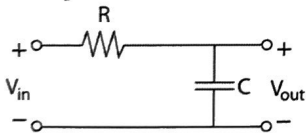

$$i(t) = C \frac{dv_{out}(t)}{dt} \Leftrightarrow i(s) = sC v_{out}(s)$$

$$Z = \frac{1}{sC}$$

Differential Equation:

$$v_{in} = iR + v_{out} = RC \frac{dv_{out}}{dt} + v_{out}$$

Laplace: “impedance” divider:

$$\frac{v_{out}}{v_{in}}(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{sRC + 1}$$

$$\text{or } v_{out} \cdot [sRC + 1] = v_{in} \Leftrightarrow RC \frac{dv_{out}}{dt} + v_{out} = v_{in}$$

3

A little arithmetic:


$$E = R - fC$$

$$C = AE = A(R - fC)$$


Collecting terms:

$$C + AfC = AR \text{ or } \frac{C}{R} = \frac{A}{1 + Af} \leftarrow \text{BLACK'S FORMULA}$$

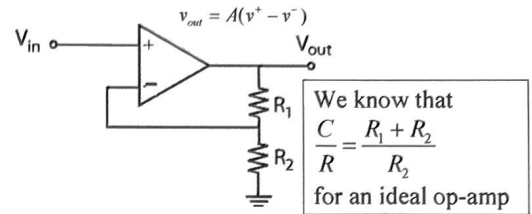Example: Non-inverting op-amp gain block:




In block diagram form:

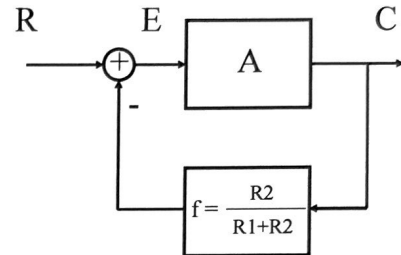


$$\text{According to Black's formula: } \frac{C}{R} = \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \rightarrow \frac{R_1 + R_2}{R_2} \text{ as } A \rightarrow \infty$$

2


Unit step response of this RC circuit:

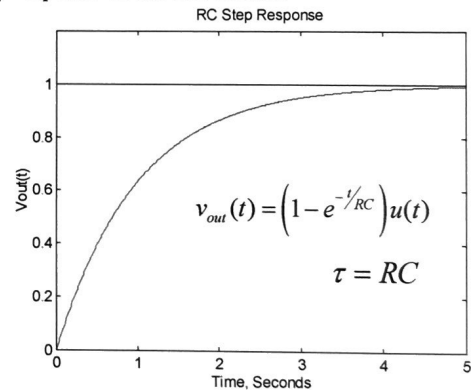

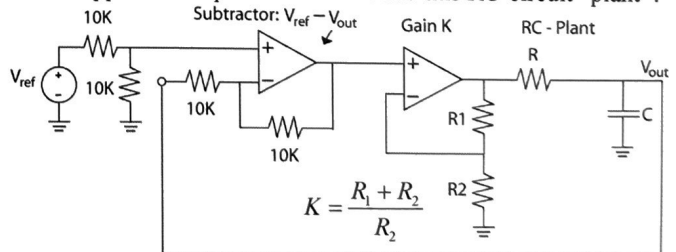What happens if we put feedback around this RC-circuit “plant”?



Block Diagram:

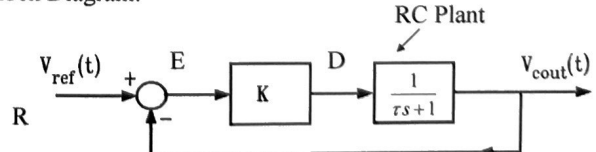

4

Apply Black's formula: $A = \frac{K}{\tau s + 1} \quad f = 1$

$$\frac{C}{R} = \frac{\frac{K}{\tau s + 1}}{1 + \frac{K}{\tau s + 1}} = \frac{K}{\tau s + 1 + K} = \frac{K}{\frac{\tau}{1+K} s + 1}$$

Pole-zero plot:

ORIGINAL RC CIRCUIT:

Recall Solution:


$$v_{out}(t) = C = \left[1 - e^{-t/\tau} \right] u(t)$$

"natural frequency"

$$s = -\frac{1}{RC}$$

$$v_{out} = \frac{K}{1+K} \cdot \left[1 - e^{-t/\tau_{1+K}} \right] u(t)$$

starts here near small $K \sim 0$

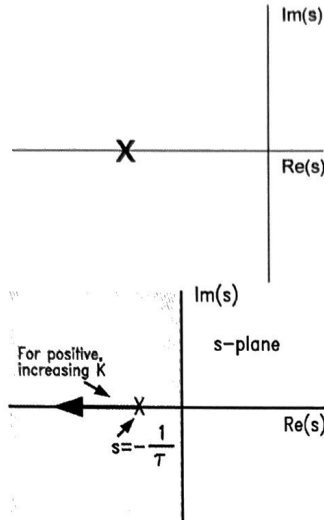


Always stable: steady state error, transient response improve as K gets large.

5

Why does the overall system appear to get "faster" if we use feedback with high gain?


Let's see how the loop "kicks" the plant.

That is what's $\frac{D}{R}(s)$?

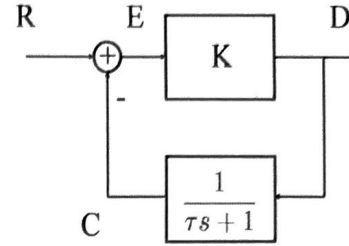

$$\frac{D}{R}(s) = \frac{K}{1 + \frac{K}{\tau s + 1}} = \frac{K(\tau s + 1)}{\frac{1+K}{s\tau} + 1} = \frac{K}{1+K} \cdot (\tau s + 1) \cdot \frac{1}{\frac{\tau}{1+K} s + 1}$$

Here is the exponential rise:



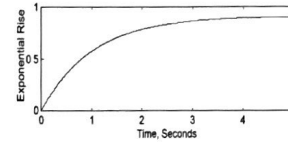


Scales by $\frac{K}{1+K}$ takes the rise "as is" This is our actual exponential rise

$$\left[1 - e^{-t/\tau_{1+K}} \right] u(t)$$

So $D(t)$ is the sum of two pieces:

6

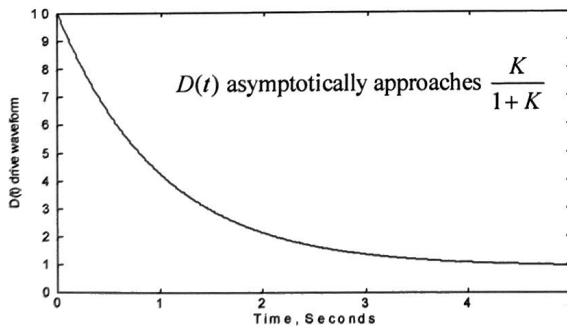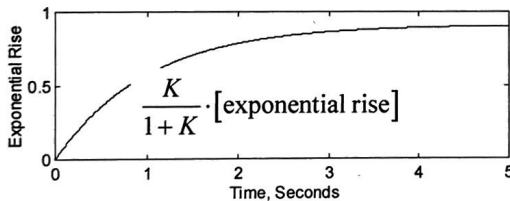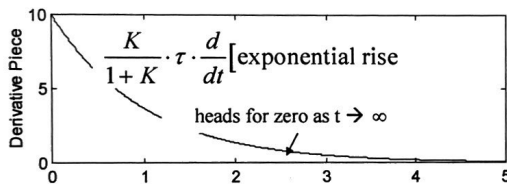

Initially, it "kicks" the RC plant very hard (relative to steady state) to get it "moving"...

7