



Speaker playback circuit

NOTE: The 12V IC's should be powered from the kit's variable power supply, not the kits fixed 12V supply, which is reserved for the R31-JP