 


We have discussed his activities...




But who is he?  
 How is he constructed?  
 Can we make our own?  
 Finite State Machines




See Horowitz and Hill, 2<sup>nd</sup> edition, Chapter 8, for more details on these topics and descriptions of these included figures.

1

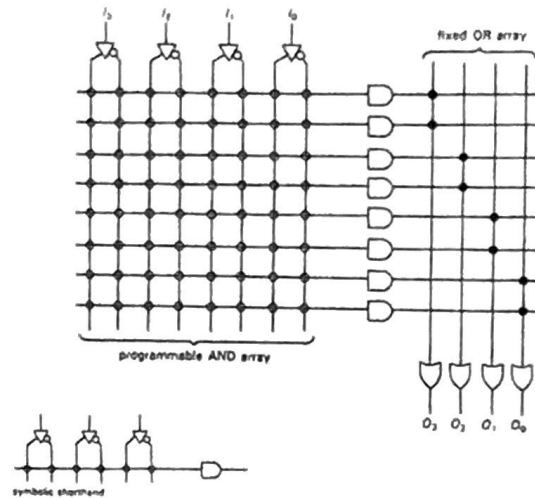A convenient way to make a bank of combinational logic, or a collection of gates programmable logic devices. We use one on our R31JP (Xilinx 9536 PLD) to create the XIO select line, and to switch memory positions for mon/run. Here's a simple model of part of a simple PAL.




 Note the schematic shorthand used to describe the programmable array




2

 A combinational PAL (16L8, with 16 inputs max and 8 outputs max:



3

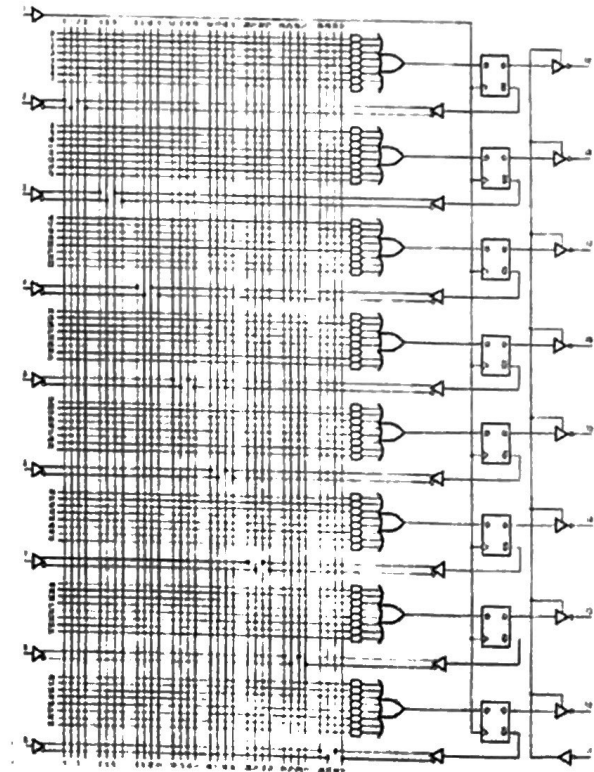A PAL with registered outputs. The flip-flops can be used to make counters or as memory for "state". This is a 16R8



4


## DIP

Display decoder, from Horowitz and Hill:

Here's the PAL in your chip kit:

It can be programmed with the CUPL language compiler, similar in many ways to RASM.

 Be careful when programming to avoid poor logic, race conditions, designs that won't fit in the device, etc:




```

/** Inputs **/
PIN 1 = a ; /* segment a */
PIN 2 = b ; /* segment b */
PIN 3 = c ; /* segment c */
PIN 4 = d ; /* segment d */
PIN 5 = e ; /* segment e */
PIN 6 = f ; /* segment f */
PIN 7 = g ; /* segment g */


/** Outputs **/
PIN 19 = !D3 ; /* msb of hex encode */
PIN 18 = !D2 ; /*
PIN 17 = !D1 ; /*
PIN 16 = !D0 ; /* lsb

```

Two-Bit Selector:  
With race condition:

 

With a fix for static race condition:

 


```

/** Declarations and Intermediate Variable Definitions **/
zero = a & b & c & d & e & f & g ;
one = !a & b & c & d & e & f & g ;
two = a & b & c & d & e & f & g ;
three = !a & b & c & d & e & f & g ;
four = !a & b & c & d & e & f & g ;
five = a & b & c & d & e & f & g ;
six = !a & b & c & d & e & f & g ;
seven = a & b & c & d & e & f & g ;
eight = a & b & c & d & e & f & g ;
nine = !a & b & c & d & e & f & g ; /* two ways */
hexa = a & b & c & d & e & f & g ;
hexb = !a & b & c & d & e & f & g ;
hexc = !a & b & c & d & e & f & g ;
hexd = !a & b & c & d & e & f & g ; /* two ways */
hexe = a & b & c & d & e & f & g ;
hexf = a & b & c & d & e & f & g ;


/** Logic Equations **/
D3 = eight # nine # hexa # hexb # hexc # hexd # hexe # hexf ;
D2 = four # five # six # seven # hexc # hexd # hexe # hexf ;
D1 = two # three # six # seven # hexa # hexb # hexe # hexf ;
D0 = one # three # five # seven # nine # hexb # hexd # hexf ;

```

Finite State Machine for a Motor Drive:

 

Hardware Implementation:

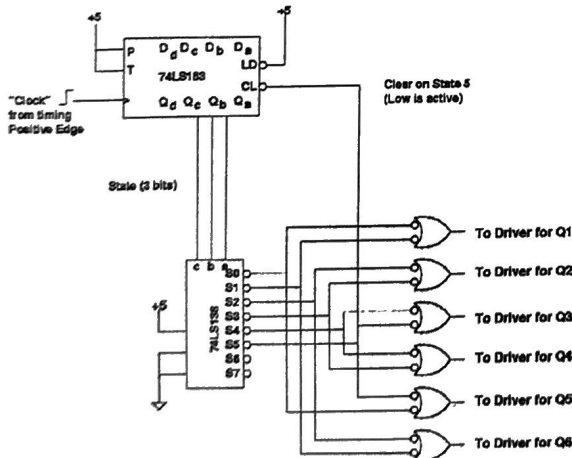

Implementation of a 138 selector in CUPL:

```

Name          demuxer;
Partno        ;
Revision      01;
Date          8/10/08;
Designer      PLD Expert;
Company       MIT;
Location      None;
Assembly      None;
Device        g22v10;

```

/\* Simple combinatorial logic: 2-to-1 MUX \*/

```

pin 2 = a;
pin 3 = b;
pin 4 = c;
pin 5 = xiosel;

```

```

pin 14 = d;
pin 15 = e;
pin 16 = f;
pin 17 = g;
pin 18 = h;
pin 19 = i;
pin 20 = j;
pin 21 = k;

```

```

d = xiosel # !(a & !b & !c);
e = xiosel # !(a & !b & !c);
f = xiosel # !(a & !b & !c);
g = xiosel # !(a & !b & !c);
h = xiosel # !(a & !b & !c);
i = xiosel # !(a & !b & !c);
j = xiosel # !(a & !b & !c);
k = xiosel # !(a & !b & !c);

```